



POLITECNICO
MILANO 1863



TUTORING on ELECTRONICS

2021-22 academic year

Iris CUSINI and Fabio SEVERINI





Power supply

Typology:

single-

or

dual- power supply

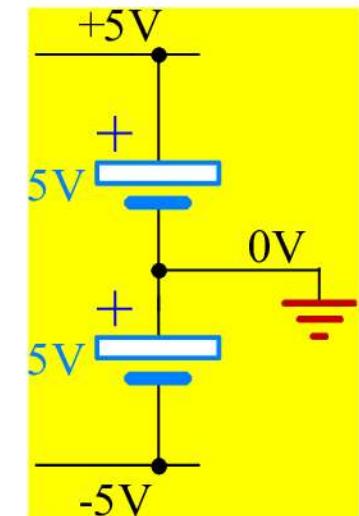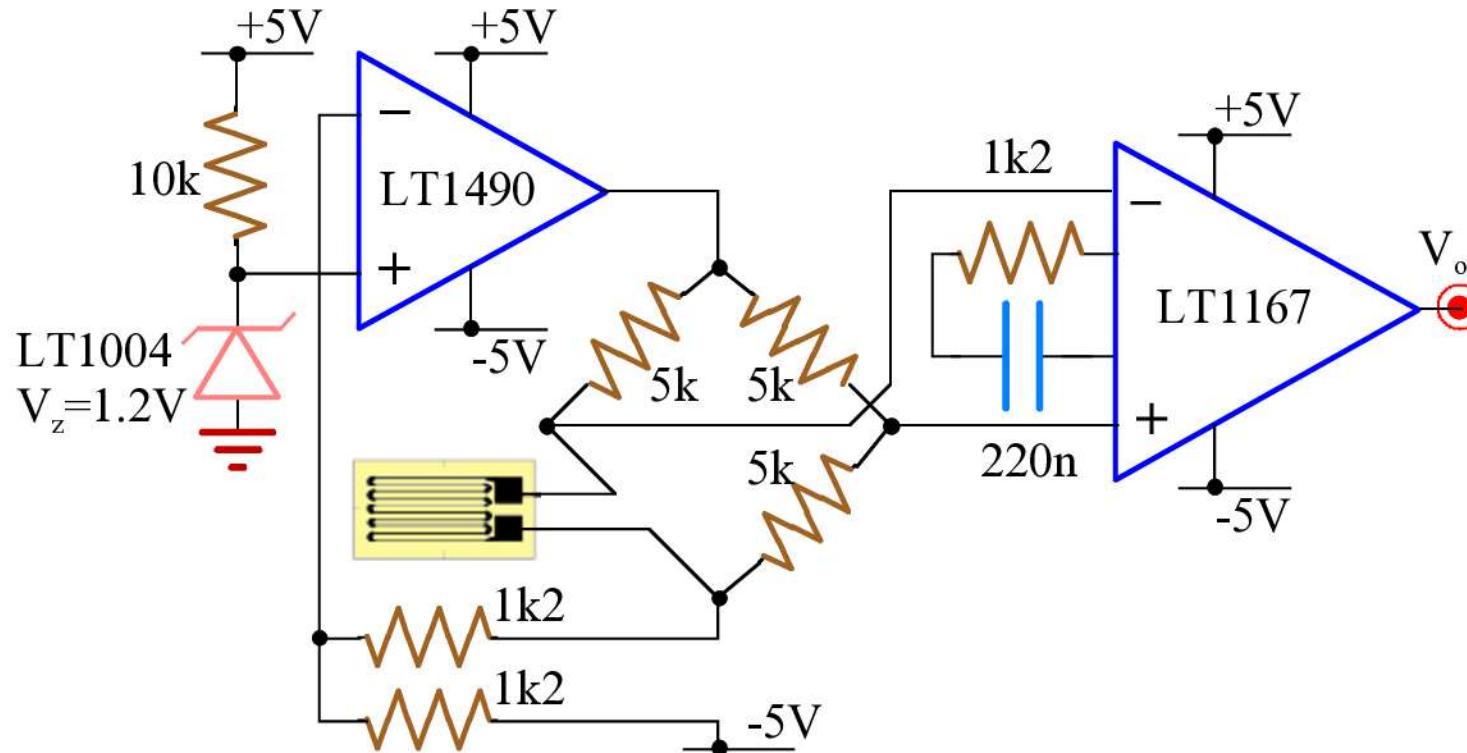

GROUND: local 0V reference



usually it is the copper plate of the printed circuit board

it can also be the chassis connection and possibly **EARTH**




Ohm's law applies only to R

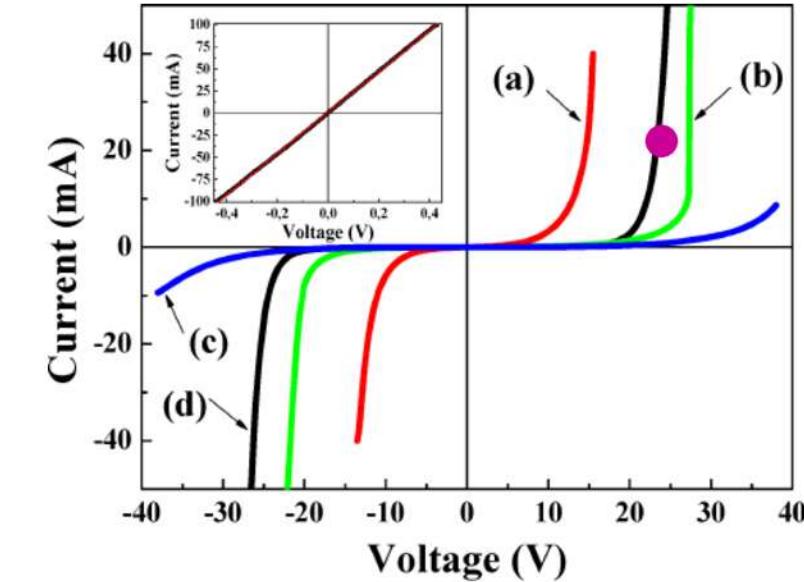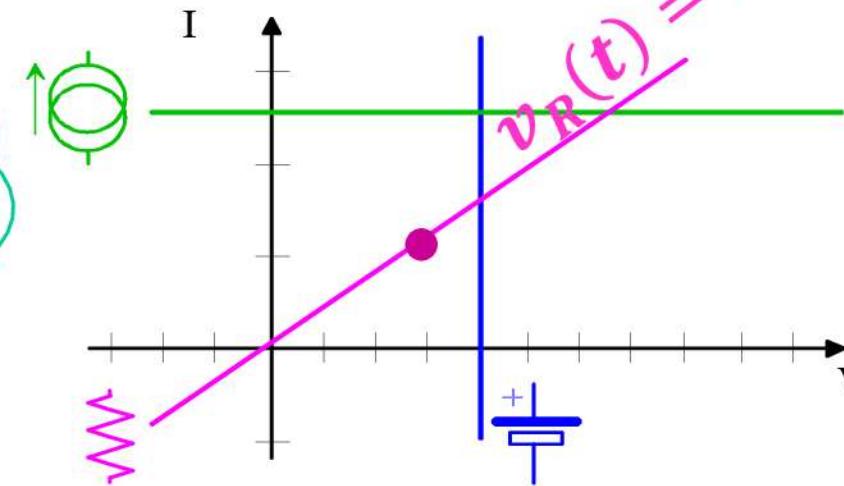I applied 3V,
then I measured
1mA, so $R=3\text{k}\Omega$



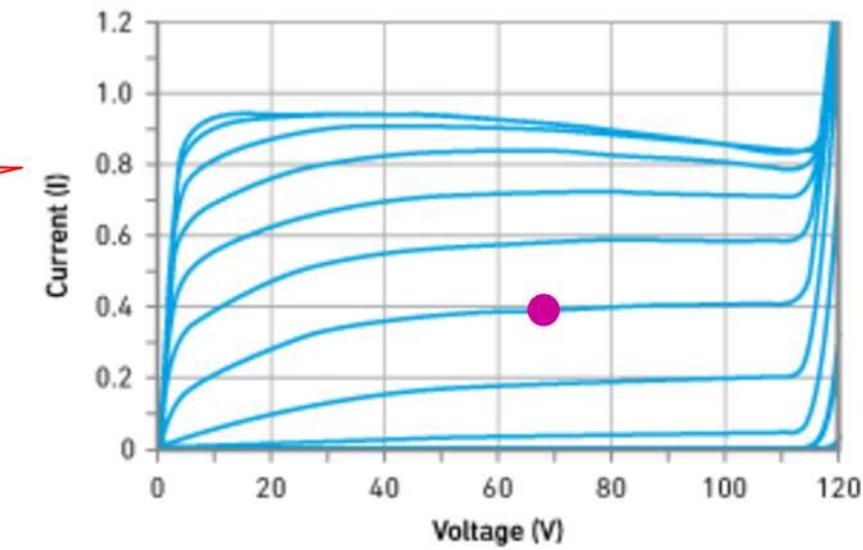NO!
Most components exhibit
NON-LINEAR IV response!







Frequency response is of utmost importance

Not just to Low-Pass, Band-Pass, High-Pass, Notch, but also for Integrators, Derivators...

Audio example

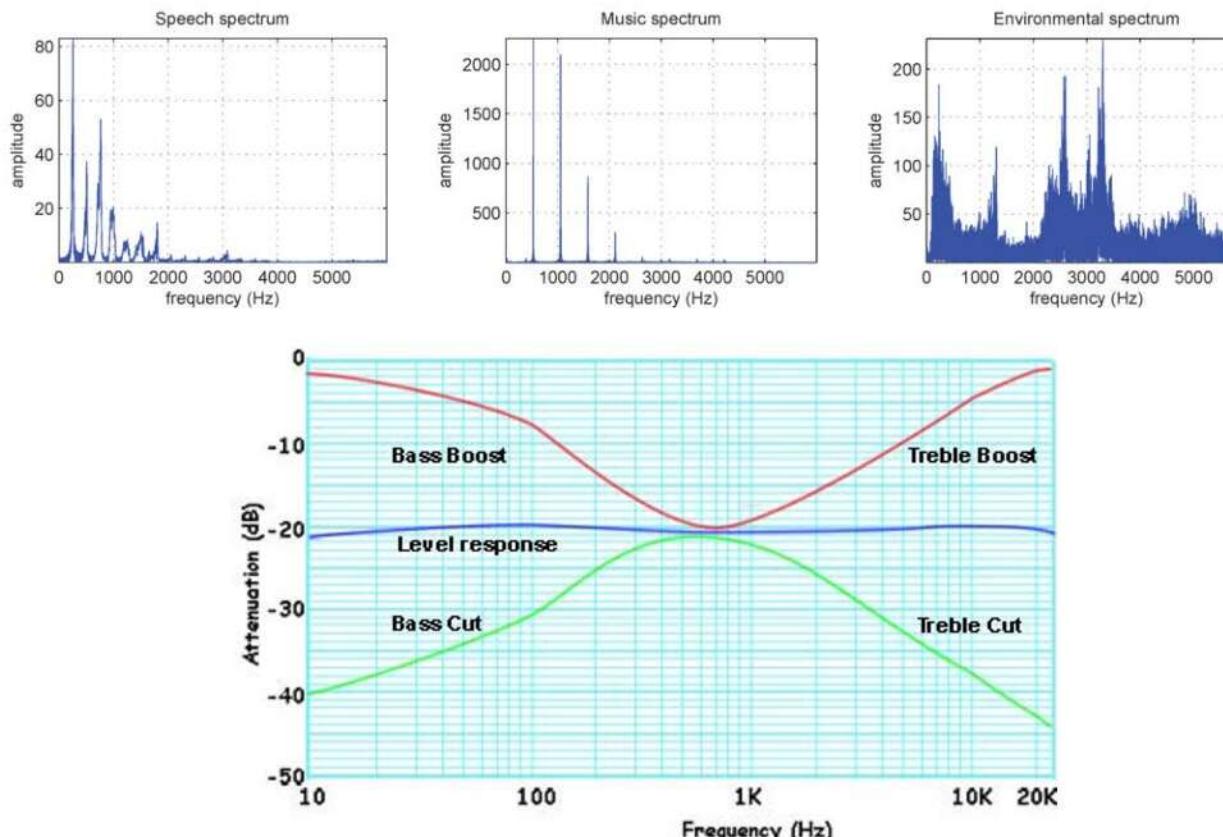



ECG example

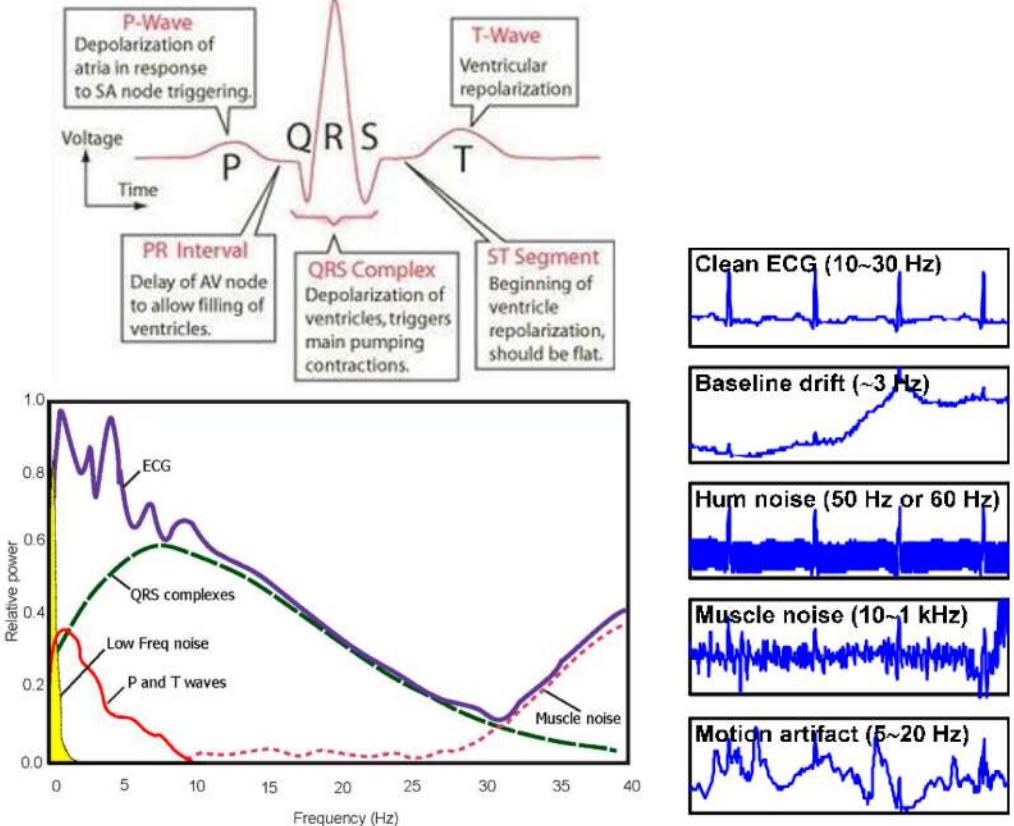




"Smart" frequency analysis:

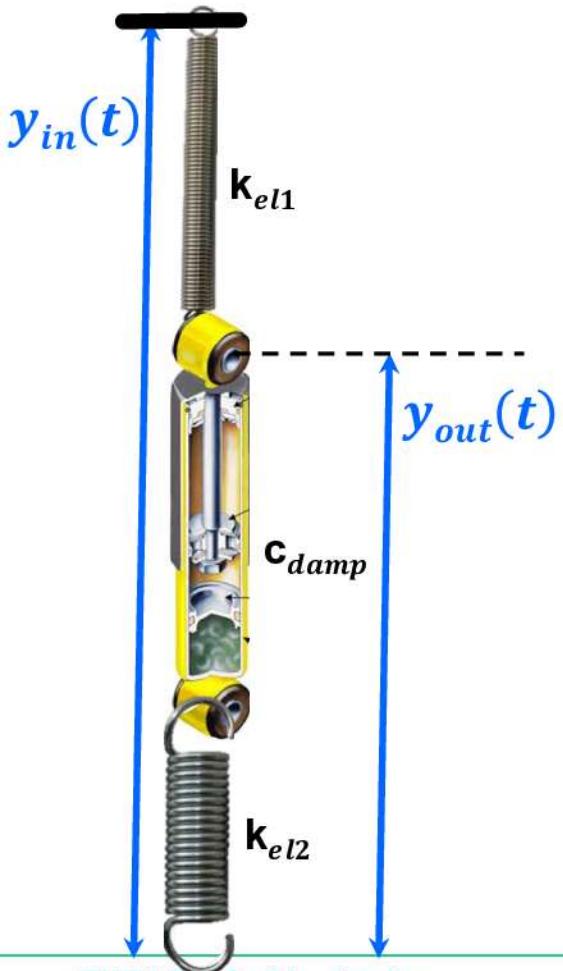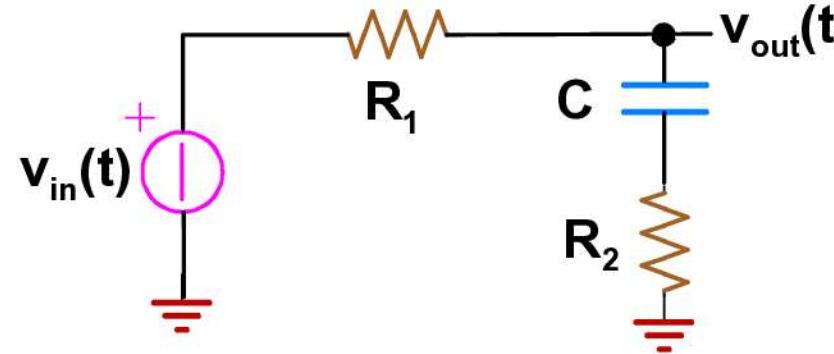Given a circuit and sinusoidal signal sources...



... complex impedances must be considered


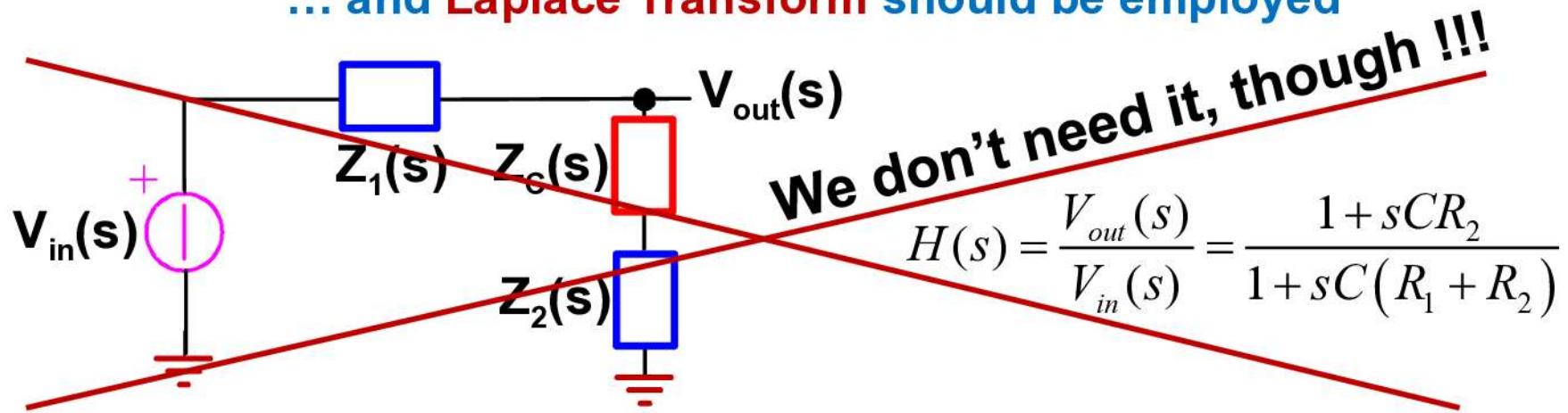
... and Laplace Transform should be employed






... “asymptotic analysis”

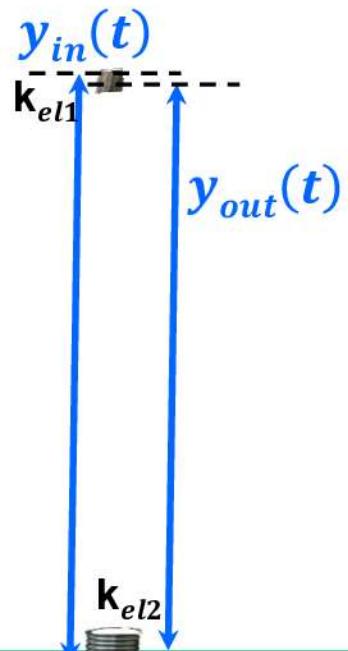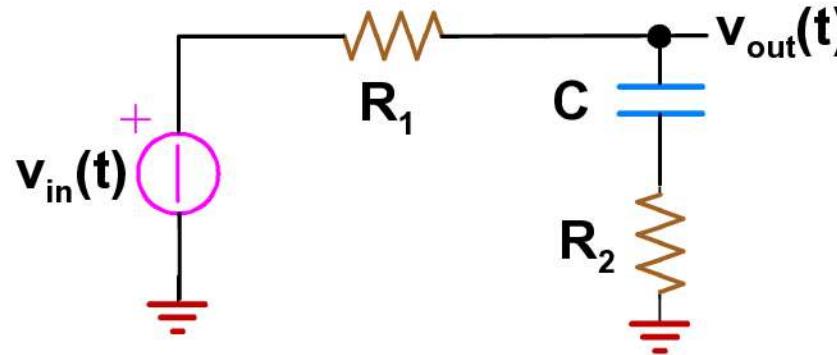1- We simply evaluate the circuit response at **0Hz** and **∞ Hz**





at DC:
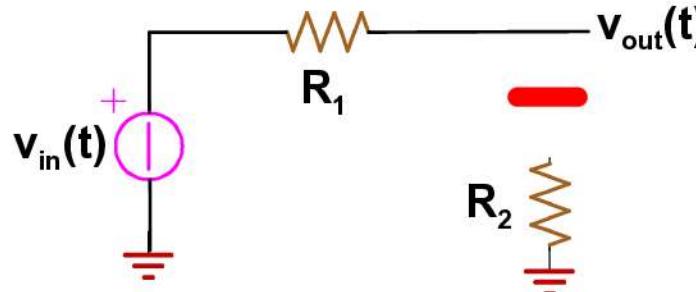
$$A_V(0) = \frac{v_{out}(0)}{v_{in}(0)} = 1$$



at ∞ Hz:

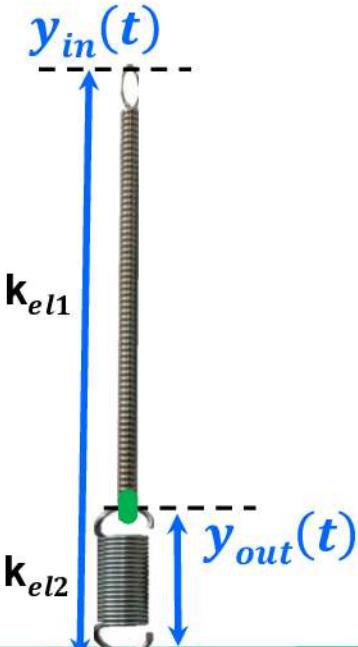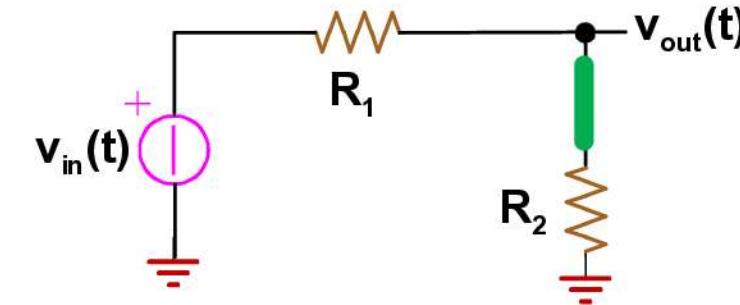
$$A_V(\infty) = \frac{v_{out}(\infty)}{v_{in}(\infty)} = \frac{R_2}{R_2 + R_1}$$





“Heartily” proposed analysis

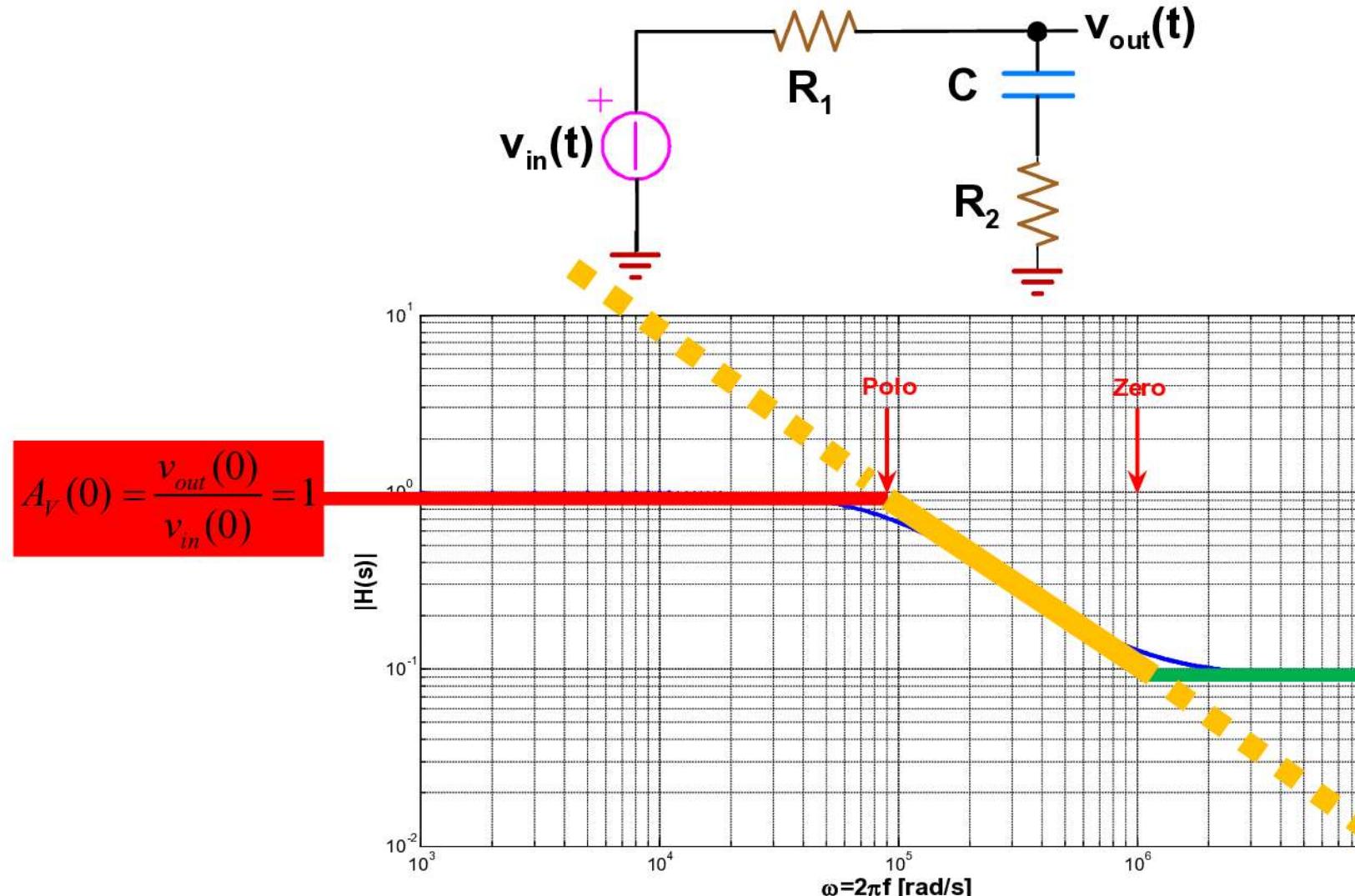2- Then, we join the **0Hz** and **∞ Hz** asymptotic trends through a **line** in log-log plot



$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{1 + sCR_2}{1 + sC(R_1 + R_2)}$$

In fact, above the pole, this "1" becomes negligible, so it decreases as $1/f$





Bode diagrams


-20dB/dec: $A_1 \cdot f_1 = A_2 \cdot f_2$ the so called constant **Gain-Bandwidth Product GBWP**

$$+20\text{dB/dec}: \frac{f_1}{A_1} = \frac{f_2}{A_2}$$
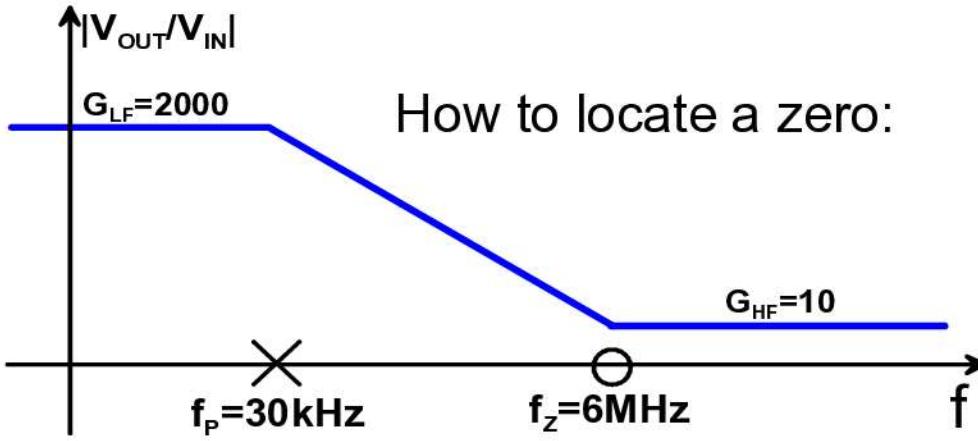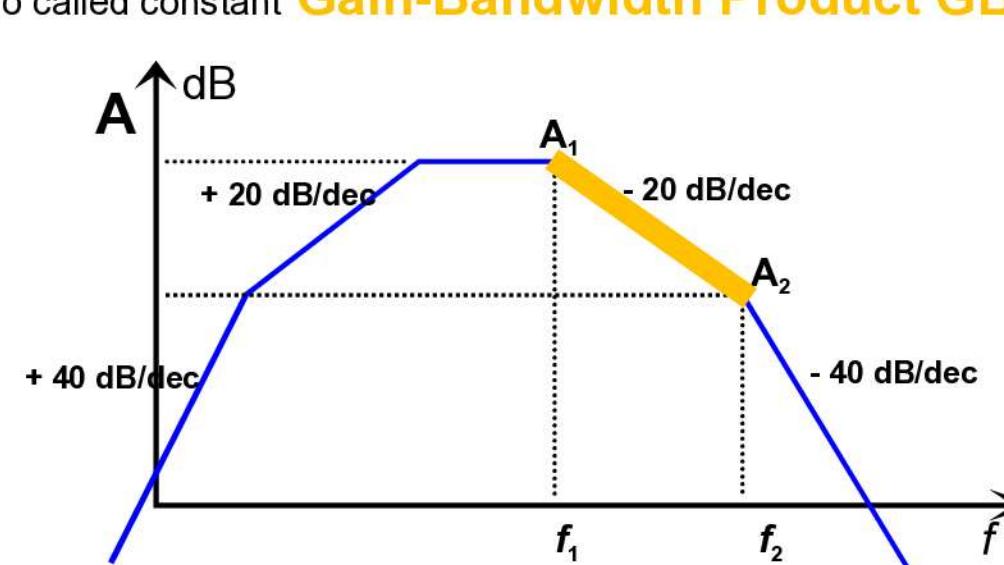
$$-40\text{dB/dec}: \sqrt{A_1} \cdot f_1 = \sqrt{A_2} \cdot f_2$$



How to locate a zero:

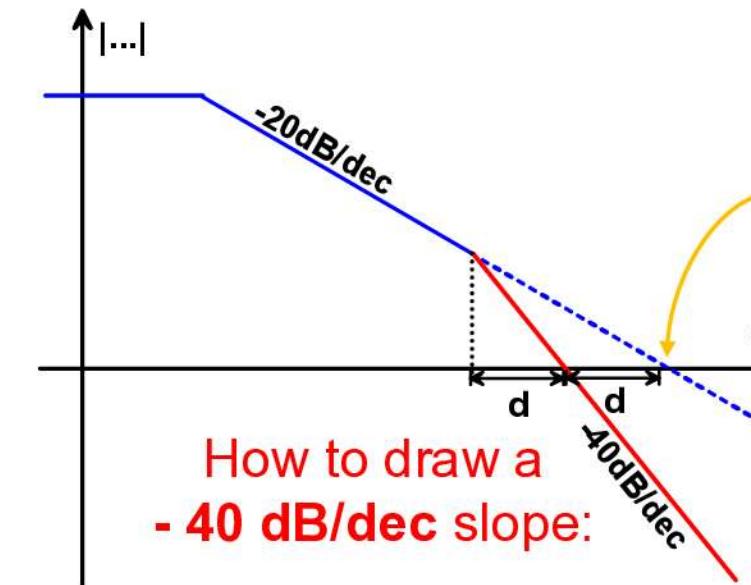

How to draw a
- 40 dB/dec slope:



How to compute poles




Switch off all generators ($V=0$ is a short-circuit, while $I=0$ is an open-circuit)

Don't care where inputs and outputs are!

Compute the overall Resistance "seen" by the Capacitor!



CAPACITÀ NON
INTERAZIONI CALCOLO LA
RESISTENZA VISTA AI
CAPI DEL CONDENSATORE
E TRAVO I Poi
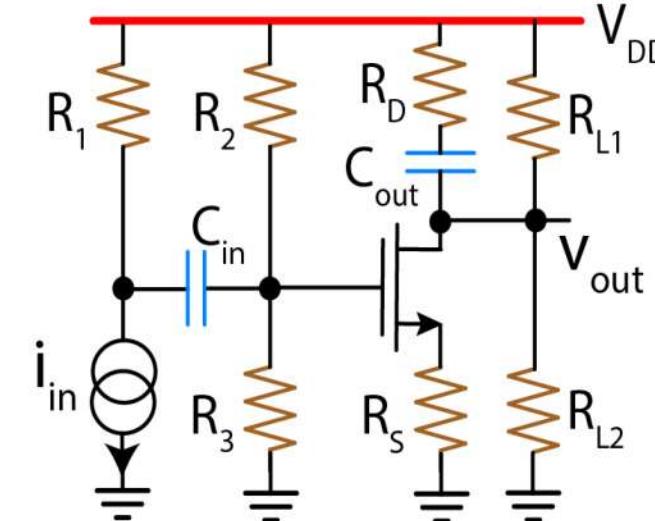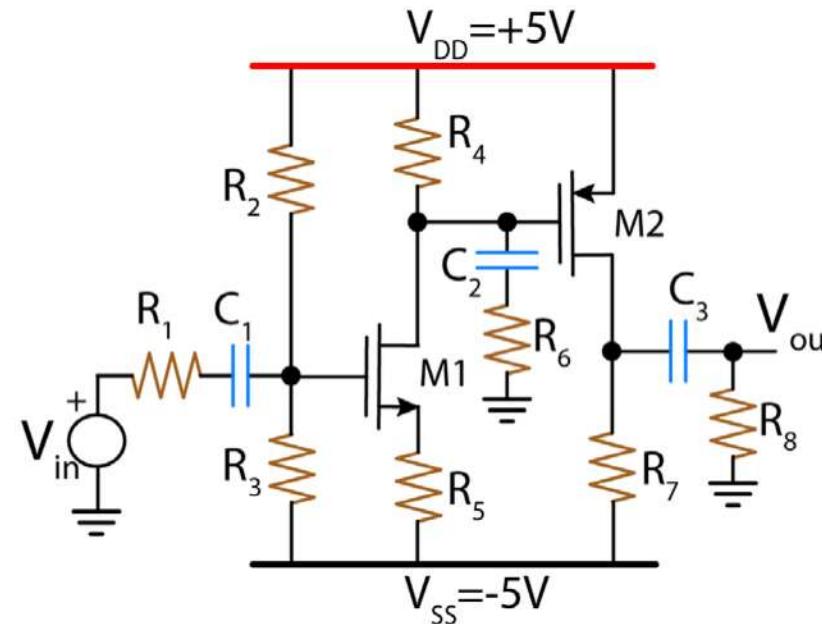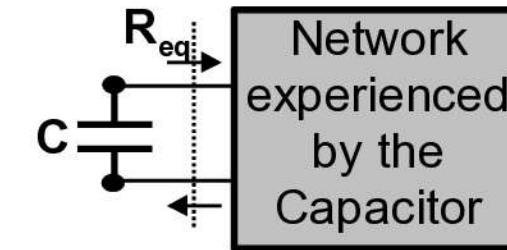
$$polo_{Hz} = \frac{1}{2\pi \cdot R_{eq} \cdot C}$$







How to compute poles

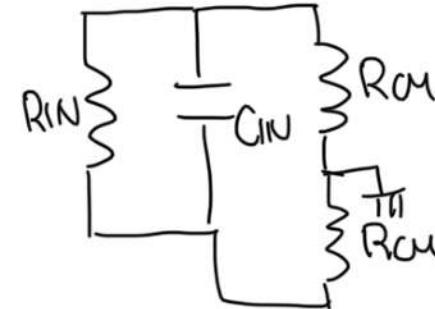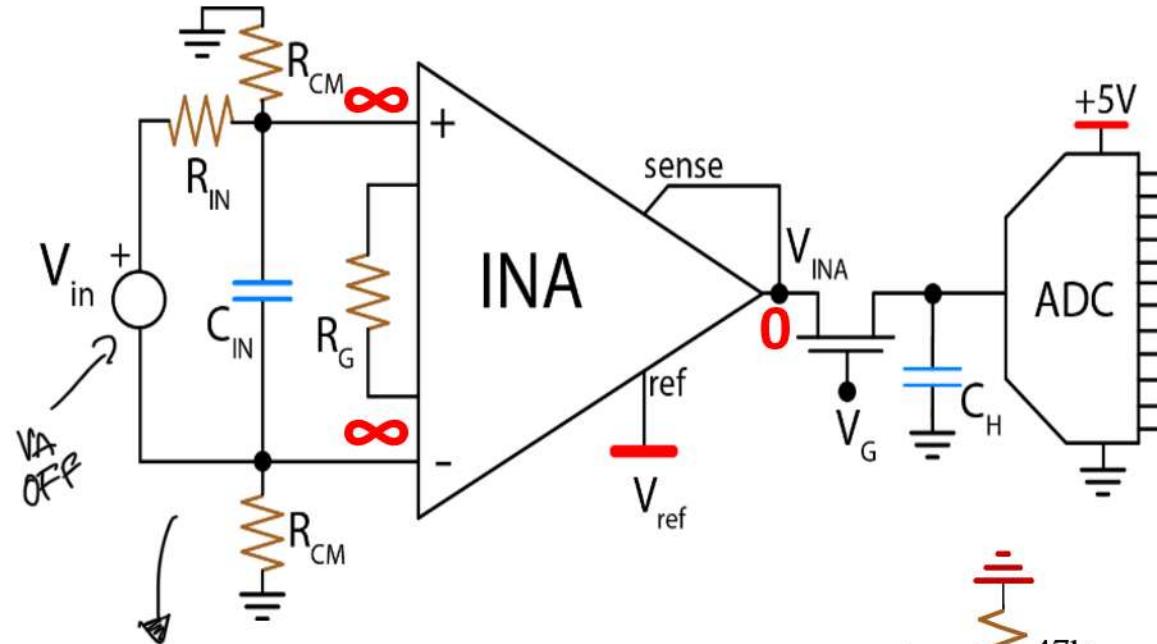

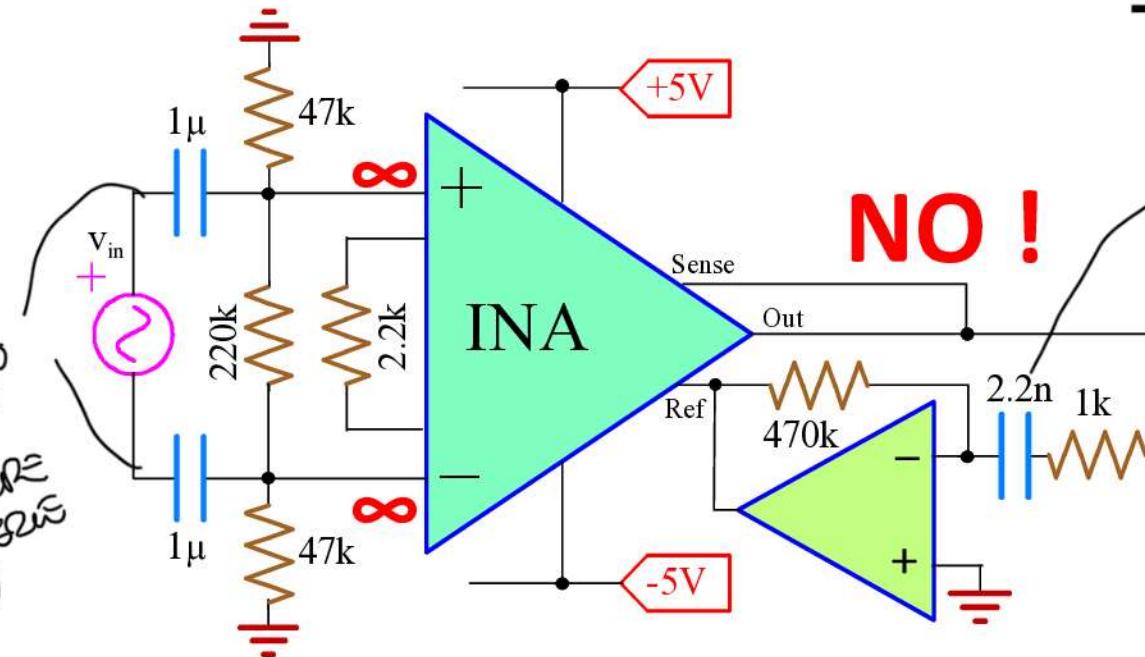CONSIDERO
COSÌ UN
SINGOLO
CONDENSATORE
(CONTI LA SERIE
DEI 2)




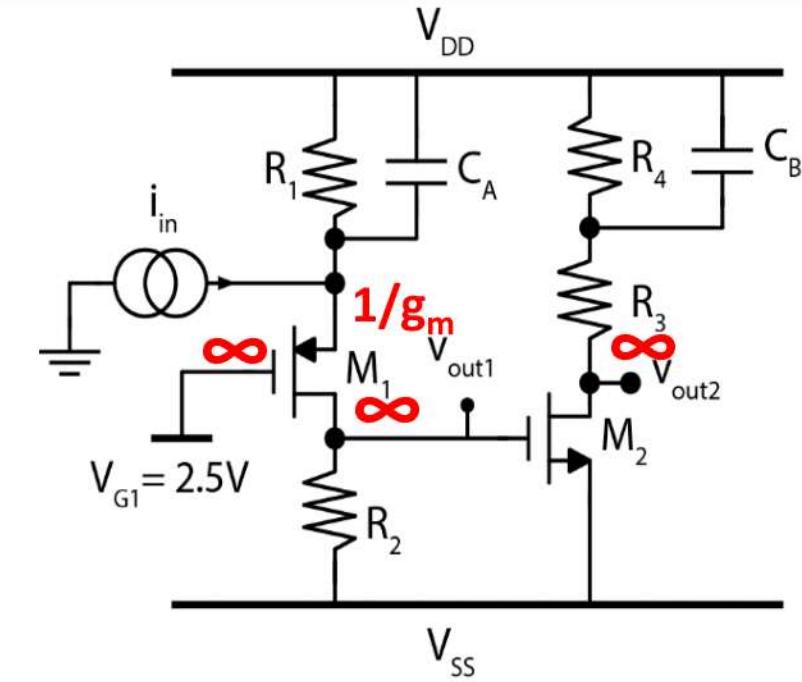Ogni volta che un
condensatore
toca un nodo
di feedback allora
non possiamo
calcolare il
pole in modo
easy









BEWARE OF FEEDBACK !

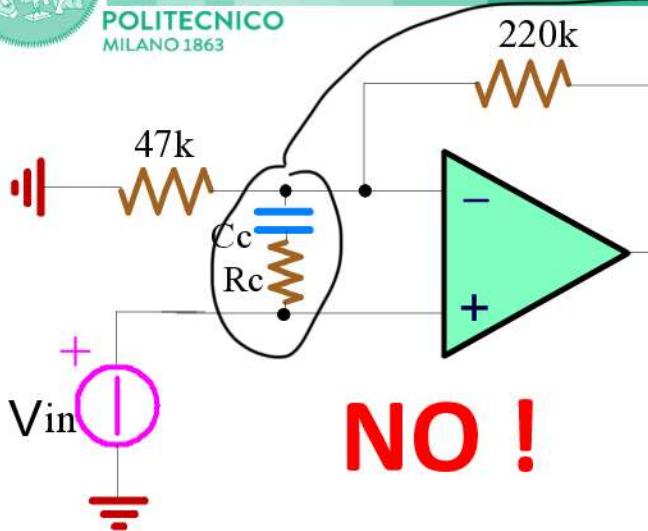

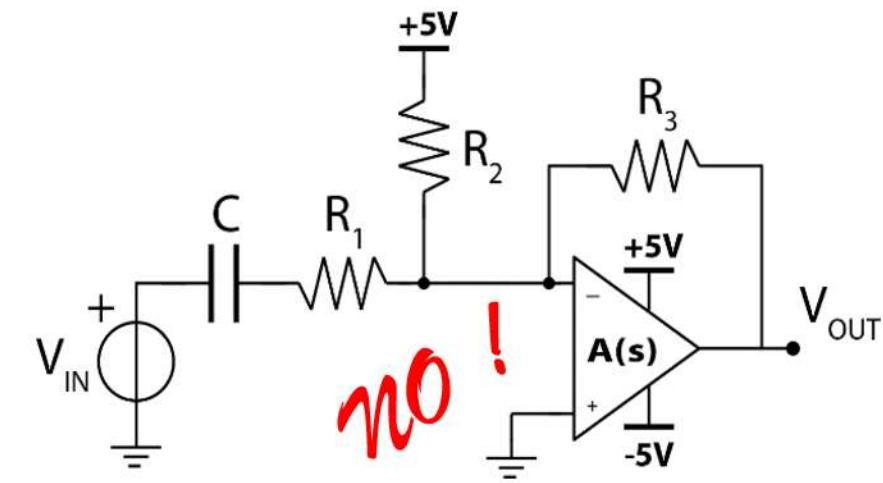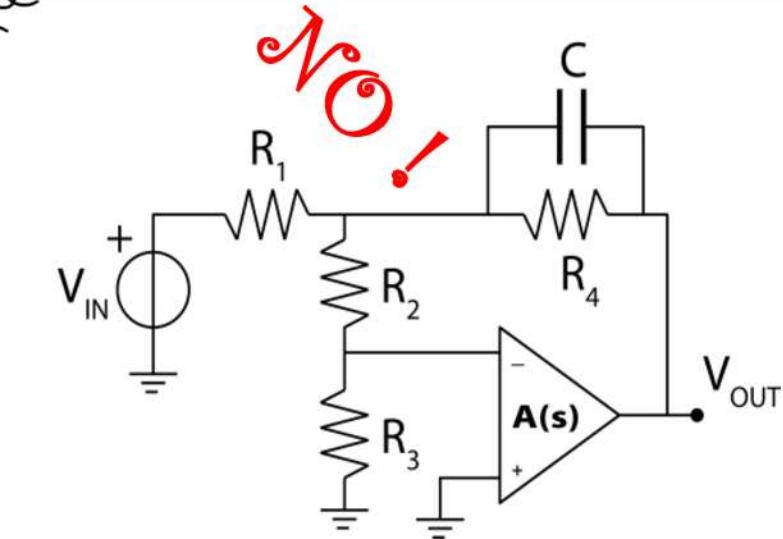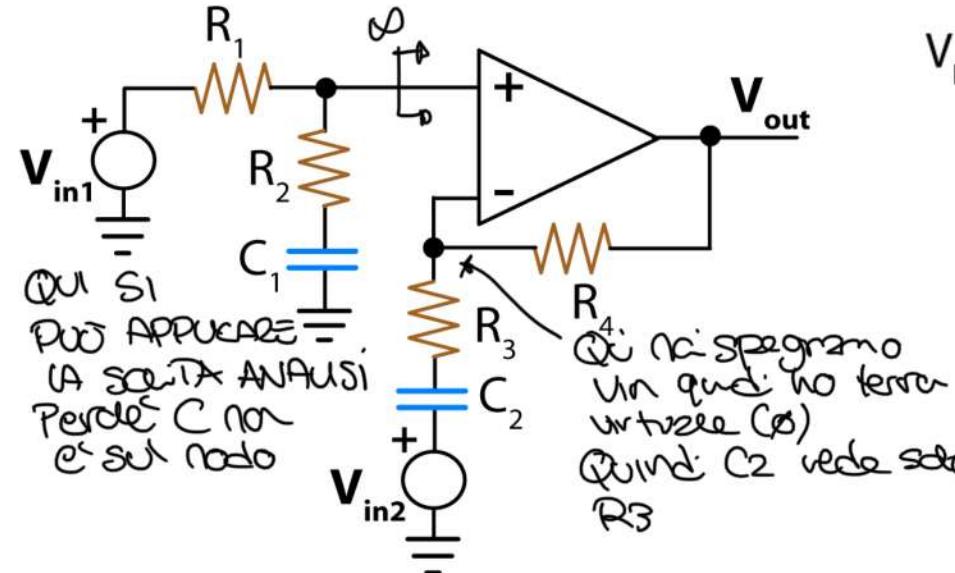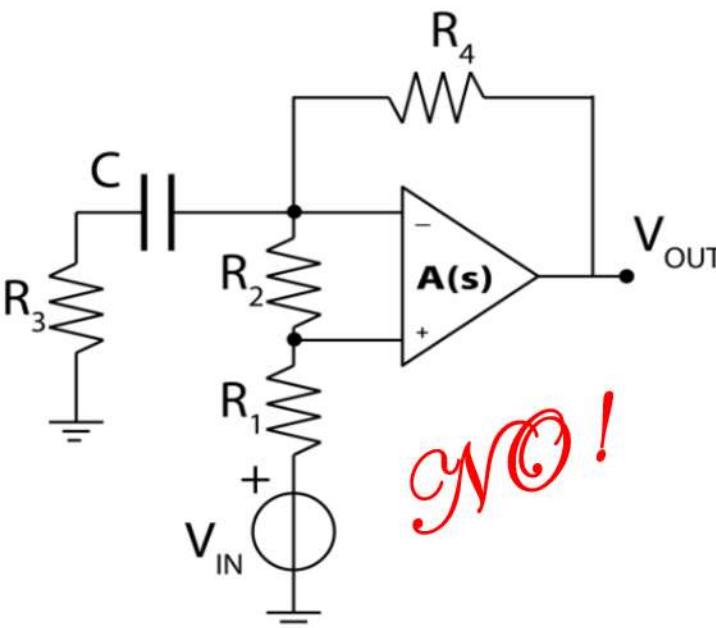L'OPAMP cerca di fare tutto per tenere la terra virtuale. Perciò se tolgo il condensatore per misurare la resistenza vedo che tutta la caduta di tensione cade su R_C , allora $V_C = R_C I_C \rightarrow R_{eq} = R_C$





How to compute zeros

– direct way


Switch off all generators (**V=0** is a short-circuit, while **I=0** is an open-circuit) **apart from the Input**

1. Apply a generic (NOT NIL) signal to the actual Input

2. Pretend to have a generic signal $V_C(t)$ and $I_C(t)$ on the C under test

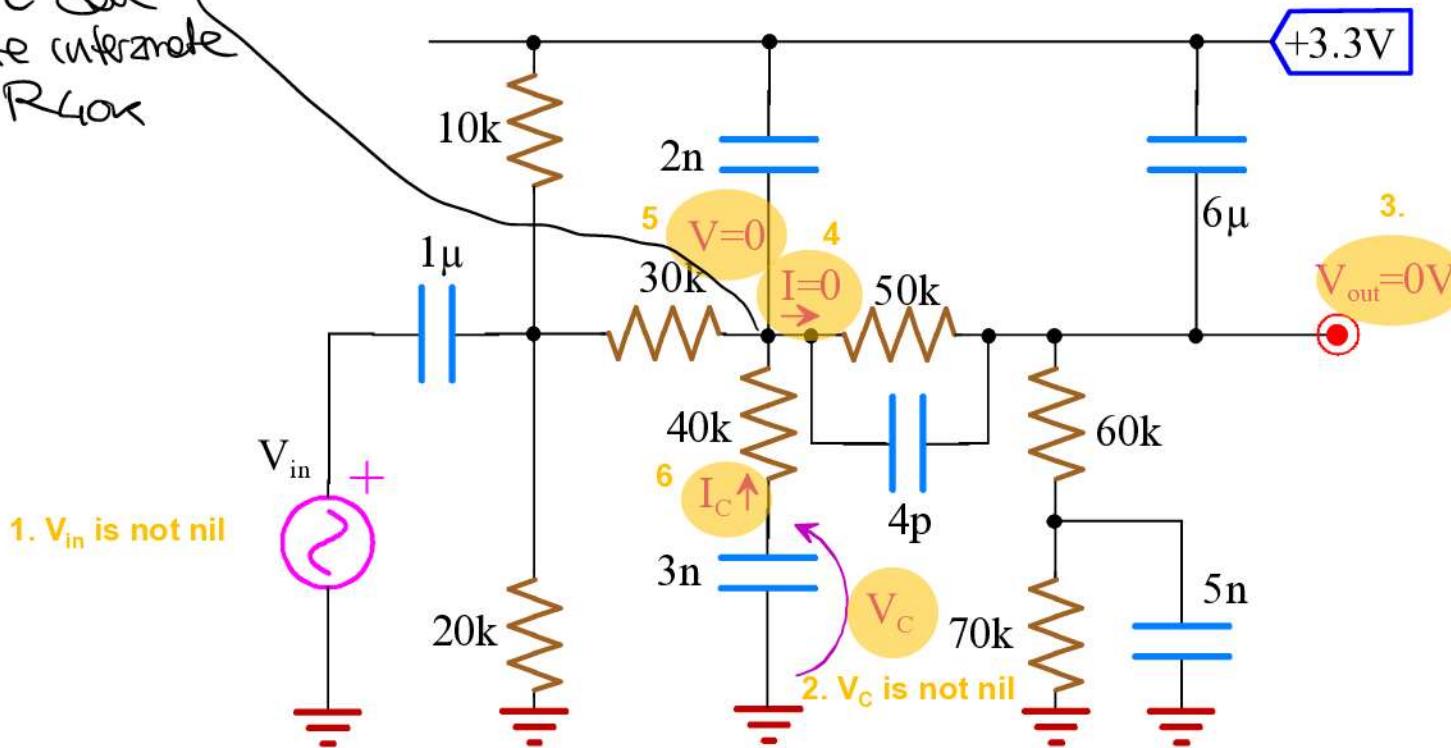3. Check if the Output can indeed be NIL anyhow

Questa nodo è
a terra visto che
 V_{out} è a terra
allora la caduta
su V_C deve
essere inferiore
su R_{40k}



Noi supponiamo $V_{out} = \emptyset$, quindi
corrente a 0 nel nodo
Poi supponiamo una tensione sul
condensatore e vediamo che giro
di caduta la tensione deve essere lo
stesso per avere $V_{out} = \emptyset$

$$7 \\ I_C = -\frac{V_C(s)}{1/sC} = \frac{V_R(s)}{R} = \frac{V_C(s)}{R}$$

$$8 \\ s = \text{zero} = -\frac{1}{R \cdot C}$$

$$f_{\text{zero}} = \frac{1}{2\pi \cdot R \cdot C}$$




How to compute zeros – most common cases

Quando abbiano
dei condensatori nel path
principale, allora,
Se ho un solo condensatore
ho uno zero nell'origine

$$f_{\text{zero}} = 0$$

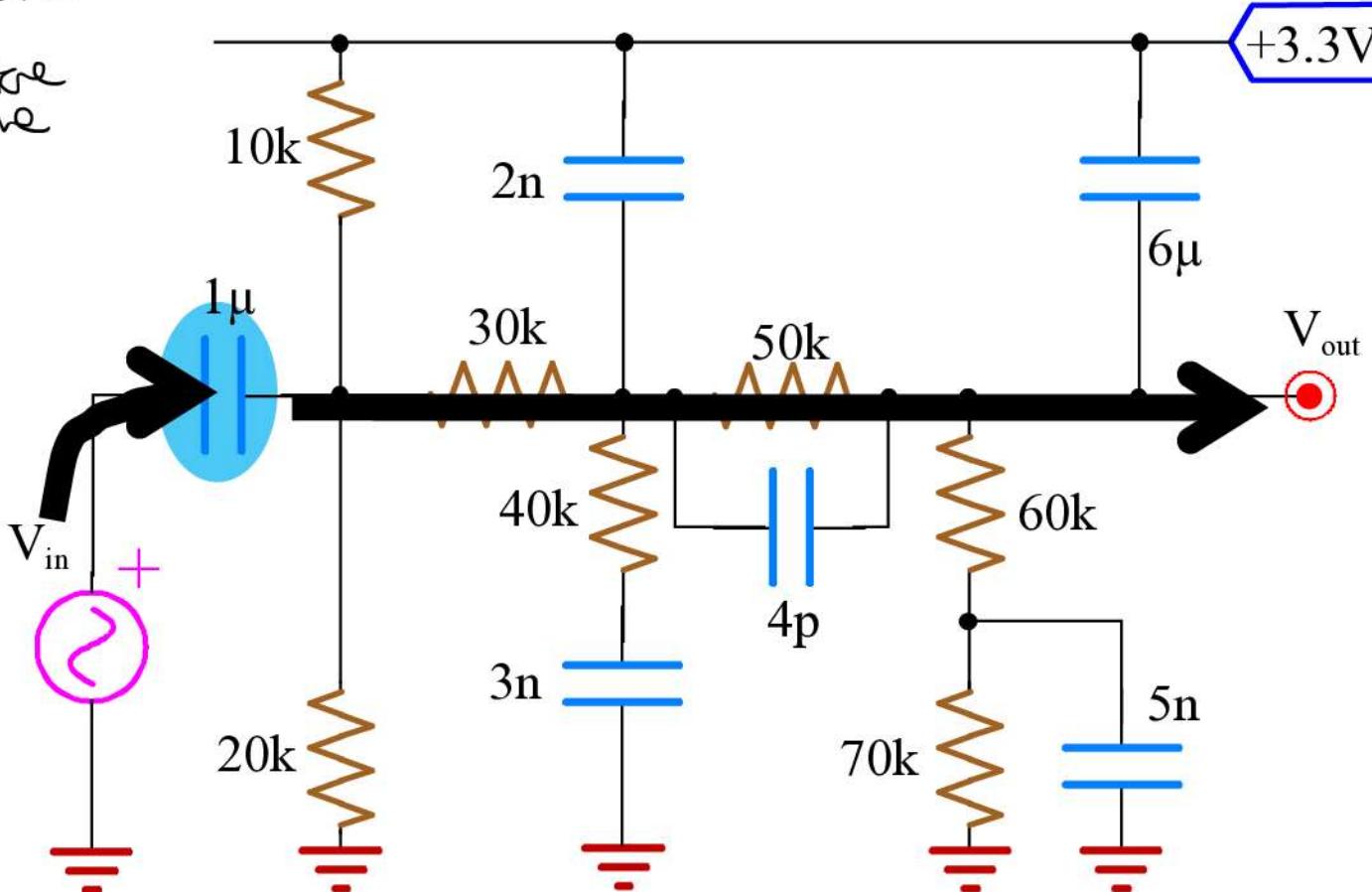
A Capacitor **along the signal path**: a zero at the origin





How to compute zeros – most common cases

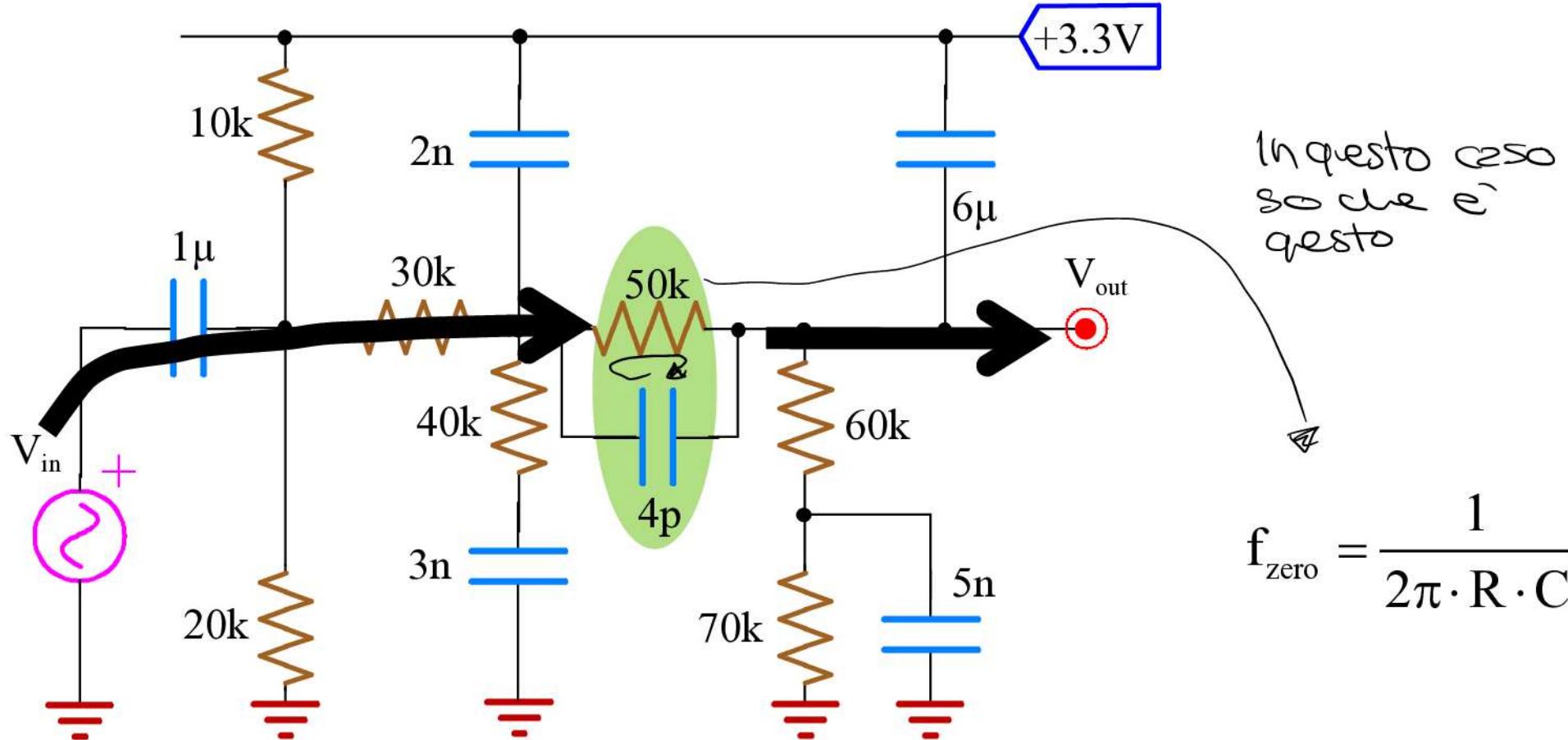
An **RC-shunt along the signal path**: a zero at finite frequency





How to compute zeros – most common cases

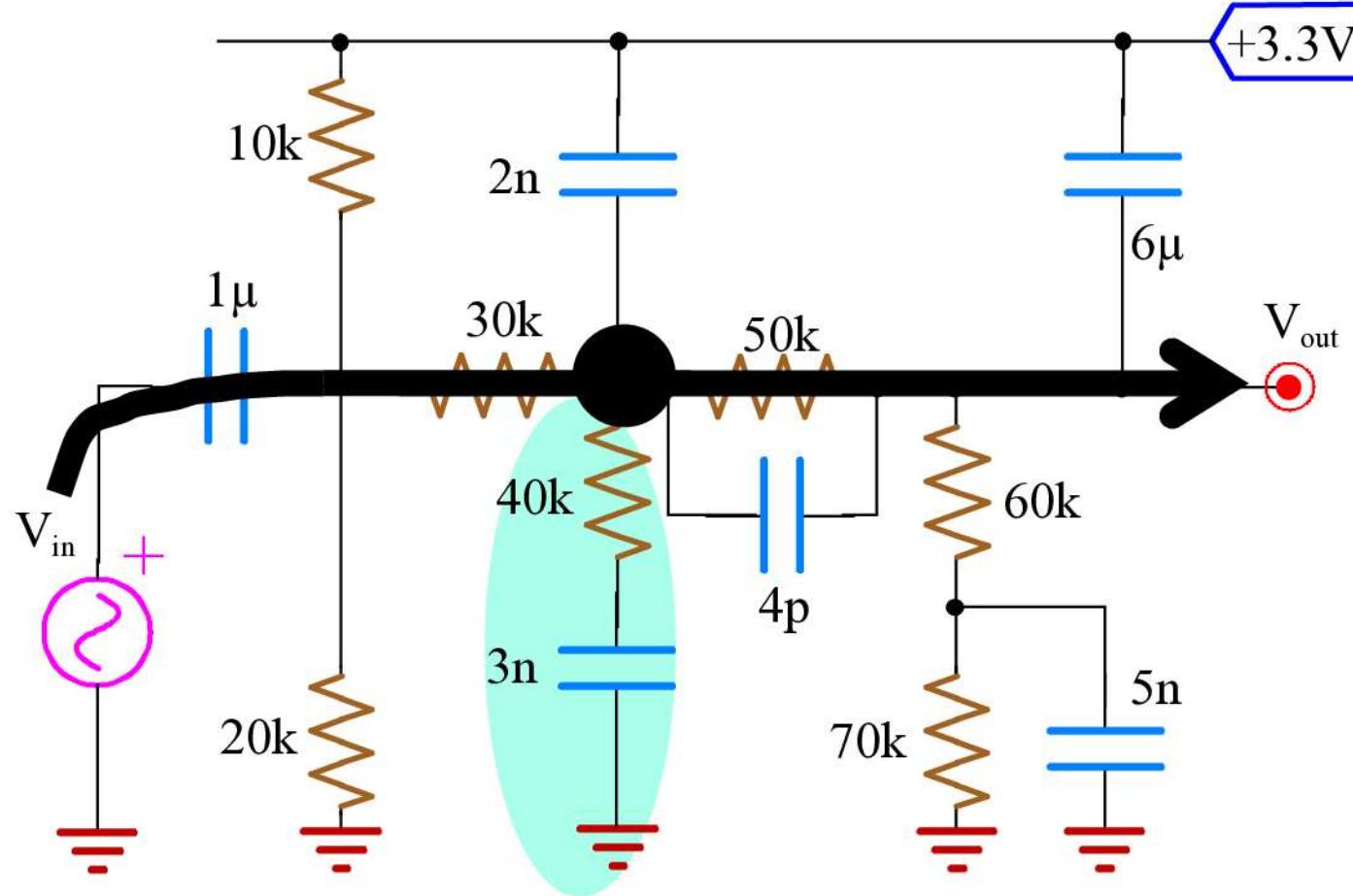An RC-series hanging at a node along the signal path: a finite zero




$$f_{\text{zero}} = \frac{1}{2\pi \cdot R \cdot C}$$



How to compute zeros – most common cases

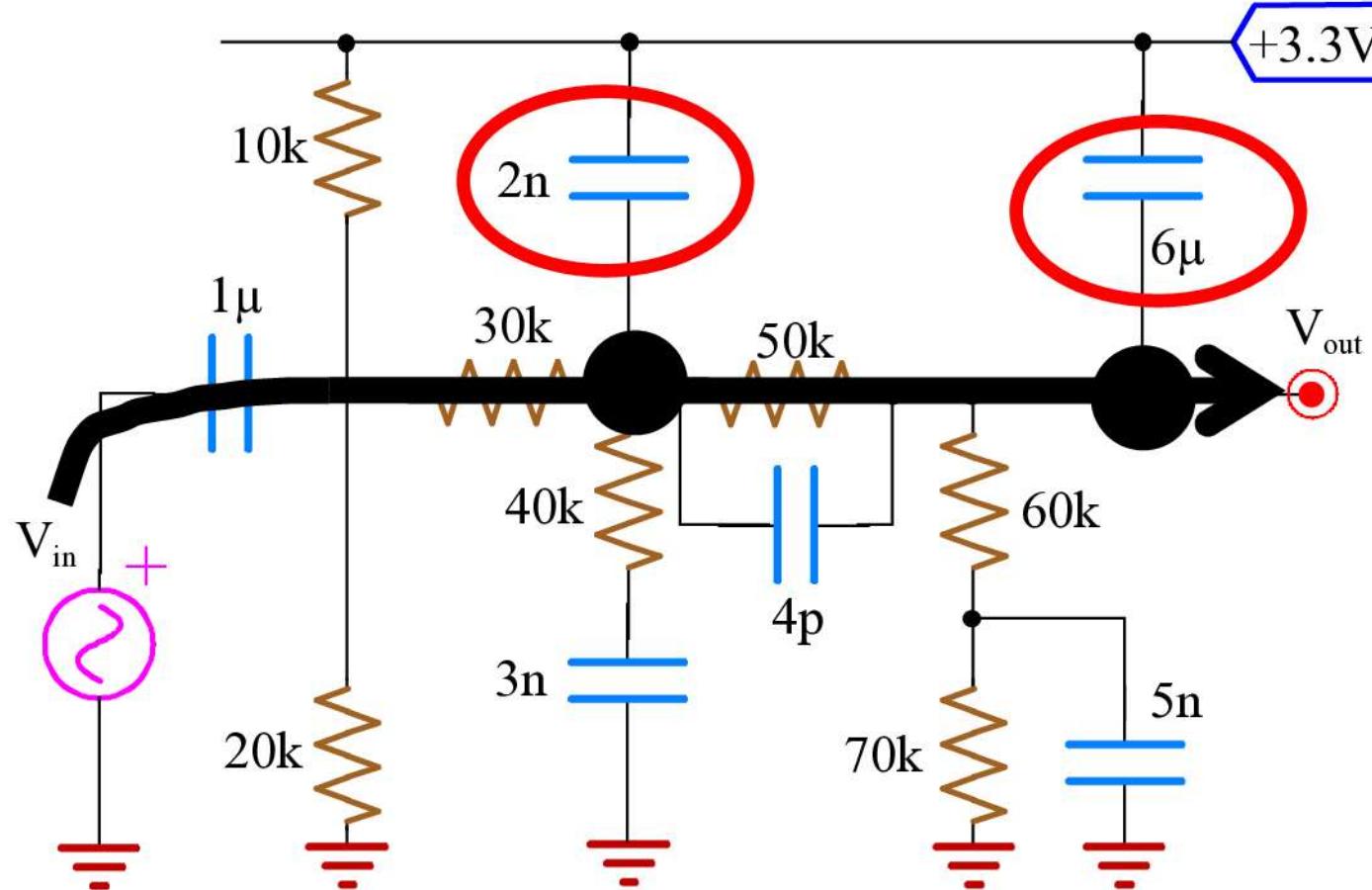
A Capacitor hanging at a node along the signal path: NO ZERO





How to compute zeros – most common cases




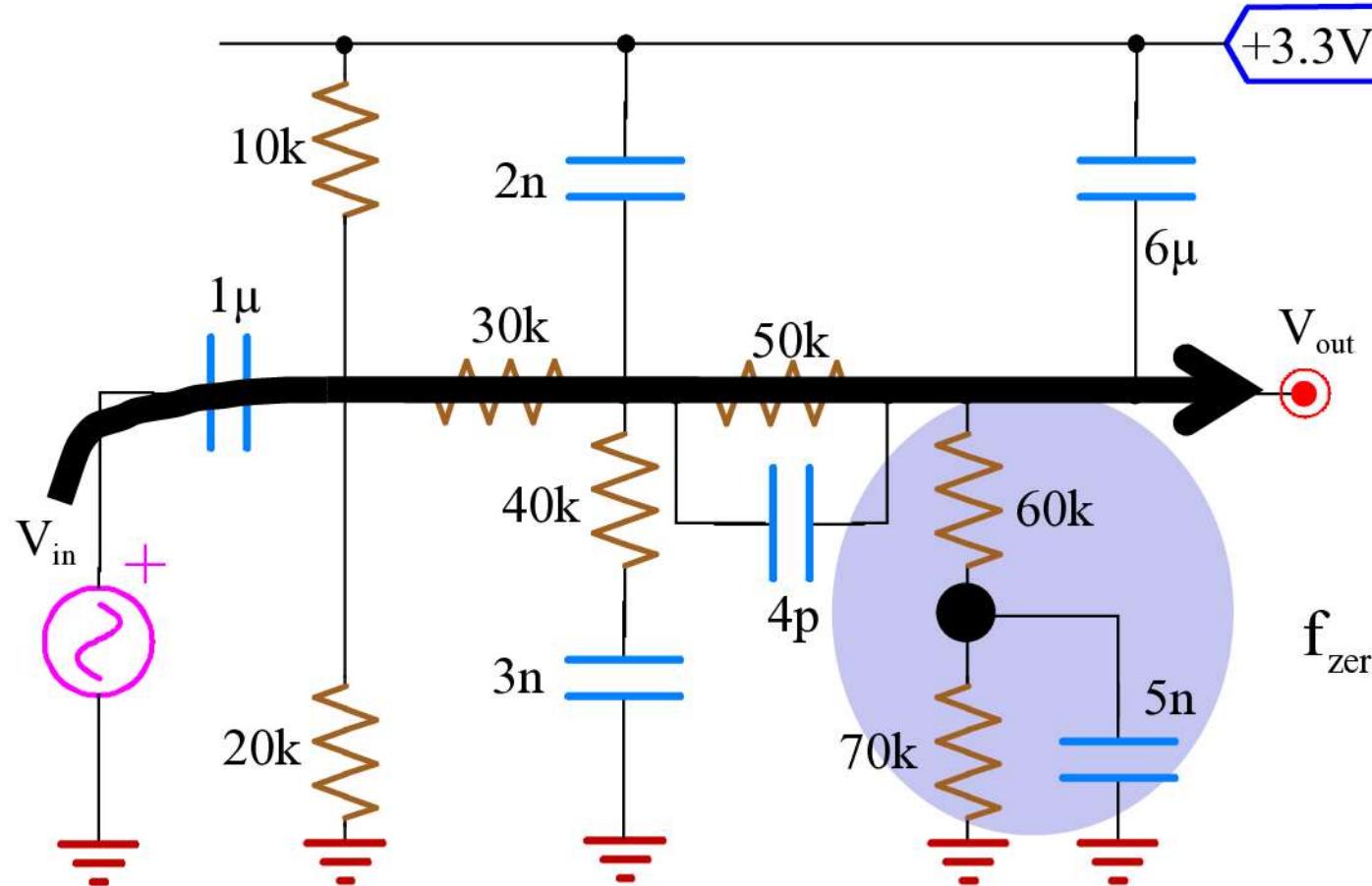
A Capacitor hanging at a node off the signal path: a finite zero



$$f_{\text{zero}} = \frac{1}{2\pi \cdot (60k / 70k) \cdot C}$$



How to compute zeros

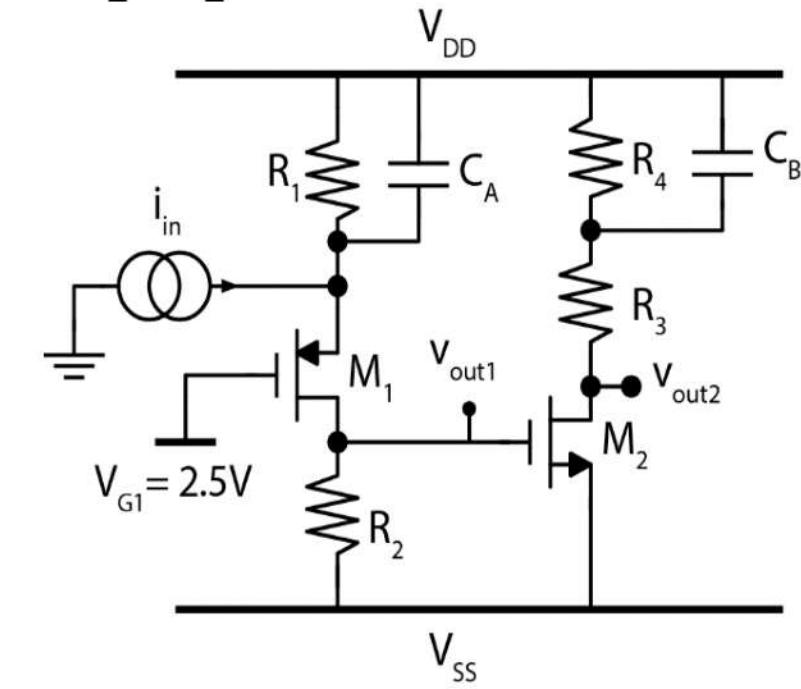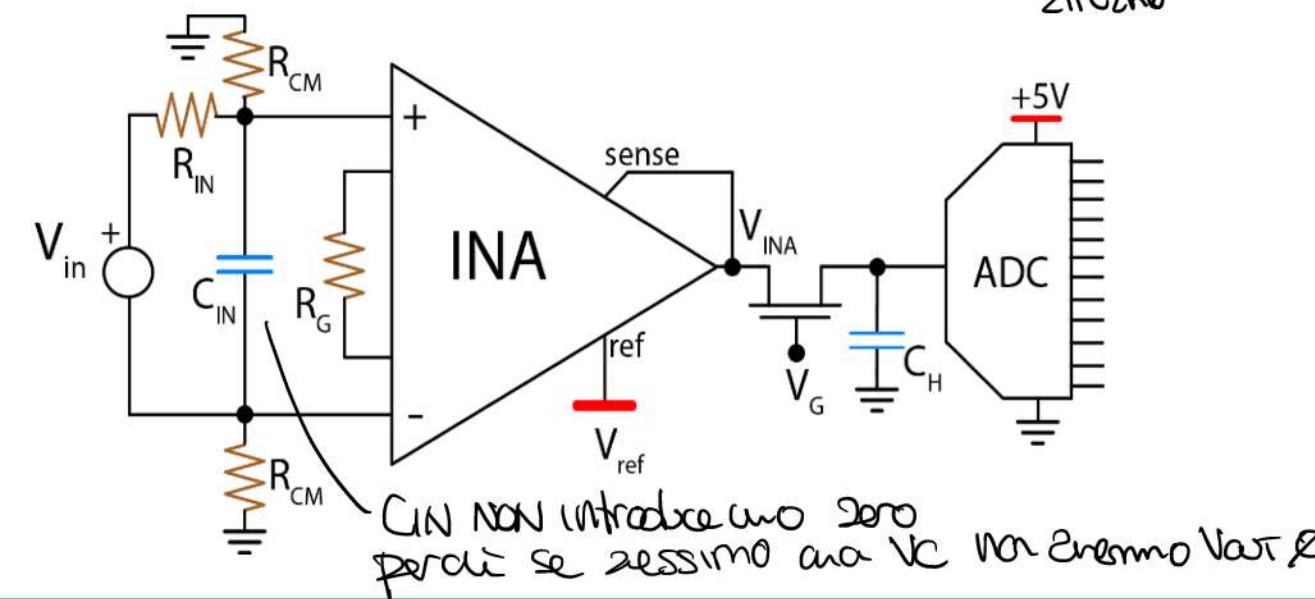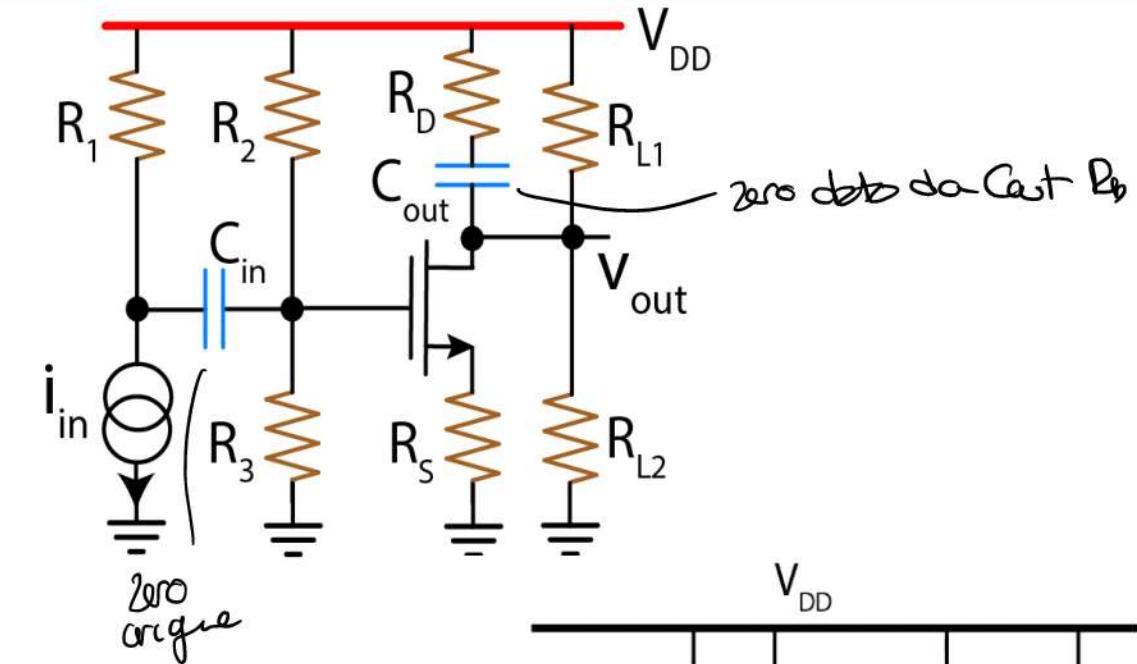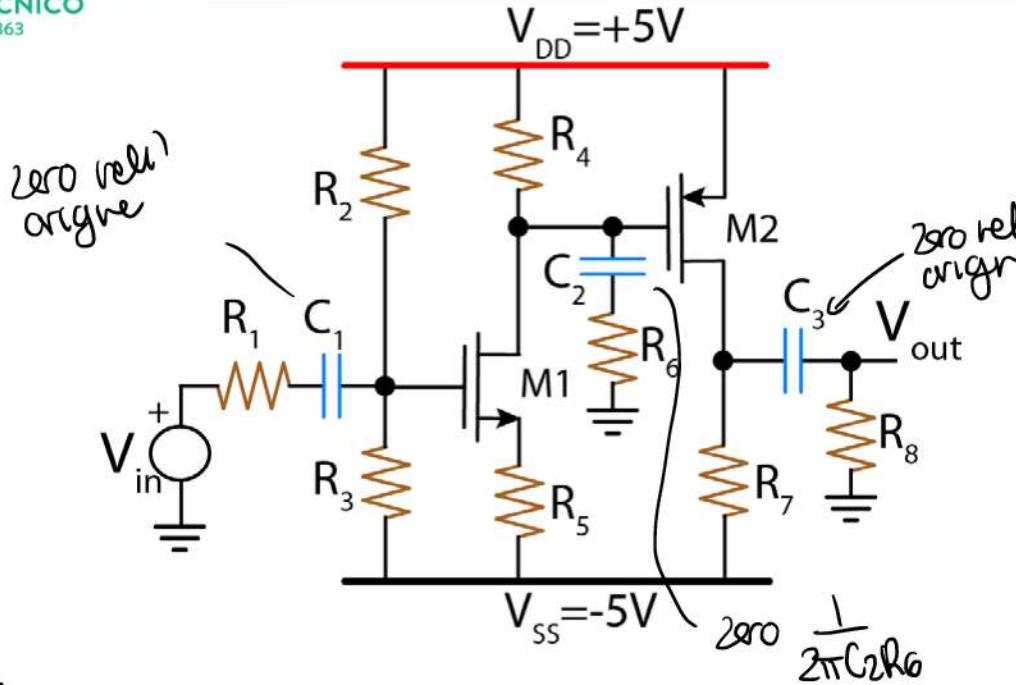




Total number of poles and zeros

CAPACITÀ
(INTERAGENTI)

In conclusion, 4 zeros and 6 poles ?

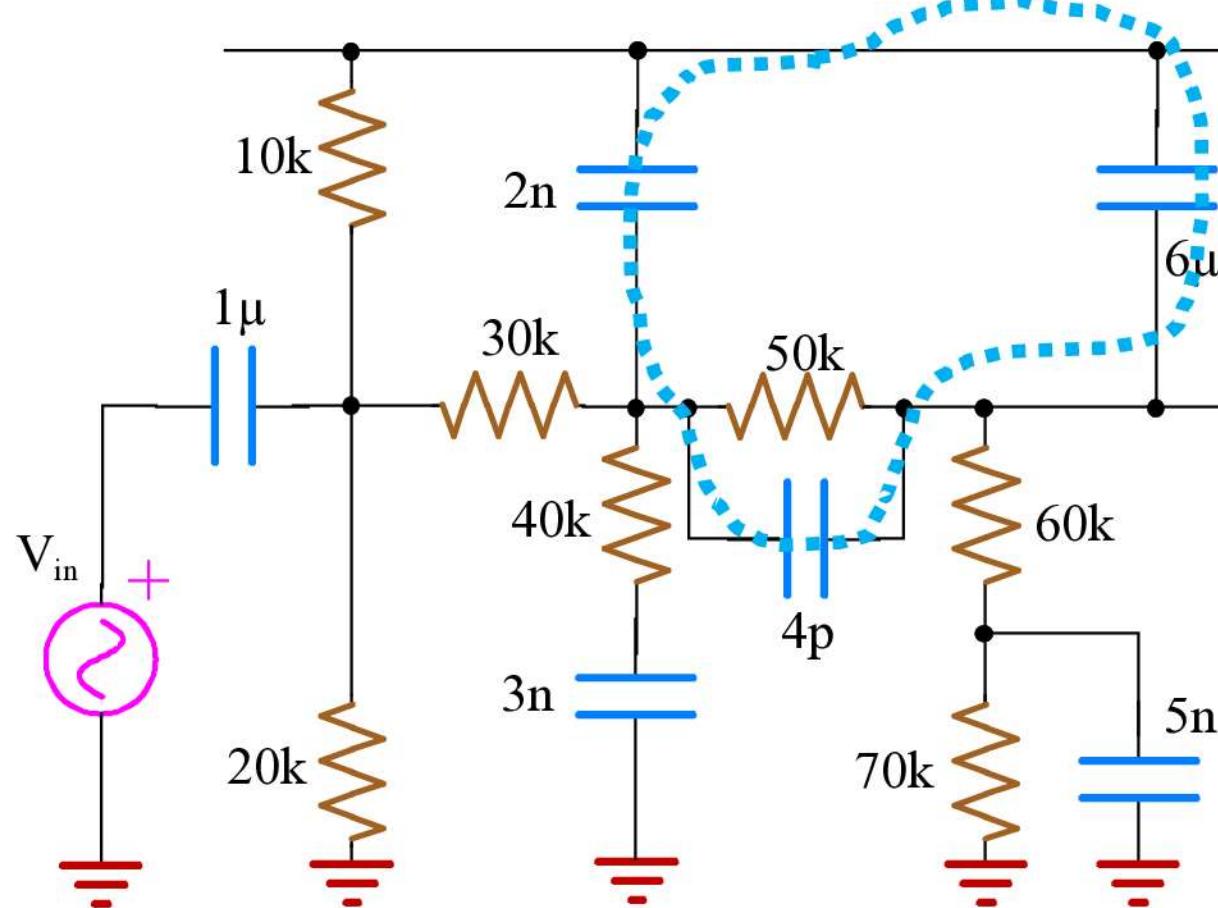Instead no... just 5 poles, because of close «dependency» of some !



Se mettiamo una
ceduta di tensione
ai capi di 2 condensatori
allora questi impagano
un 2 dep zere sul
 V_{out} tranne e
quindi sono interagenti.




Resistors

POLITECNICO
MILANO 1863

Values:

$0.1\Omega \div 4.7M\Omega$

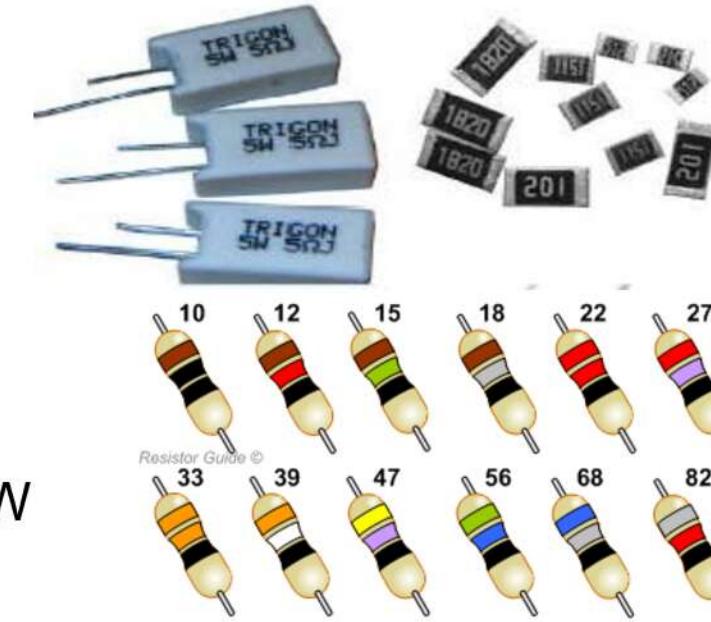


Tolerances:

$10\% \div 1\%$

Power ratings:

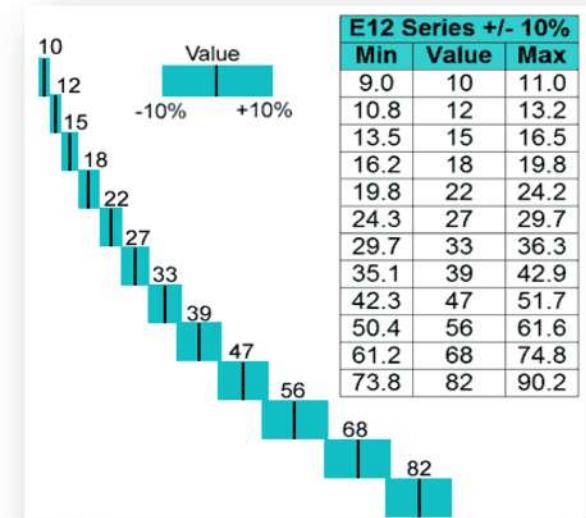$1/8, \frac{1}{4}, \frac{1}{2}, 1, 2, 5, 10W$



	Colour coding									
anello	-	1	2	3	4	5	6	7	8	9
1°	-	1	2	3	4	5	6	7	8	9
2°	0	1	2	3	4	5	6	7	8	9
3°	-	0	00	000	0000	00000	000000	0000000	00000000	000000000
4°										

Preferred values:

10%: 10 12 15 18 22 27 33 39 47 56 68 82

5% e 2%: 11 13 16 20 24 30 36 43 51 62 75 91


1%: 100 102 105 107 110 113 115 118 ...




Resistors

POLITECNICO
MILANO 1863



Technology: wire

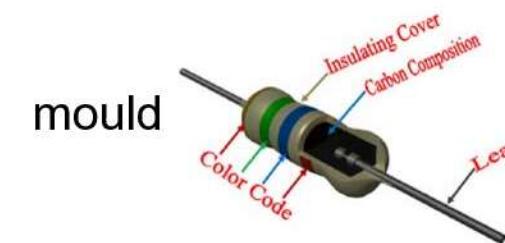

metal layer

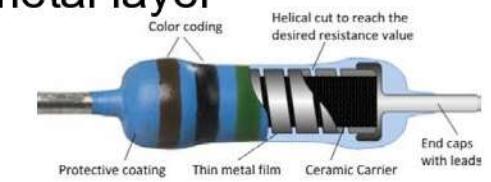

Package: through-hole

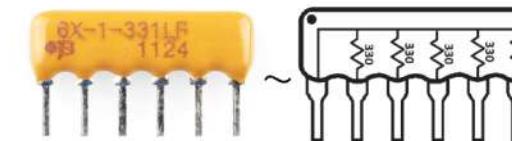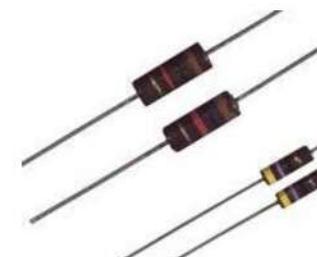


SMD, Surface Mounting Device




Variable: potentiometer




trimmer

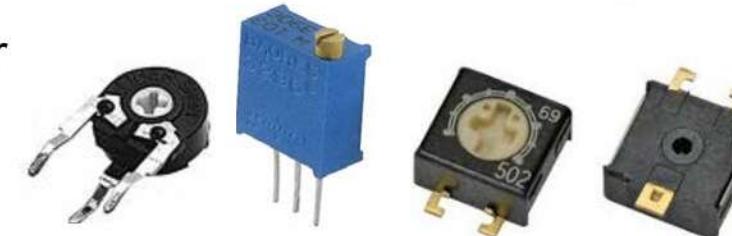

Sensors: photoR

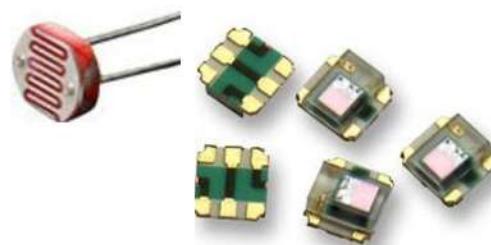

thermoR

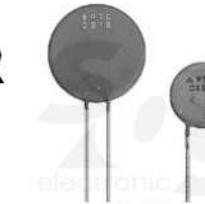

...



Capacitors



Values: $1\text{pF} \div 1'000\mu\text{F}$

Asian coding:

pF

“10₄”=100'000pF=100nF

American coding:

pF starts with figure; μF with “.”

“1.8”=1.8pF “0.0012”=1.2nF

European coding:

pF starts with “.”; nF with “n”; μF with “u”

“1p5”=1.5pF “n15”=0.15nF “u1”=0.1 μF

Tolerance: 20% \div 5%

“M” 20%

“K” 10%

“J” 5%

Voltage ratings: 5V \div 400V

“104M100” = 100nF 20% 100V_{max}



Capacitors

Technology: ceramic




electrolytic




tantalum



Package: through-hole

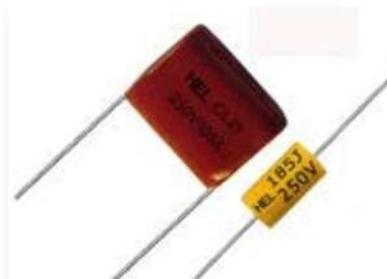

SMD

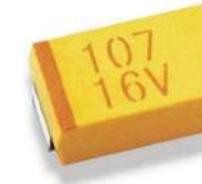

Variable: open air



mica



SMD



varicap



Sensors: weight



humidity




touch

...



Inductors

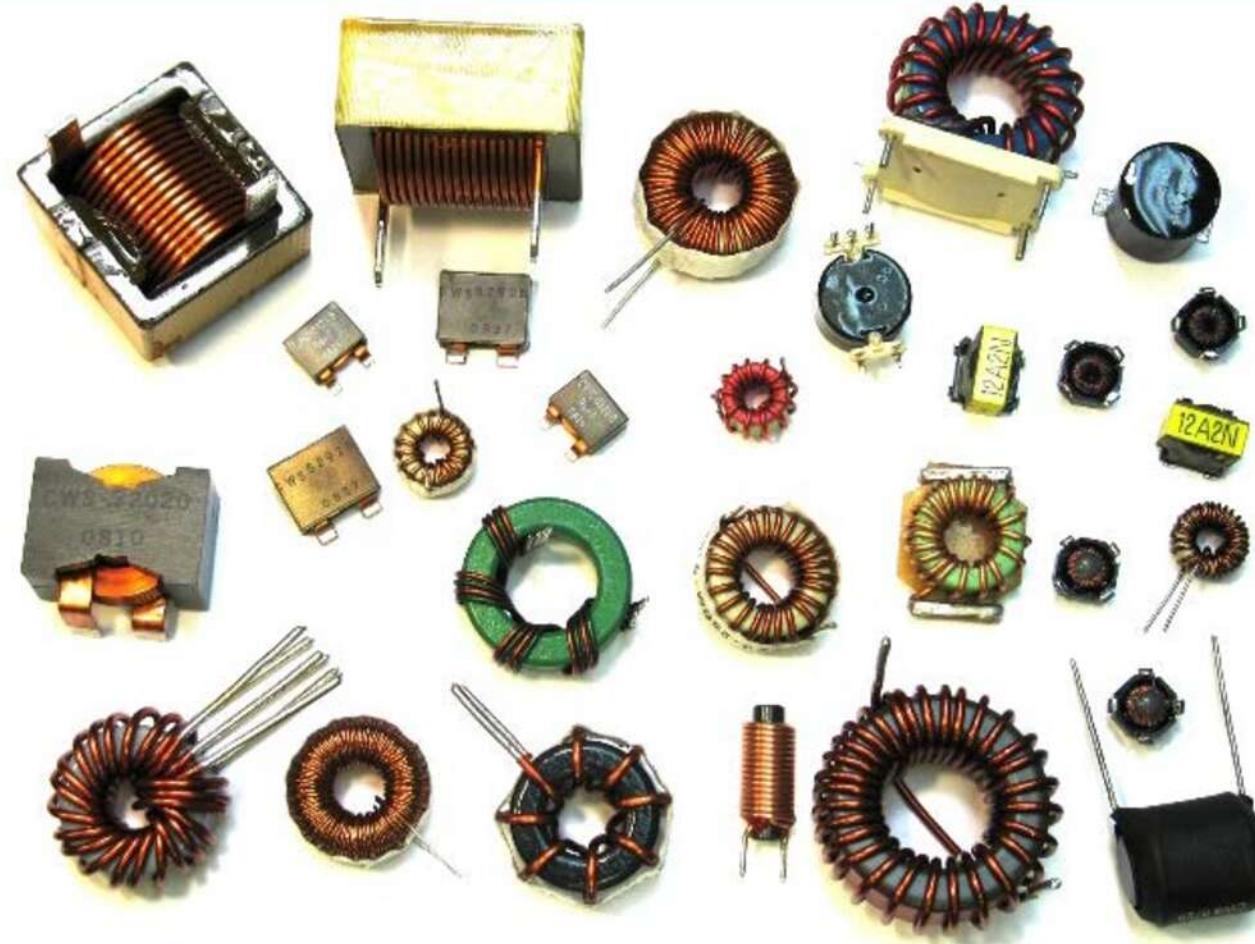

Values: $1\text{nH} \div 100\text{mH}$

Tolerances: $20\% \div 5\%$

Current ratings: $1\text{mA} \div 1\text{A}$



Inductors

POLITECNICO
MILANO 1863

Technology:

coil



transformer



Package:

through-hole



SMD



Variable:



Sensors:

proxi



magnetic fields

...