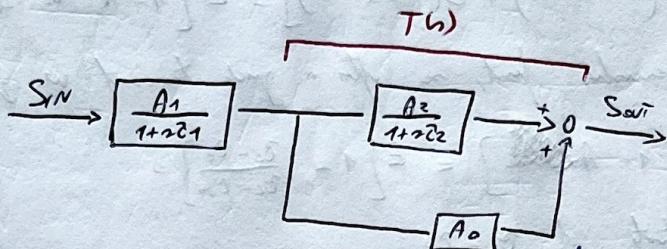


## In-Band Zero-Pole Doublets

In-band zero-pole doublets appear any time we need for example to drive a large load capacitance with a nulling-compensated OTA stage, or when we use a FEED-FORWARDS compensation technique:



$$T(s) = \frac{A_2}{1 + s\bar{C}_2} + A_0 = \frac{1 + \frac{s(A_0\bar{C}_2)}{(A_2 + A_0)}}{1 + s\bar{C}_2} \quad (A_2 + A_0)$$

↳ In-pass blocks with broad band and low gain (BWP trade-off)

so we get a zero  $\bar{C}_2 = \frac{A_0}{A_2 + A_0} \bar{C}_2 < \bar{C}_2$  ( $\Rightarrow f_2 > f_1$ ).

These doublets increase Q\_m but worsen the transient response of the amplifiers.  
Let's consider

$$A(s) = \frac{A_0 (1 + s\bar{C}_2)}{(1 + s\bar{C}_0)(1 + s\bar{C}_p)} \quad (\text{T.F. of a nulling-compensated OTA})$$

and  $\bar{C}_p < \bar{C}_2 < \bar{C}_0$ . The closed loop T.F. in a buffer configuration will be

$$H(s) = \frac{(1 + s\bar{C}_2)}{(1 + s\bar{C}_L)(1 + s\bar{C}_M)}$$

Let's consider the response to a step function  $E$


$$V_{AT}(s) = \frac{E}{s} H(s)$$



$$= \frac{E}{s} \frac{1 + s\bar{C}_2}{(1 + s\bar{C}_L)(1 + s\bar{C}_M)}$$


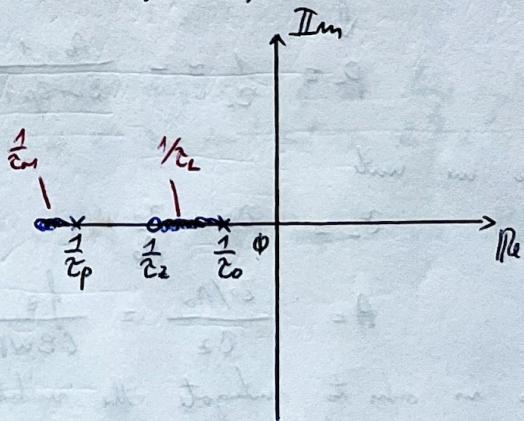
$$= \frac{E}{s} \left[ \frac{A}{1 + s\bar{C}_L} + \frac{B}{1 + s\bar{C}_M} \right]$$



where

$$A = \lim_{s \rightarrow -\frac{1}{\bar{C}_2}} H(s) (1 + s\bar{C}_L) = \frac{1 + \bar{C}_2 \left( -\frac{1}{\bar{C}_L} \right)}{1 + \bar{C}_M \left( -\frac{1}{\bar{C}_L} \right)} = \frac{\bar{C}_L - \bar{C}_2}{\bar{C}_L - \bar{C}_M}$$

$$B = \lim_{s \rightarrow -\frac{1}{\bar{C}_M}} H(s) (1 + s\bar{C}_L) = \frac{1 + \bar{C}_2 \left( -\frac{1}{\bar{C}_M} \right)}{1 + \bar{C}_L \left( -\frac{1}{\bar{C}_M} \right)} = \frac{\bar{C}_M - \bar{C}_2}{\bar{C}_M - \bar{C}_L}$$

44

We get that

$$H(t) = \frac{A}{Z_L} e^{-\frac{t}{Z_L}} + \frac{B}{Z_H} e^{-\frac{t}{Z_H}}$$

so, by integration, we get:

$$\text{var}(t) = E \left[ A \left( 1 - e^{-\frac{t}{Z_L}} \right) + B \left( 1 - e^{-\frac{t}{Z_H}} \right) \right] = E \left[ 1 - Ae^{-\frac{t}{Z_L}} - Be^{-\frac{t}{Z_H}} \right]$$

The first exponent vanishes first, so after a quick transit we get

$$\text{var}(t) \approx E \left[ 1 - Ae^{-\frac{t}{Z_L}} \right] = E \left[ 1 - \frac{Z_L - Z_p}{Z_L - Z_H} \right] =$$

We need an estimate of  $Z_L - Z_p$ :

$$(loop(s)) = -A_0 \frac{1 + r Z_p}{(1 + r Z_o)(1 + r Z_p)}$$

$$-(loop(s)) + 1 = 0$$

↓

$$-A_0 - A_0 Z_p \cdot r = 1 + r Z_o + r Z_p + r^2 Z_o Z_p$$

↓

$$r^2 Z_o Z_p + r(Z_o + Z_p + A_0 Z_p) + A_0 + 1 = 0$$

↓

$$P_L = -\frac{1}{Z_L} \approx -\frac{A_0 + 1}{Z_o + Z_p + A_0 Z_p} = -\frac{1}{Z_p + \frac{Z_o}{A_0}} \quad (\text{big } Z_o \gg Z_p)$$

So we write

$$Z_L = Z_p + \frac{Z_o}{A_0}$$


$$A = \frac{Z_o / A_0}{Z_L} = \frac{f_z}{GBWP}$$

so in order to mitigate the residual gain that has to be coped with the slow time constant, we must shift  $f_z$  to LF, but this must also to share  $Z_L$  even down!

For the case of feed-forward compensation,  $Z_o > Z_p > Z_L$  so the net loss is different and we expect

$$Z_L < Z_p$$

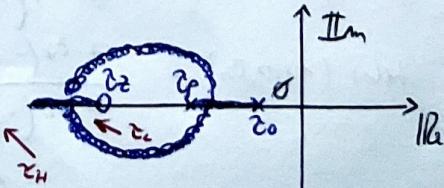so the response has an overshoot that is then removed with the slow time constant  $Z_L$




### SLEW RATE

The slew-rate performance is related to the power available to charge capacitors.

If we consider a large input signal for example  $I_{13}$  at fully nonlinearities the differential signals, thus mostly  $I_{11} - I_{13} = I_{14}$  off and little  $I_{11}$  flows into  $C_c$ . As a result,  $V_{c,s} \downarrow$  and  $I_{15}$  comes

$$\frac{I_s + \Delta I_s}{2I_0}$$

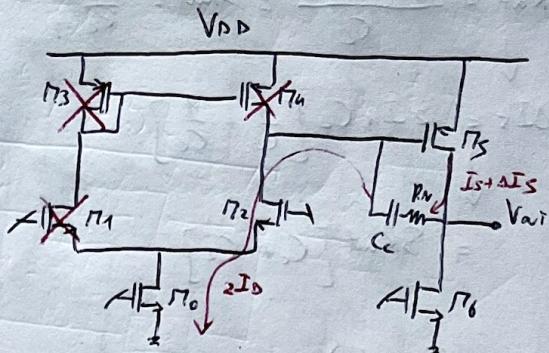

The initial response is a linear ramp with  $SR = \frac{I_0}{C_c}$ . If we come to have the OTA in a buffer configuration, then we recover the expected behavior when

$$\begin{cases} SR = \frac{\Delta V}{2} \\ (\Delta V = V_{(00)} - SR \cdot t_{SLEW}) \\ \downarrow \\ \begin{cases} \Delta V = SR \cdot z \\ t_{SLEW} = \frac{V_{(00)}}{SR} - z \end{cases} \end{cases}$$

$$\Rightarrow V_{out}(t) = \begin{cases} SR \cdot t & (t \leq t_{SLEW}) \\ V_{(00)} - \Delta V \cdot e^{-\frac{(t-t_{SLEW})}{z}} & (t \geq t_{SLEW}) \end{cases}$$

This discussion is valid under the assumption that the ring bias of the large input signal is  $< \frac{z_L}{G(b)} = \frac{1}{GBWP(OTA)}$  of the OTA, so that  $V_{out}$  doesn't reach to the large input at first.

If we consider an harmonic signal instead, whose amplitude is the maximum one allowed by the output dynamics, then

$$2\pi f_{max} = \frac{dV_{out}}{dt}_{max} \leq SR$$

$$f_{max} \leq \frac{SR}{2\pi t_{max}} \stackrel{D}{=} \underline{\text{POWER BANDWIDTH}}$$

Finally, we can point out that

$$SR = \frac{I_0}{C_c} = \frac{V_{out,1} \cdot g_m,1}{C_c} = 2\pi V_{out,1} \cdot GBWP$$

[one GBWP is not, we need to mean  $V_{out,1}$  in order to mind SR, but the  $\leftrightarrow$  symbol  $Ein^2$ ]

### EXTERNAL SR

Let's consider now a load capacitance. We must distinguish now two cases

① Large  $V_p$  (positive)


$I_{11} - I_{13} - I_{14}$  are off and  $2I_1$  flows into  $C_c$ . Under the assumption that  $V_A$  reaches a steady state, the ~~ring~~ ramp rate across  $C_c$  can't be equal to the

(46) one across C, being it equal to  $S_{\text{crit}} = \frac{2I_1}{C_C}$  required by the first stage, so it must be  $\frac{I_1}{C_C}$

$$SR_{out}^+ = \frac{\Delta Is - 2I_1}{C_L} = S_{load} = \frac{2I_1}{C_C}$$

$$\Delta I_s = 2 I_1 C_L \left[ \frac{1}{C_L} + \frac{1}{C_C} \right]$$

$$= S \int_{\text{int}} [C_c + C_e]$$

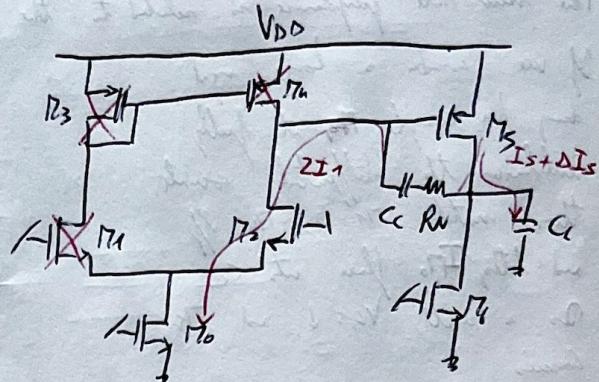

② Vp large (negative)

$M_2$  off, 2I<sub>1</sub> flux into  $M_1 - M_3 - M_4$ ,  $M_5$ 's unit decreases

$$S_{Rout} = \frac{\Delta Is - 2I_1}{C_L} = S_{Rint} = \frac{2I_1}{C_L} \quad (\text{if } S_{Rint} \text{ is now unity then the output load})$$

$$\Delta T S = 2 J_1 C_L \left[ \frac{1}{C_L} + \frac{1}{C_C} \right] = S_{\text{limit}}(C_L + C_C)$$


But if  $\Delta I_s > I_s$ , the  $I_s$  turns off and  $I_b$  has to bias both  $C_e$  and  $C_b$ . In this case, at steady state the avg rate across  $C_e$  matches the one across  $C_b$ , so

$$\frac{I_6 - I_4}{C} = \frac{I_h}{C} = S_{Ran}$$

$$\begin{cases} I_u = I_b \cdot \frac{C_c}{C_u + C_c} & \leftarrow 2I \\ S_{kav} = \frac{I_b}{C_u + C_c} \end{cases}$$

In the end
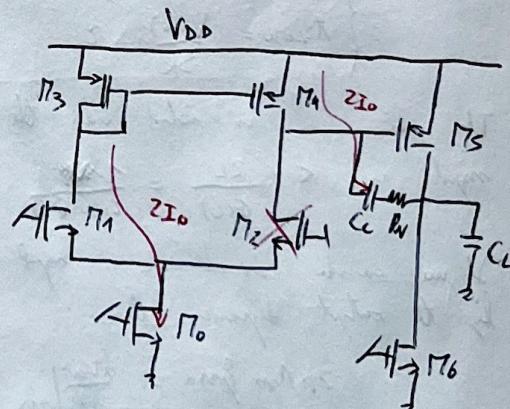
$$SR_{\text{var}} = \min \left\{ SR_{\text{int}}, \frac{I_6}{C_L + C_C} \right\}$$



Have to love that Shavit is the living one and both presidents?


→ instead I6

→ use a class A-B, raise  $T_b$  until only when needed!

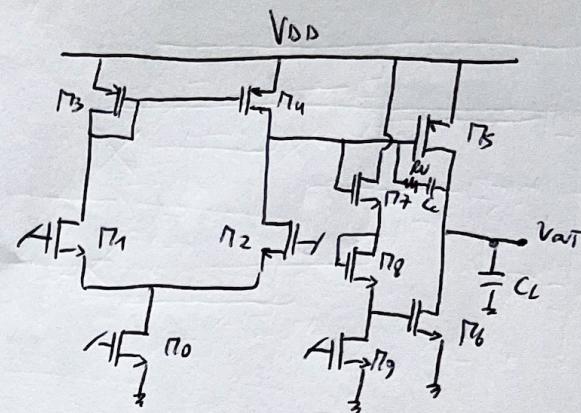
# LASS AB Source For Slew Rate

$M_2 - M_3$  act as voltage shifter to properly set  $M_6$ 's bias. We mix them in order to provide a shift of  $0.8V + 0.8V$ .

In this way  $M_6$  reacts in order to reduce its count only when needed, so we do not exceed static power consumption!



NOTE: the gain changes

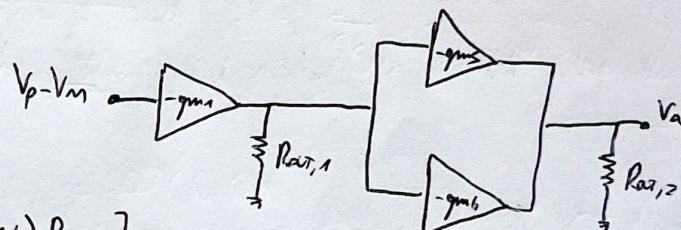

$$G_d = \frac{[g_{m1} \cdot R_{out,1}] \cdot [(g_{m5} + g_{m6}) R_{out,2}]}{G_2}$$

A possible alternative is the AC coupling:

the capacitance  $C_{ac}$  makes it possible to properly bias the  $M_6$  transistor and also to let it come into action when needed.

