



POLITECNICO
MILANO 1863



ELECTRONIC SYSTEMS

2021-22 academic year


prof. Franco ZAPPA



- Principle of current feedback
- Comparisons with voltage feedback
- Modeling
- Internal schematics
- Further improvements



Voltage Mode (VOA)


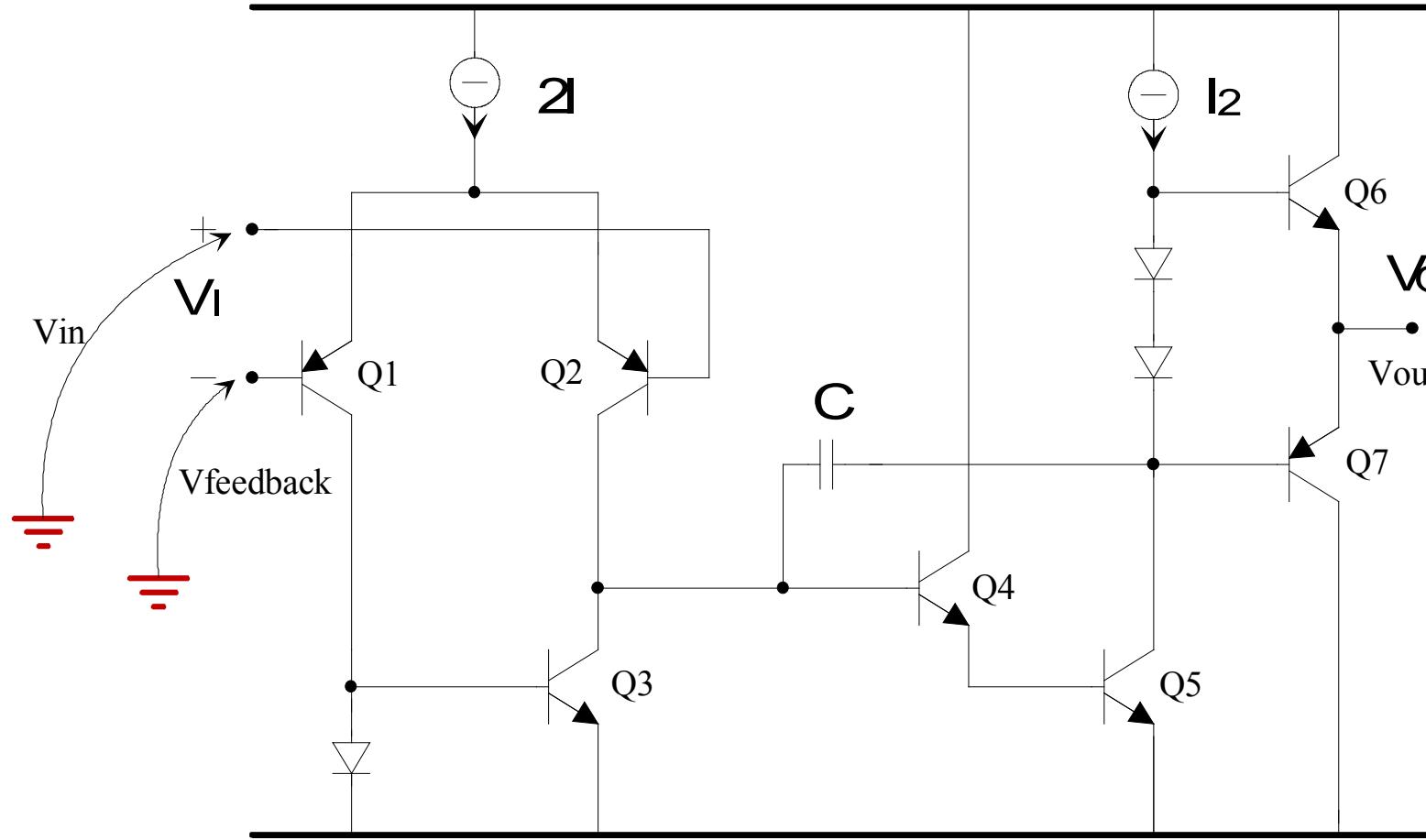


Requirements:

- voltage-driven inputs → high impedance inputs
- voltage output → low-impedance output



Voltage Mode (VOA)

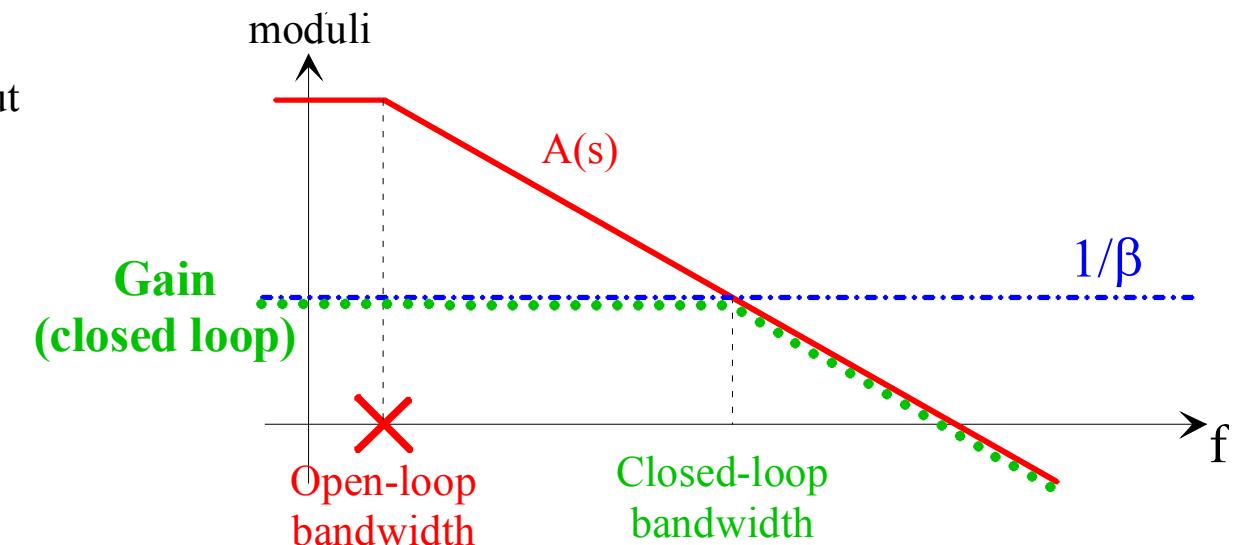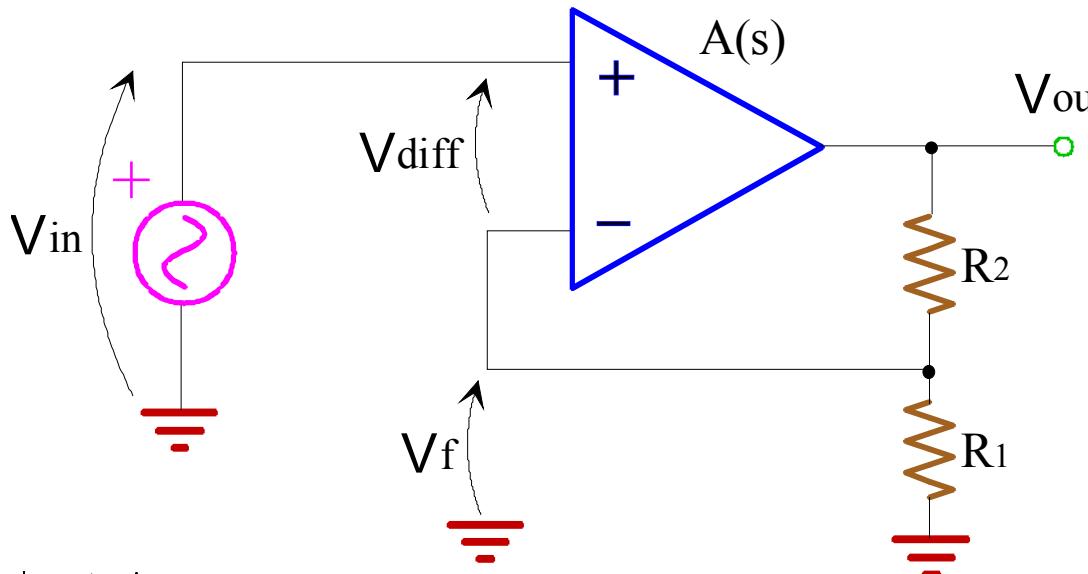

Con il VOA se voglio aumentare il guadagno la banda cala perché il guadagno è strettamente dipendente da $1/\beta$. Se aumenta il guadagno di 10, allora R^* scende di un valore 10.

Performances:

-20dB/dec slope

constant GBWP

limited SR

(hence trade-off between gain and bandwidth)

(tens of V/ μ s)


strict relationships among f_0 I_{tail} C_{comp} SR (again trade-off)



Current Feedback (CFA)

Qui in uscita no un errore
di corrente

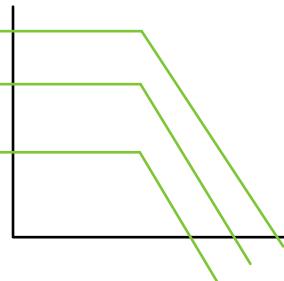Se cambio il guadagno
Cambiendo solo R_A (R_S) allora
posso avere **Requirements:**
la struttura di




non devo cambiare
 R_F perché il polo dipende
da lei.

- one high-impedance input
- one low-impedance input
- voltage output

$$G_c = 1 + \frac{R_F}{R_S}$$

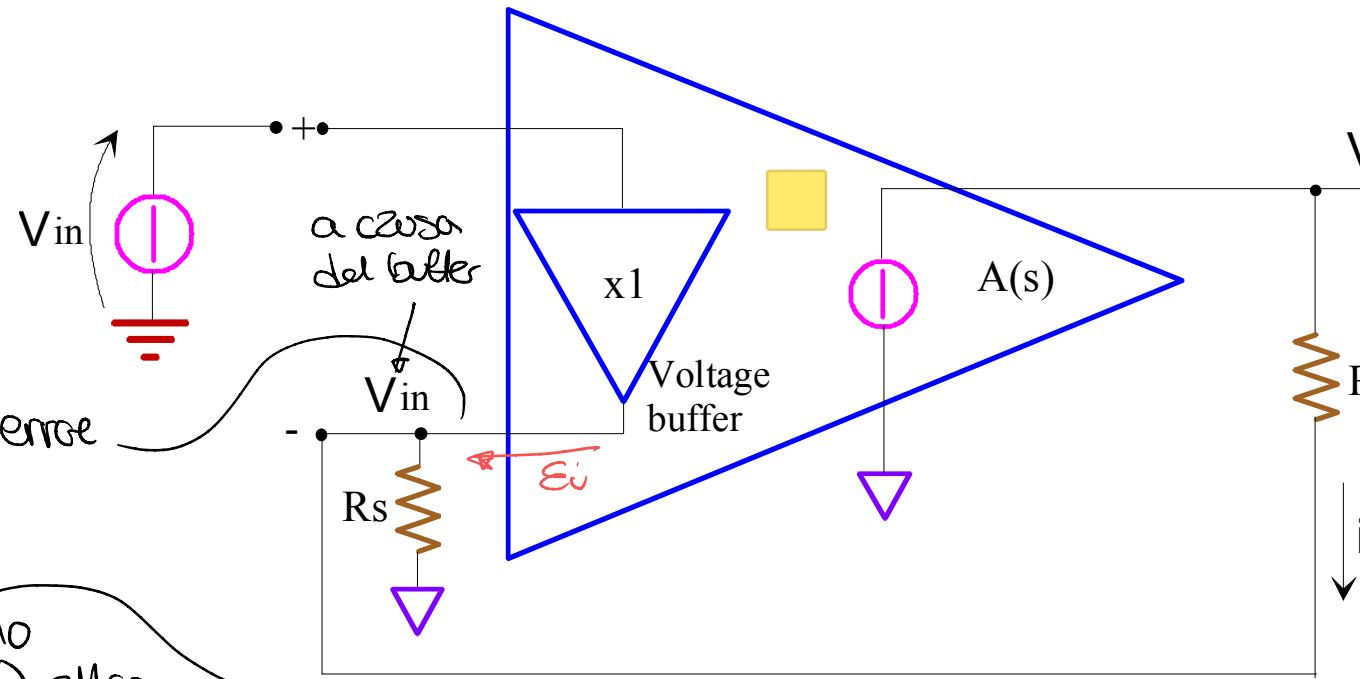It looks identical to VOA, but completely different feedback action





(hence voltage-driven input)

(hence input-current, i.e. Acting as an output)

(proportional to the input current)

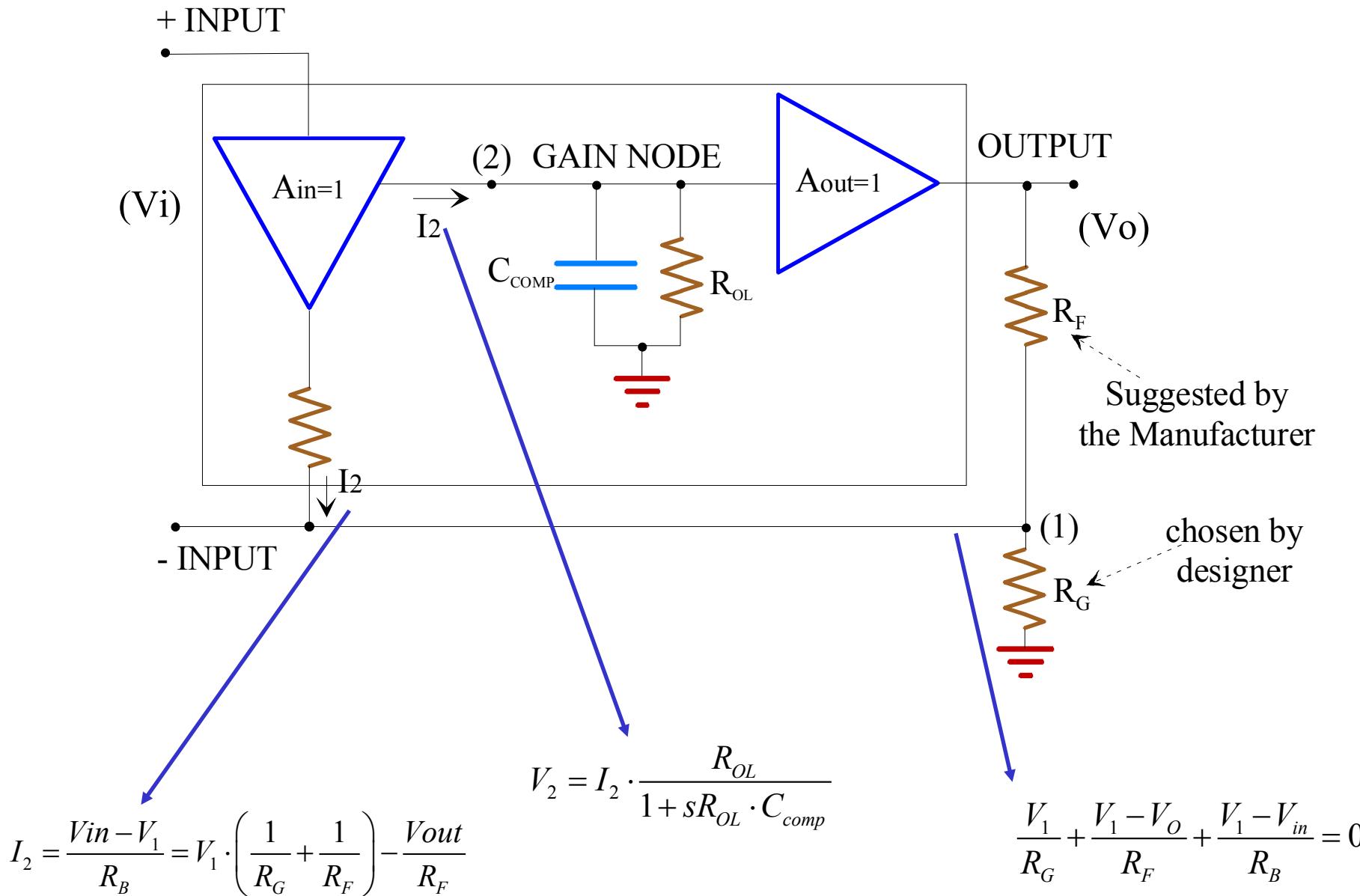ho da $A(s)$
tentare di portare
 V_o ad una tensione
moto etto
questo fa sì che
si dà un
comune in
Contrapposizione
a $E_i = V_{in}/R_s$
e farà sì che
si annulli.
Se $E_i = \emptyset$ noi
sappiamo che
 $A(s) = R_o E_i$
e quindi va
al valore da mi
fa sì che $E_i = i$ in
modo che si annullino.



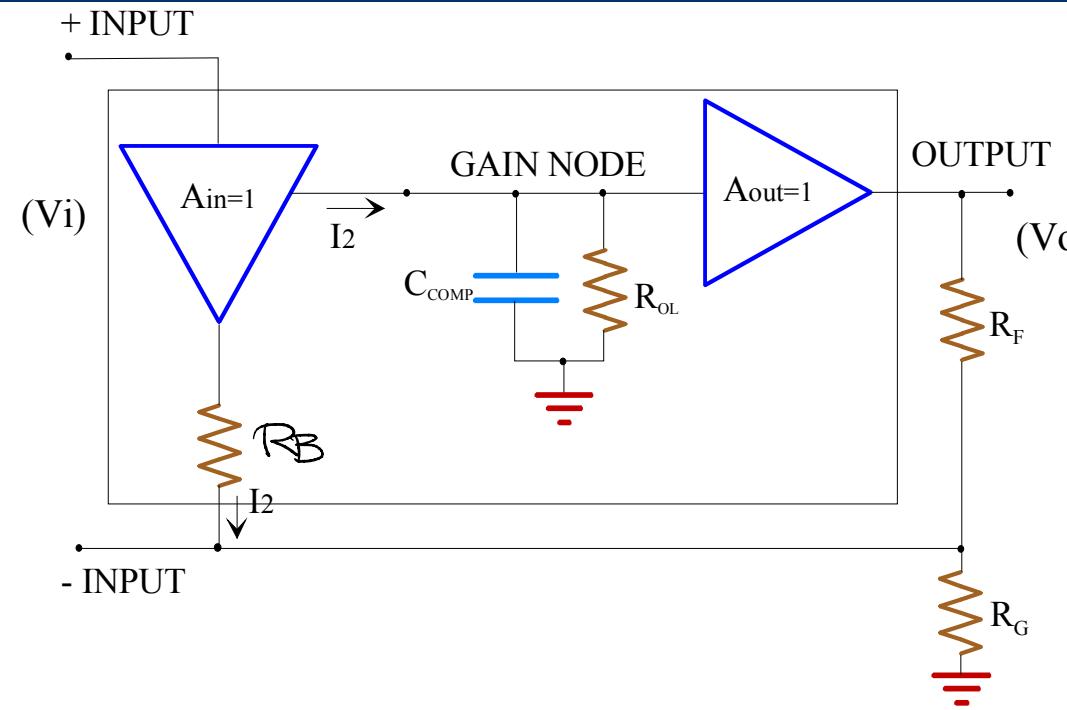

Closed-loop Gain:

È un casinò di formula
dobbiamo fare delle semplificazioni
 $R_G \gg R_B$

$$\frac{V_{out}}{V_{in}} = \frac{1 + \frac{R_F}{R_G}}{\left(1 + \frac{R_F + \left(1 + \frac{R_F}{R_G} \right) \cdot R_B}{R_{OL} \cdot A_{out}} \right) \cdot \left[1 + s \frac{R_F + \left(1 + \frac{R_F}{R_G} \right) \cdot R_B}{R_F + \left(1 + \frac{R_F}{R_G} \right) \cdot R_B} \cdot C_{comp} \right] \cdot A_{out} + \frac{R_F + \left(1 + \frac{R_F}{R_G} \right) \cdot R_B}{R_{OL}}]}$$



Bandwidth:

$$f_{pole} \cong \frac{A_{out}}{2\pi \left[R_F + \left(1 + \frac{R_F}{R_G} \right) \cdot R_B \right] \cdot C_{comp}}$$

Per $R_G \gg R_B$,
allora si può
approssimare con



For low gain ($R_B \ll \frac{R_F \cdot R_G}{R_F + R_G} = R_F \parallel R_G$) we get $f_{pole} \cong \frac{1}{2\pi \cdot R_F \cdot C_{comp}}$

Bandwidth depends only on R_F , not on R_G , hence NOT ON GAIN!

Instead for high gain (> 50)

we get $GBWP = \frac{A_{out}}{2\pi R_B \cdot C_{comp}}$


As for VOA, again trade-off Gain & Bandwidth (i.e. constant GBWP)



CFA: bandwidth

Let's study the feedback
in a smarted way...
...same result at the end!

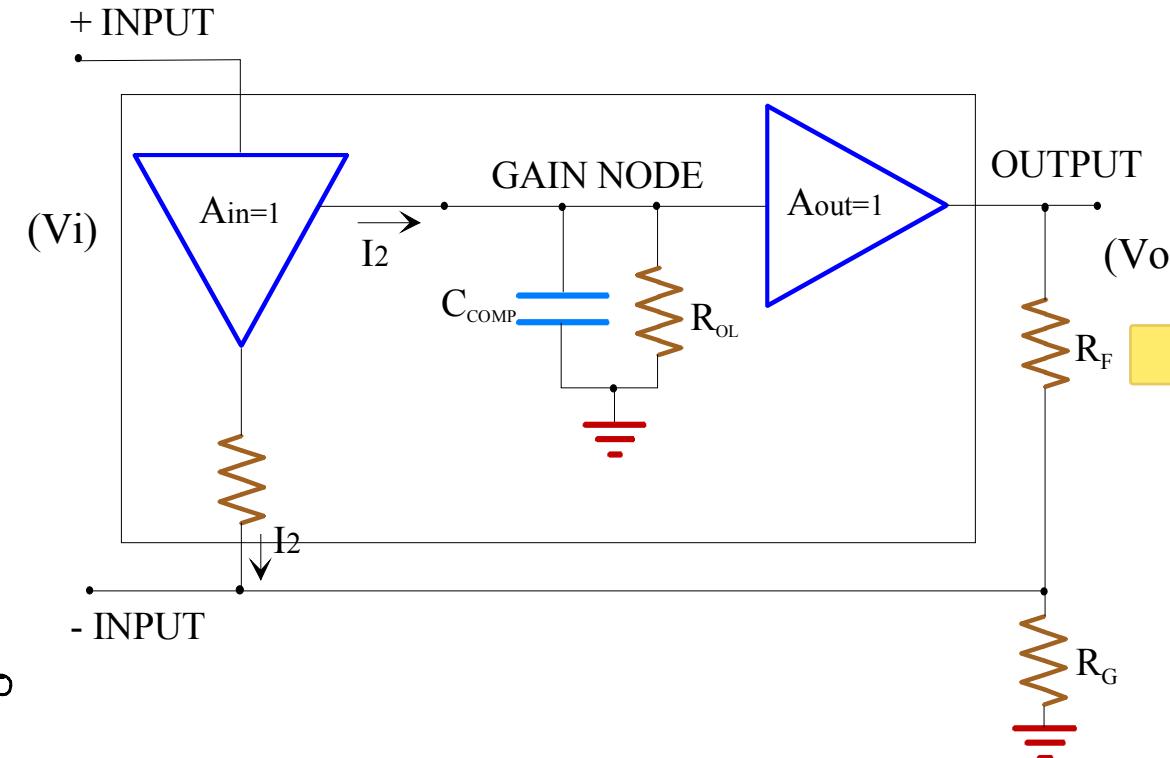Il polo a circuito chiuso è
quello a circuito aperto che sarebbe
quello con lo (RaComp) moltiplicato
per (1-Gloop)



With open-loop: $pole_{openloop} \approx \frac{-1}{C_{comp} \cdot R_{OL}}$

$$G_{loop} \approx -R_{OL} \cdot A_{out} \cdot \frac{1}{R_B + R_F} \approx -\frac{R_{OL}}{R_F}$$

... hence, when loop is closed:


$$pole_{closedloop} = pole_{openloop} \cdot (1 - G_{loop}) \approx \frac{-1}{C_{comp} \cdot R_{OL}} \cdot \frac{R_{OL}}{R_F} = \frac{-1}{C_{comp} \cdot R_F}$$




CFA: bandwidth

In conclusion, at low gains...

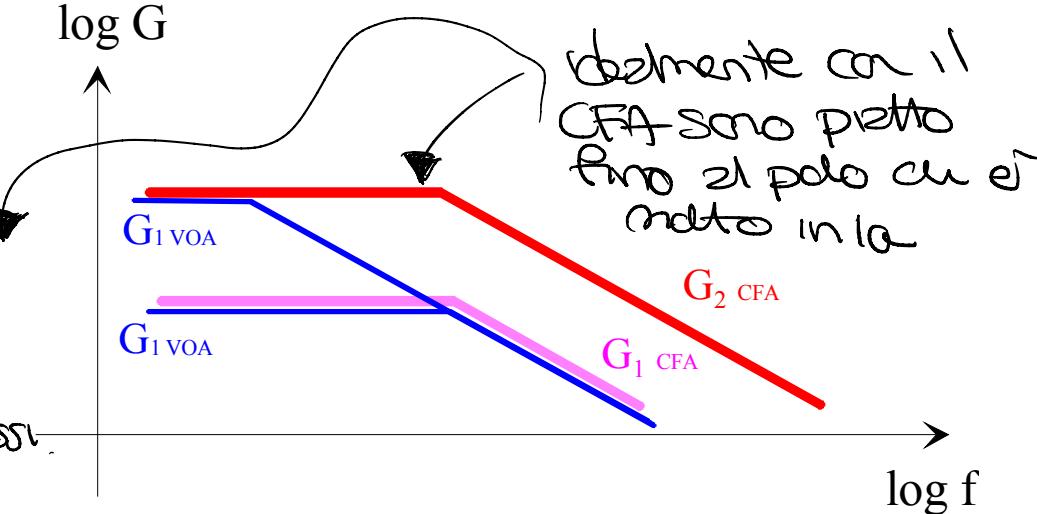Questa e'
vero solo per
guadagni
abbastanza bassi.



Instead at high gains...

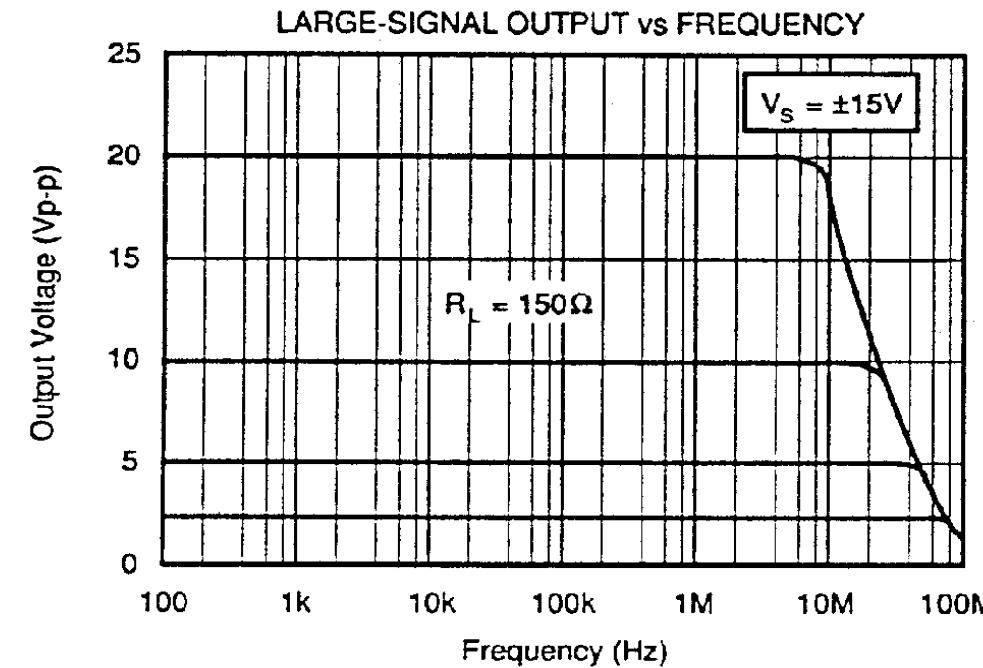





CFA: a real architecture

POLITECNICO
MILANO 1863

Non possono usare un buffer così

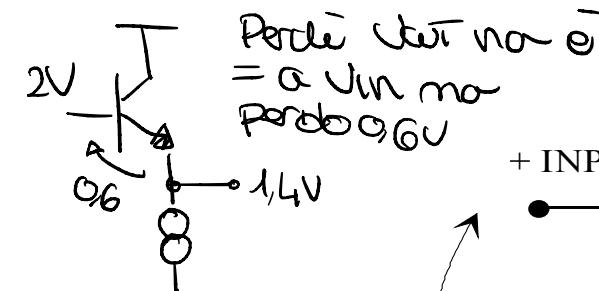


Potremo usare
un'altra struttura tipo

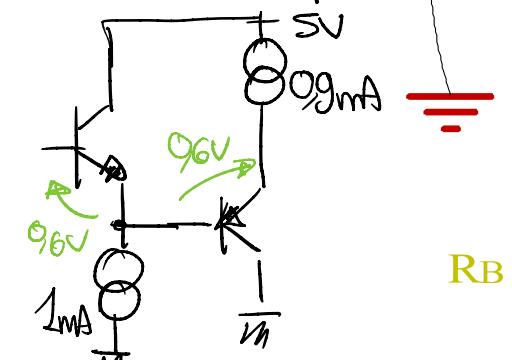


ho $V_{out} = V_{in}$, il problema
è che la corrente massima

sull'alt è 0,9mA
2 tratti i PNP si
spegne

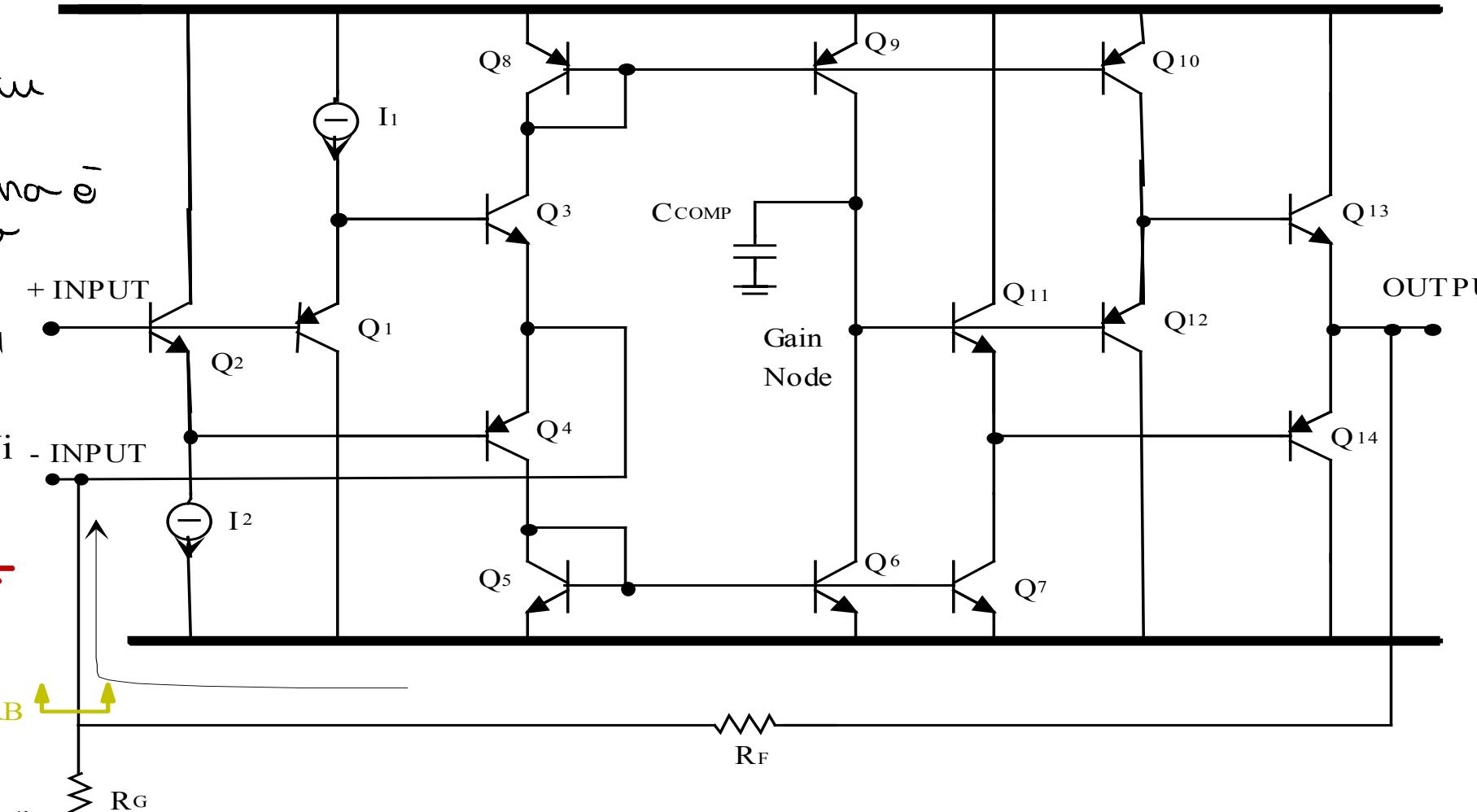
Complementary npn+npn darlington configurations, hence better SR...
but problems of matching, hence higher offset voltage



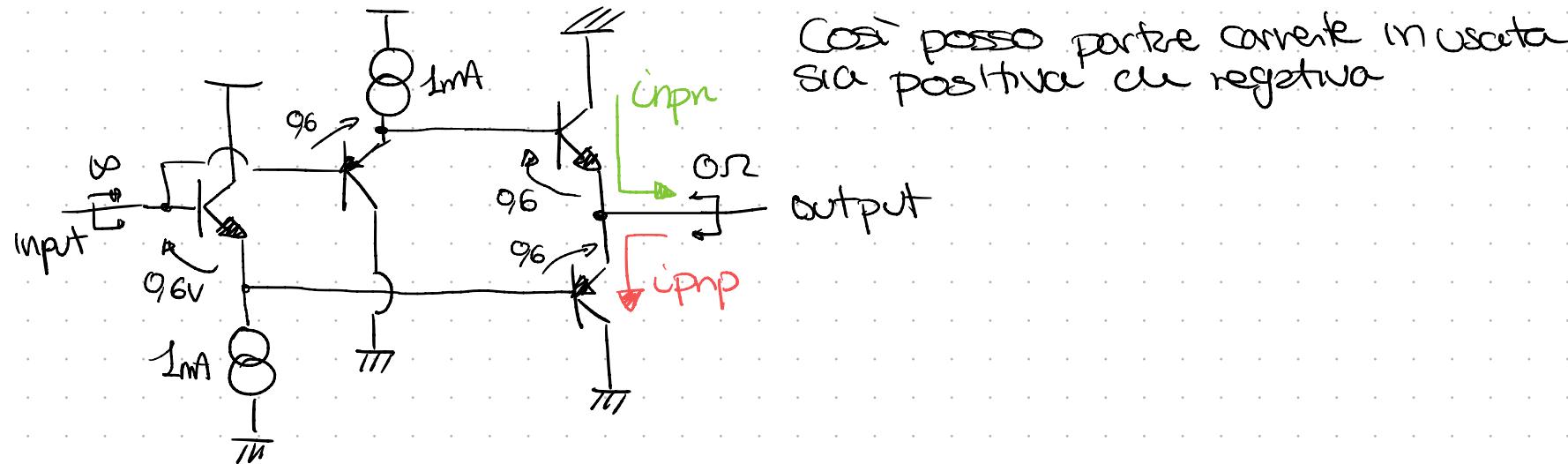Duplichiamo il circuito di prima per avere un buon buffer




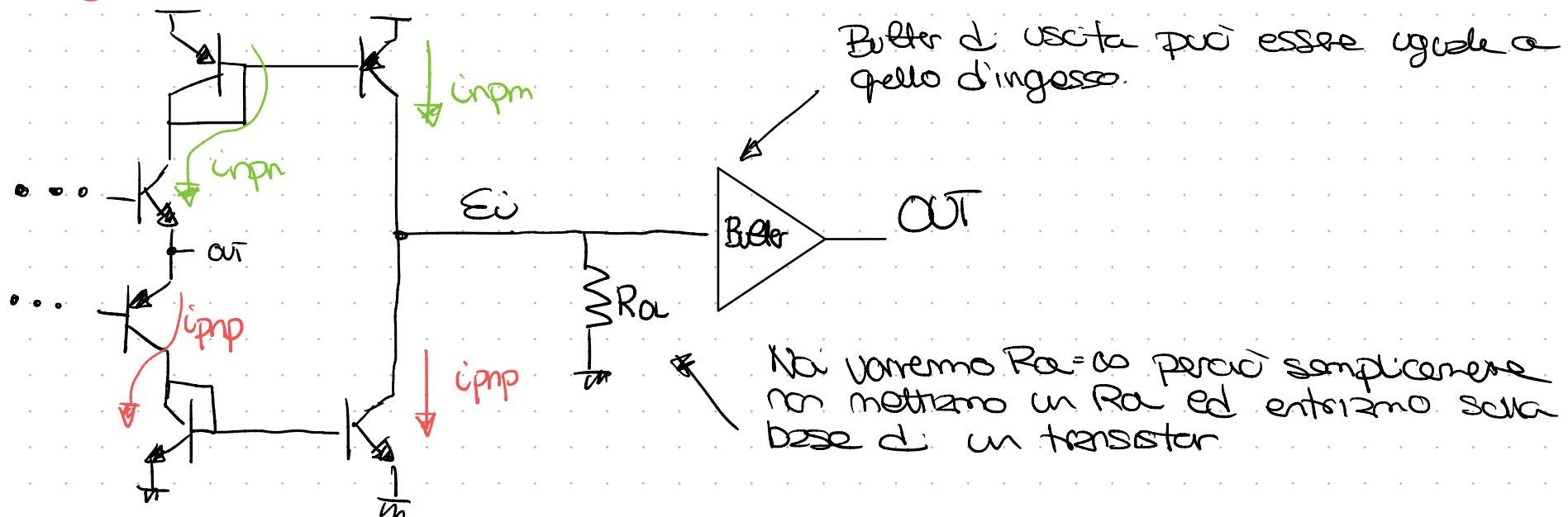Noi vogliamo coprire la corrente data dai mos n-p-n e p-n-p





CFA: transient response... SlewRate

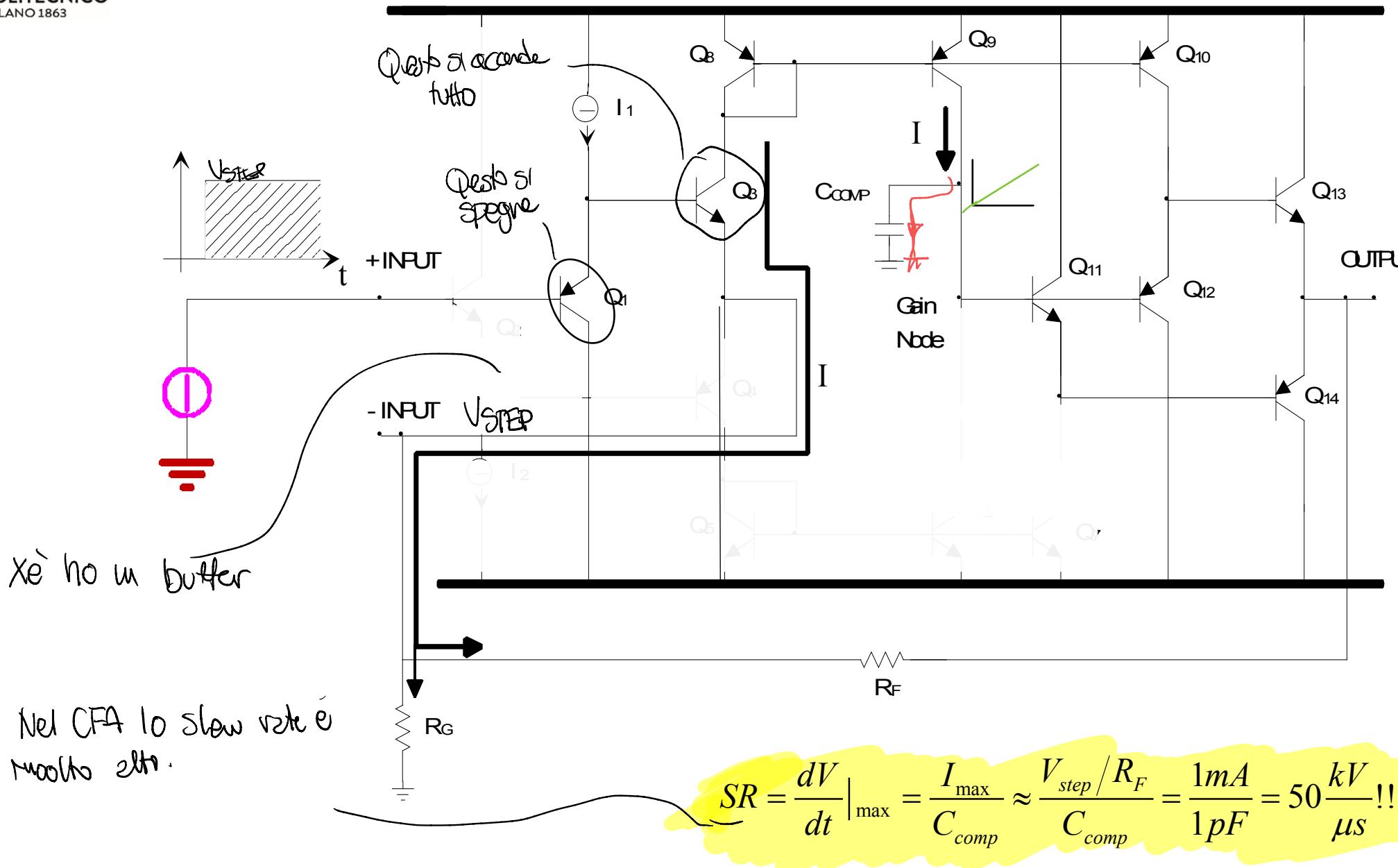





CFA: transient response

Indeed there are second-order effects, which degrade SR

hodabile capacità parallela ovvero si che zbb12 in transitorio. Per crescere queste capacità non c'è un problema perché si cercano veloci ma quando abbiamo uno step negativo ho che il BJT si spegne e quindi la capacità si può scaricare solo sulla r resistenza del gen di come.

si spegne perché $V_{in} = V_B < V_E$

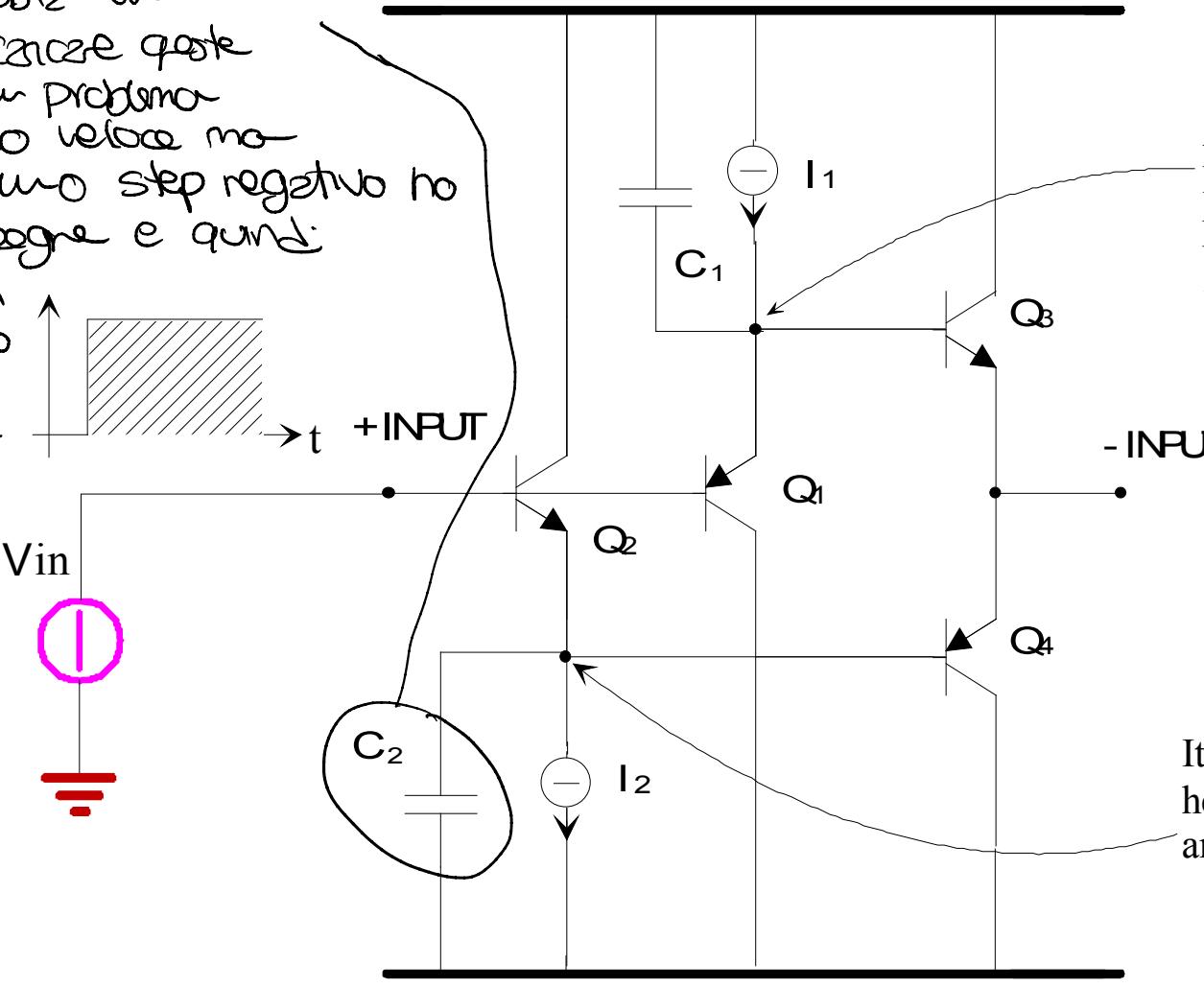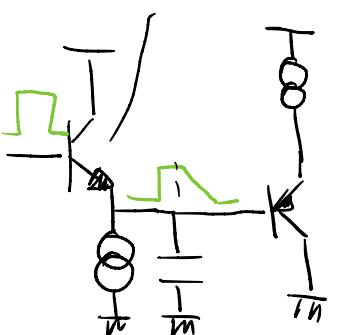


At first it stays charged hence Q₁ goes off instead of pulling up the node


It takes time to be charged up hence the node stays low and Q₄ keeps sinking current



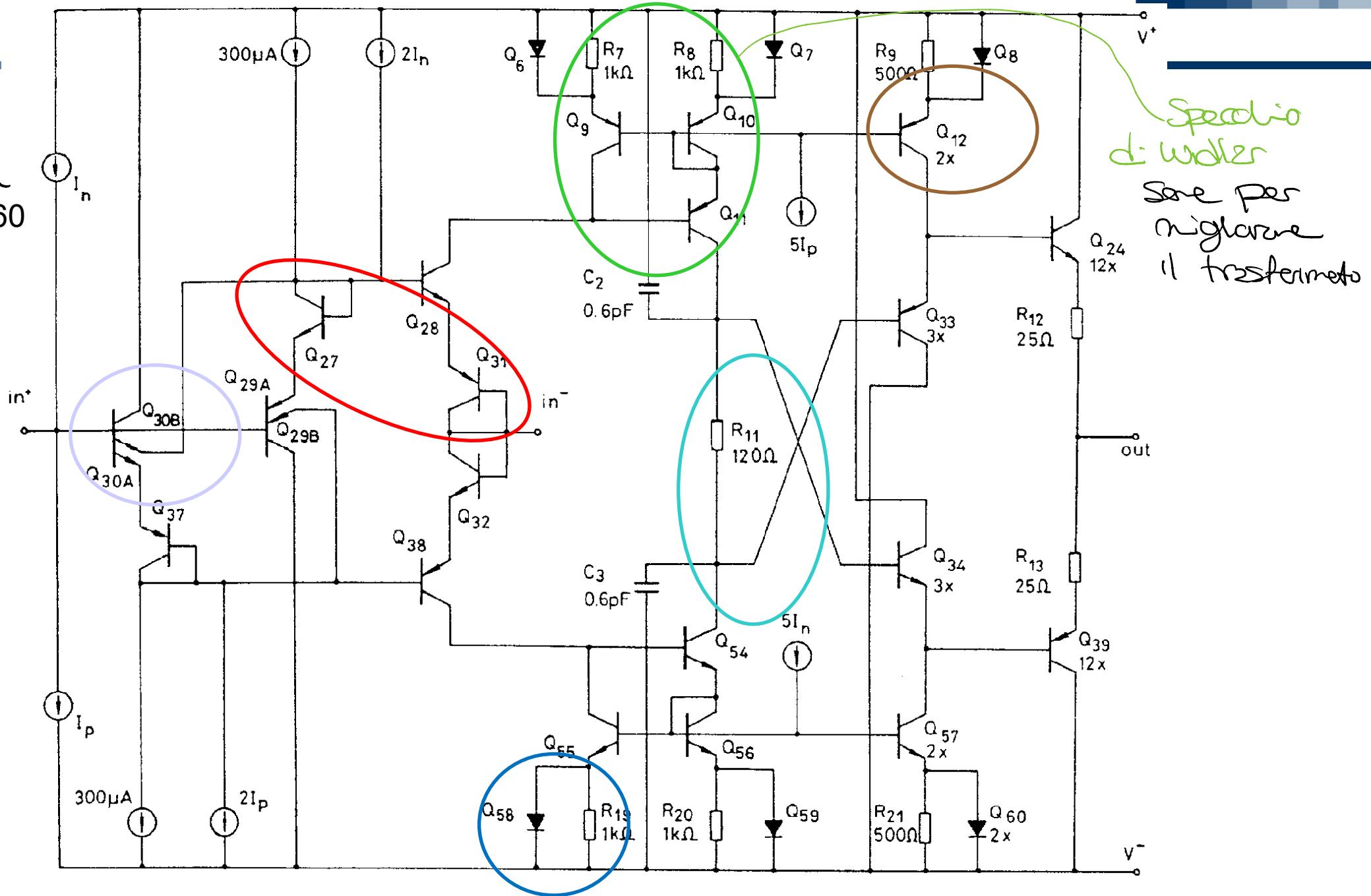Questa e' un'altra architettura
e migliora OPA260
tutto.



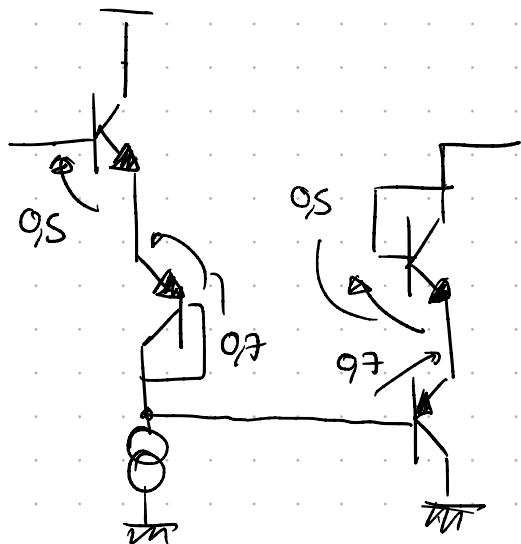
Penso che una cosa del tipo per compansare



faccio 2 transistori in modo che se V_T drifta in modo diverso tra 2 npn e pnp ho che i 2 std sono comunque compensati

(Bisogna far fare la stessa cosa con l'altra parte del circuito batteria)

Altro problema di zzzzuzzo è che

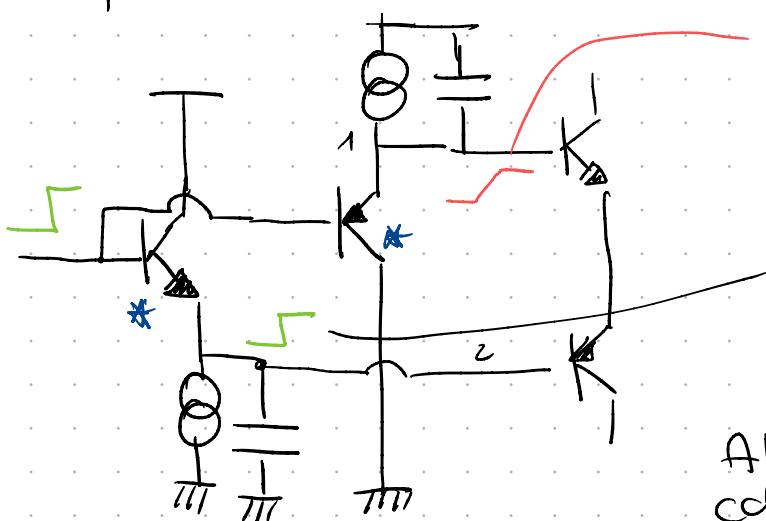

Al contrario qui ho che il segnale è molto lento

Sono felice perché qui ho che lo step è veloce


Per risolvere questo uso un transistor multivettore

Al posto di questi 2 transistori ~~blu~~ netto, 2 multivettori da collegare a 1 e 2. queste porte del transistor è sempre off tranne quando ho un grandissimo step in ingresso



CFA: other architectures

Data-sheet LH4117:

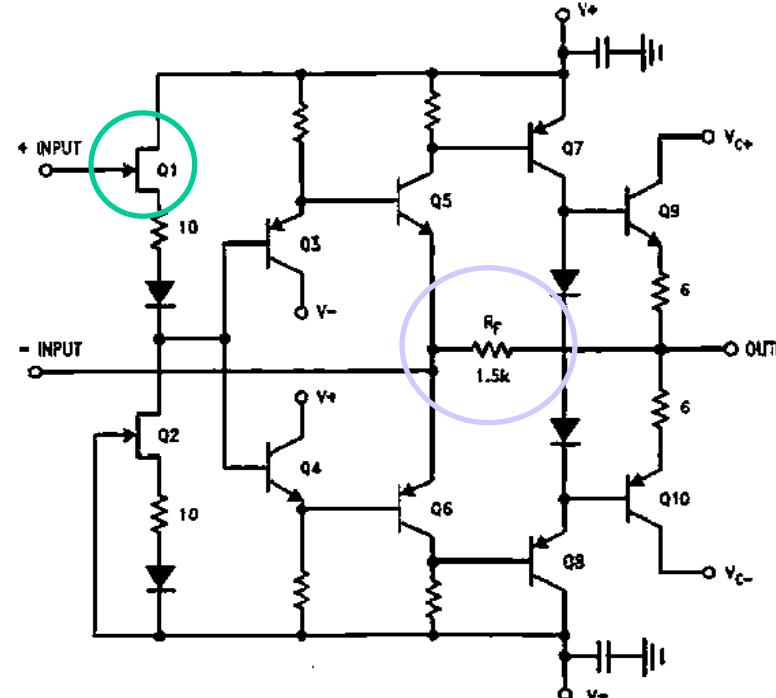

Application-note:



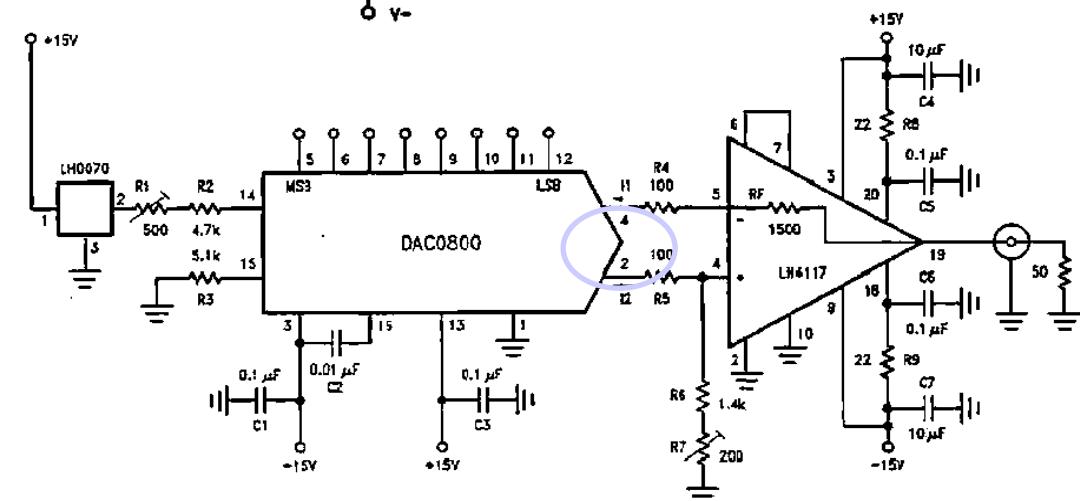
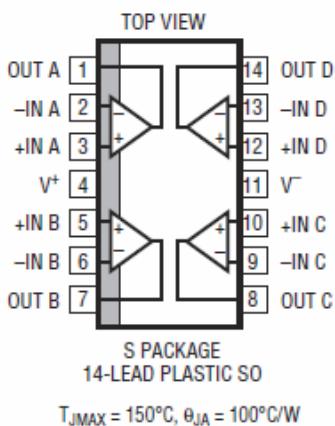
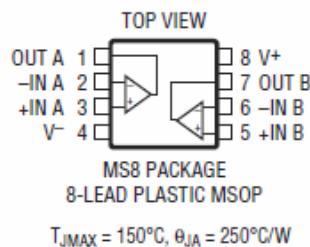


FIGURE 7. Fast Current-to-Voltage Current Mode DAC Amplifier

TL/K/10377-1D

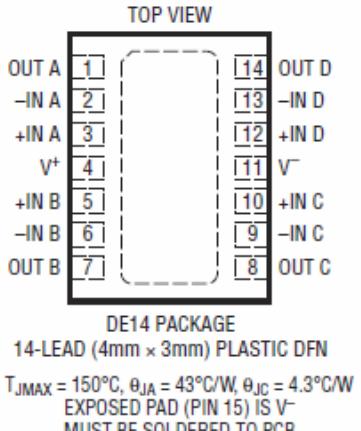

Data-sheet LT1395:

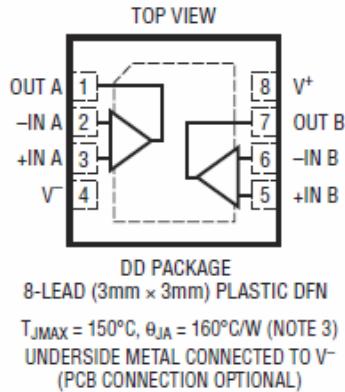

FEATURES

- 400MHz Bandwidth on $\pm 5\text{V}$ ($A_v = 1$)
- 350MHz Bandwidth on $\pm 5\text{V}$ ($A_v = 2, -1$)
- 0.1dB Gain Flatness: 100MHz ($A_v = 1, 2$ and -1)
- High Slew Rate: 800V/ μs
- Wide Supply Range: $\pm 2\text{V}(4\text{V})$ to $\pm 6\text{V}(12\text{V})$
- 80mA Output Current
- Low Supply Current: 4.6mA/Amplifier
- LT1395: SO-8, TSOT23-5 and TSOT23-6 Packages
LT1396: SO-8, MSOP and Tiny 3mm x 3mm x 0.75mm DFN-8 Packages
LT1397: SO-14, SSOP-16 and Tiny 4mm x 3mm x 0.75mm DFN-14 Packages
- Low Profile (1mm) ThinSOT™ Package

APPLICATIONS

- Cable Drivers
- Video Amplifiers
- MUX Amplifiers
- High Speed Portable Equipment
- IF Amplifiers

DESCRIPTION

The LT®1395/LT1396/LT1397 are single/dual/quad 400MHz current feedback amplifiers with an 800V/ μs slew rate and the ability to drive up to 80mA of output current.



The LT1395/LT1396/LT1397 operate on all supplies from a single 4V to $\pm 6\text{V}$. At $\pm 5\text{V}$, they draw 4.6mA of supply current per amplifier. The LT1395CS6 also adds a shutdown pin. When disabled, the LT1395CS6 draws virtually zero supply current and its output becomes high impedance. The LT1395CS6 will turn on in only 30ns and turn off in 40ns, making it ideal in spread spectrum and portable equipment applications.

For space limited applications, the LT1395 is available in TSOT-23 packages, the LT1396 is available in a tiny 3mm x 3mm x 0.75mm dual fine pitch leadless DFN package, and the LT1397 is available in a tiny 4mm x 3mm x 0.75mm DFN package.

The LT1395/LT1396/LT1397 are manufactured on Linear Technology's proprietary complementary bipolar process. They have standard single/dual/quad pinouts and they are optimized for use on supply voltages of $\pm 5\text{V}$.

LT, LTC, LTM, Linear Technology and the Linear logo are registered trademarks of Linear Technology Corporation. All other trademarks are the property of their respective owners.

TYPICAL APPLICATION

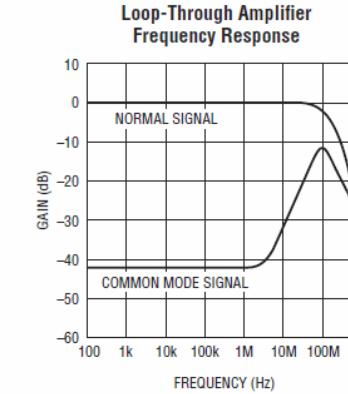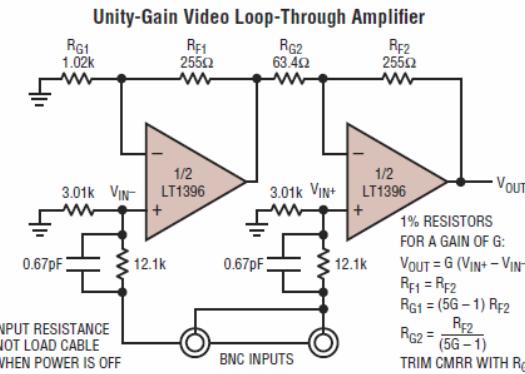



Data-sheet LT1395:


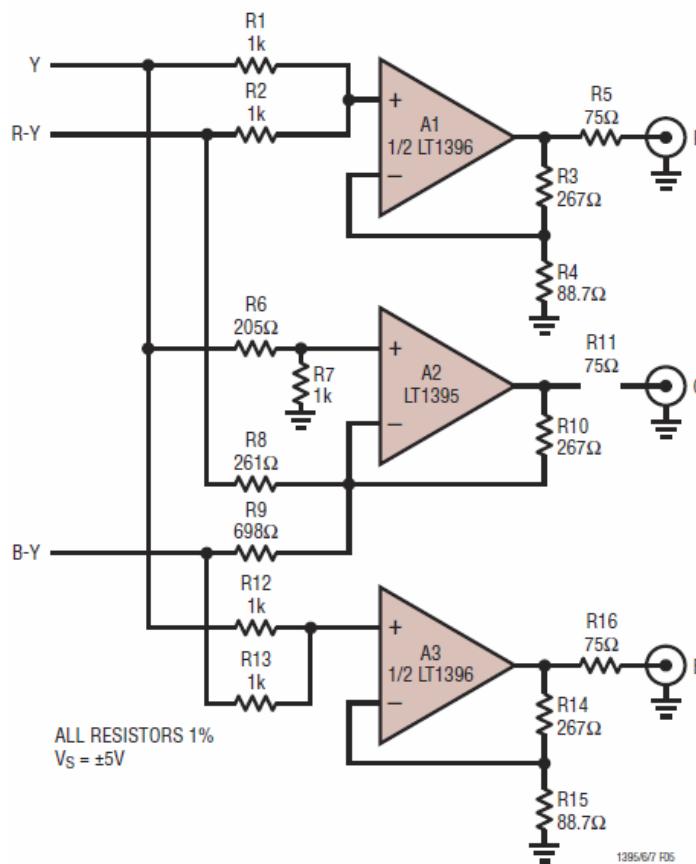


Figure 5. Buffered Color-Difference to RGB Matrix

$$K_R + K_G + K_B = 1$$
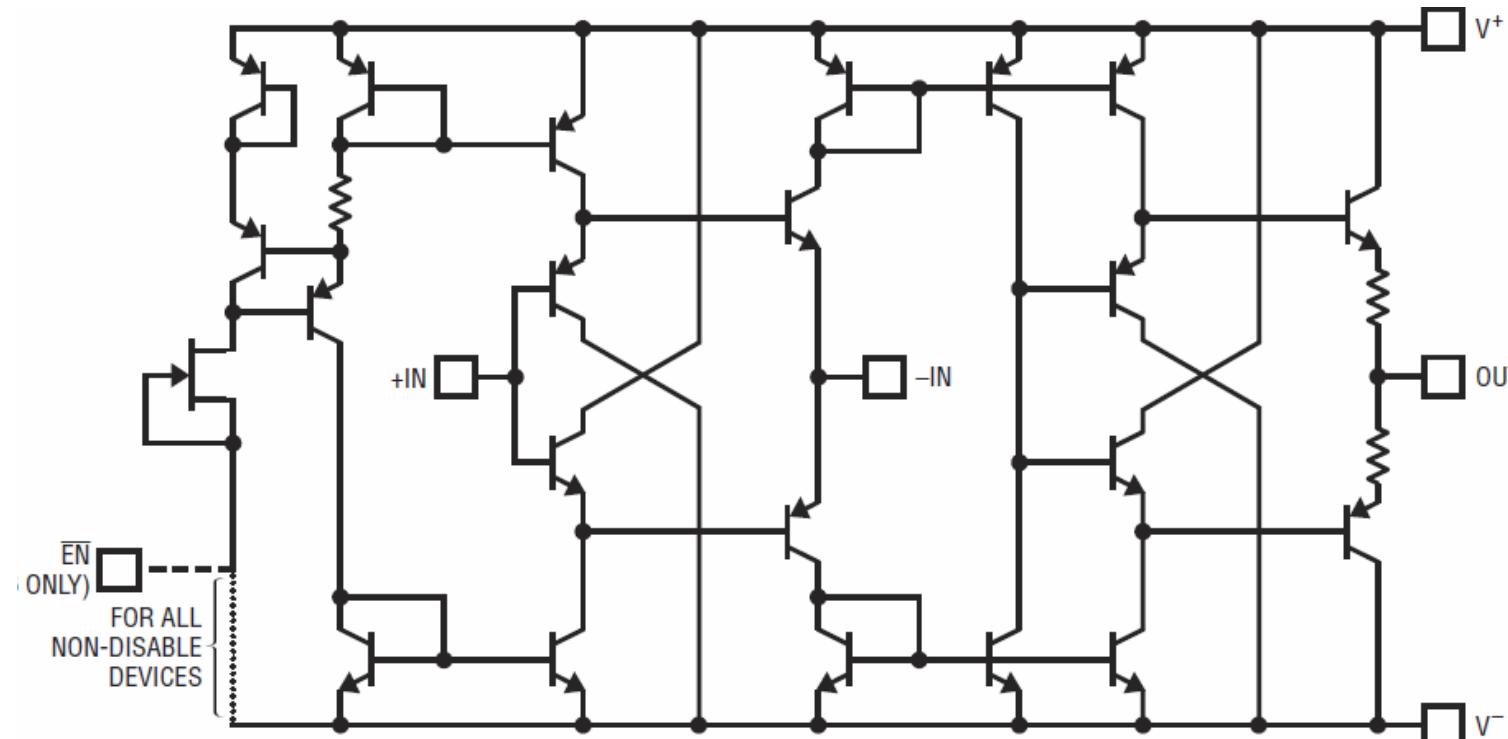
$$\begin{aligned}K_R &= 0.299 \\K_G &= 0.587 \\K_B &= 0.114\end{aligned}$$



$$Y' = K_R \cdot R' + K_G \cdot G' + K_B \cdot B'$$

$$P_B = \frac{1}{2} \cdot \frac{B' - Y'}{1 - K_B}$$

$$P_R = \frac{1}{2} \cdot \frac{R' - Y'}{1 - K_R}$$

digital component video



- New topology of feedback
- Don't limit your imagination (always investigate new solutions)
- Very high bandwidth (at low gain though)

Next lesson: **08 – OTA and ISO amplifiers**