

Variability And Matching

OMR and effect performances of a different amplifier are mainly affected by components' tolerances. They depend on material properties variability and on dimensional parameters variability.

→ RESISTORS

$$R = \frac{S}{W\Delta} L = R_0 \cdot \frac{L}{W} \quad R_0 \in [10 \Omega; 1 k\Omega]$$

$$\Delta R = \frac{L}{W} \Delta R_0 + \frac{R_0}{W} \Delta L + R_0 L \frac{\Delta W}{W^2} \quad (\text{We sum them up in abs to account for the worst case})$$

$$\frac{\Delta R}{R} = \frac{L}{W} \frac{\Delta R_0}{R_0} + \frac{R_0}{W} \frac{\Delta L}{L} + R_0 \cdot L \frac{\Delta W}{W}$$

Mutually negligible

We assume that S and Δ are subjected to variability over a characteristic spatial length $\Lambda \ll W, L$. From this condition, we can divide the resistors in elementary volumes of height Δ and area $A_0 = \Lambda \cdot \Lambda$. Each elementary volume will have a random distribution of R_0 with \bar{R}_0 mean value and $\sigma(\bar{R}_0)$ standard deviation.

We can see the resistors as a matrix of $m \times n$ resistors, $m = \frac{L}{\Lambda}$ and $n = \frac{W}{\Lambda}$, each of them being a sample of a Gaussian distribution.

① ROWS $G_1 = \sum_{i=1}^N G_{1,i}$

$$E[G_1] = \sum_{i=1}^N E[G_{1,i}] = N \bar{G}_0$$

Now, being $G = \frac{1}{R}$ we may write


$$\frac{dG}{G} = \frac{dR}{R}, \Rightarrow \frac{\sigma^2(G)}{G^2} = \frac{\sigma^2(R)}{R^2}$$

assigning to R_0 with small variances, in

order not to have PERCOLATIVE PATHS (high total resistance, high variability)

$$\sigma^2(G_1) = \sum_{i=1}^N \sigma^2(G_{1,i}) = N \sigma^2(\bar{R}_0)$$
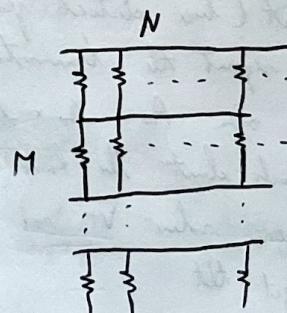
$$\frac{\sigma(G_1)}{G_1} = \frac{\sqrt{N} \sigma(\bar{R}_0)}{N \bar{R}_0} = \frac{\sigma(\bar{R}_0)}{\bar{R}_0} \cdot \frac{1}{\sqrt{N}} = \frac{\sigma(\bar{R}_0)}{\bar{R}_0} \cdot \frac{1}{\sqrt{N}} = \frac{\sigma(R_0)}{R_0}$$



② COLUMNS

$$R_{\text{row}} = \frac{1}{N \bar{R}_0} = \frac{\bar{R}_0}{N}$$

$$\frac{\sigma(R_{\text{row}})}{R_{\text{row}}} = \frac{\sigma(\bar{R}_0)}{\bar{R}_0} \cdot \frac{1}{\sqrt{N}}$$

34) So we get that the mean value of the total resistance is

$$\bar{R} = M \frac{\bar{R}_0}{N}$$

and the standard deviation is

$$\frac{\sigma(\bar{R})}{\bar{R}} = \frac{\sqrt{M \sigma^2(R_{\text{row}})}}{M \frac{\bar{R}_0}{N}} = \frac{\sigma(R_{\text{row}})}{\bar{R}_0} = \frac{\sigma(R_0)}{R_0} \cdot \frac{1}{\sqrt{MN}} = \frac{\sigma(R_0)}{R_0} \cdot \frac{\sqrt{M}}{\sqrt{WL}}$$

$$\Rightarrow \frac{\sigma(R)}{R} = \frac{M \sigma R}{\sqrt{WL}}$$

Let's consider now two nominally identical resistors R_1 and R_2 : if they are manufactured close to each other, the mismatch is mainly due to statistical variability, so we can write

$$\Delta R = \sigma(\Delta R) = \sqrt{\sigma^2(R_1) + \sigma^2(R_2)}$$

$$\frac{\sigma(\Delta R)}{\Delta R} = \sqrt{\frac{\sigma^2(R_1)}{R^2} + \frac{\sigma^2(R_2)}{R^2}} = \sqrt{\frac{2 \sigma^2(R)}{WL}} = \frac{\sqrt{2} \sigma R}{\sqrt{WL}} = \frac{M \sigma R}{\sqrt{WL}}$$

→ TRANSISTORS

As for resistors, also for transistors the variability due to threshold and conductivity coefficient (base electrical properties) are limited with respect to dimensional parameters.

Let's represent the transistors area into a matrix of $M \times N$ shorted transistors with area $A_0 = 1 \times 1$ in which the variability affects the V_T value.

For each short the local V_T is a sample extracted from a Gaussian distribution of mean value \bar{V}_T and standard deviation $\sigma(V_T)$

We get that

[The overall threshold is the average of all the average conductivities of each shorted area]

$$\bar{V}_T = E[E[V_{T,i}]] = \bar{V}_T = \frac{1}{M \cdot N} \sum_{i=1}^N \sum_{j=1}^M V_{T,j}$$

$$\sigma^2(\bar{V}_T) = E[(E[V_{T,i}])^2] = \frac{1}{(M \cdot N)^2} \cdot \sigma^2 \left(\sum_{i=1}^N V_{T,i} \right) = \frac{1}{(M \cdot N)^2} \cdot M \cdot N \cdot \sigma^2(V_{T,0})$$

$$\sigma(\bar{V}_T) = \sqrt{\frac{A_0}{W \cdot L} \sigma^2(V_{T,0})} = \frac{M \sigma}{\sqrt{WL}}$$

and, considering two nominally equal transistors,

$$\sigma(\Delta V_T) = \frac{\sqrt{2} M \sigma}{\sqrt{WL}} = \frac{M \sigma}{\sqrt{WL}}$$

$V_{T,i} \triangleq$ threshold of an shorted area
 $V_{T,0} \triangleq$ average threshold of an shorted area
 $\sigma(V_{T,0}) \triangleq$ standard deviation of an shorted area

CIRR

We can write, in general,

$$V_{out} = G_d V_d + G_m V_{cm} = G_d \left[V_d + \frac{G_m}{G_d} V_{cm} \right] = G_d \left[V_d + \frac{V_{cm}}{CMRR} \right]$$

so the common mode signal, together with the CMRR, is responsible for an output referred offset. Since CMRR depends on frequency, @ HF this effect contribution may be relevant.


Let's assume to have an input common mode signal at the input, it is almost entirely bypassed at this node, being thus follows:

$$i_{cm} = \frac{V_{cm}}{2R_{o,g}} \quad [\text{Common mode current flowing in the two branches}]$$

One to remember we may have that $i_{out} = \epsilon i_{cm}$, so

$$G_m = \frac{\epsilon R_{out}}{2R_{o,g}}$$
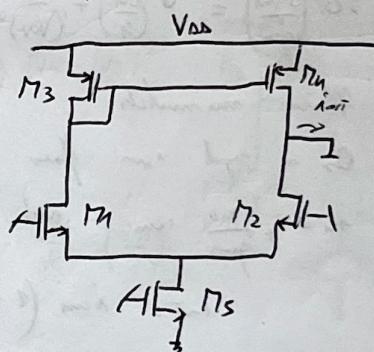
$$CMRR = \frac{gm_{ds} R_{out}}{\frac{\epsilon R_{out}}{2R_{o,g}}} = \frac{2gm_{ds} R_{o,g}}{\epsilon}$$



→ DETERMINISTIC ϵ

(1) Matching error

i_{cm} in the left-hand branch is partially lost into $R_{o,g}$ and not mirrored, thus causing



$$\epsilon = i_{cm} \frac{1/gm_{M1}}{\frac{1}{gm_{M1}} + R_{o,g}} = i_{cm} \frac{1}{1 + gm_{M1} R_{o,g}} \approx \frac{i_{cm}}{gm_{M1} R_{o,g}}$$

(2) Unbalanced resistances at the output pair's drain nodes

$$R_{S,1} = \frac{\frac{1}{gm_{M1}} + R_{o,D}}{1 + gm_{ds} R_{o,D}} =$$

$$R_{S,2} = \frac{\frac{R_{o,D}}{gm_{M2}}}{\frac{1}{gm_{M2}} + R_{o,D}} = \frac{R_{o,D}}{1 + gm_{ds} R_{o,D}}$$

$$\epsilon i_{cm} = 2i_{cm} \frac{R_2}{R_1 + R_2} - 2i_{cm} \frac{R_1}{R_1 + R_2} = \frac{R_2 - R_1}{R_2 + R_1} 2i_{cm} = \frac{\frac{1}{gm_{M1}}}{2R_{o,D} + \frac{1}{gm_{M1}}} 2i_{cm}$$

$$R_2 - R_1 = -\frac{1}{gm_{M1}}$$

$$R_2 + R_1 = \frac{2R_{o,D} + \frac{1}{gm_{M1}}}{1 + gm_{ds} R_{o,D}}$$

(36)

$$\text{iam } \Sigma \approx \frac{1}{2\rho_{0,D} g_{m,11}} \cdot 2 \text{iam} = \frac{1 \text{iam}}{\rho_{0,D} g_{m,11}}$$

$$\Rightarrow \left[\Sigma_{\text{DET}} \approx \frac{1}{\rho_{0,D} g_{m,11}} + \frac{1}{\rho_{0,T} g_{m,11}} \right]$$

→ STATISTICAL OVR

$$dgm = d(2 \text{iam}) = 2 d\text{iam} + 2 dV_T$$

$$\frac{dgm}{gm} = \frac{dk}{k} + \frac{dV_T}{V_T}$$

Assume that Δk and ΔV_T are statistically independent (they are not) we get

$$\sigma^2 \left(\frac{\Delta gm}{gm} \right) = \sigma^2 \left(\frac{\Delta k}{k} \right) + \frac{1}{(V_T)^2} \sigma^2 (\Delta V_T)$$

[Because for example a variation of V_T multiplies C_{ox} , which is present both in k and V_T formulae]

① Mirror mismatch

On a rigid iam flows into N_3 , $i_{N_3} = - \frac{1 \text{iam}}{gm_3}$, then we get

$$i_k = + \frac{gm_6}{gm_3} \text{iam} \quad \text{and so}$$

$$i_{\text{out}} = \text{iam} \left(1 - \frac{gm_6}{gm_3} \right) = \frac{gm_3 - gm_6}{gm_3} \text{iam} \approx \frac{\Delta gm_6}{gm_6} \text{iam}$$


so

$$\Sigma_m^{(\text{STAT})} \approx \frac{\Delta gm_6}{gm_6}$$

② Input mismatch

We need i_{N_5} , so we fold one transistor on the other
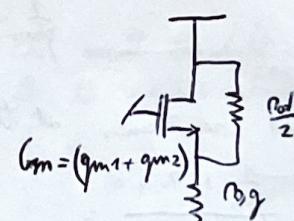
$$\begin{aligned} i_5 &= \text{iam} \cdot \frac{\frac{\rho_{0,g}}{2} / \frac{\rho_{0,D}}{2}}{\frac{\rho_{0,g}}{2} / \frac{\rho_{0,D}}{2} + \frac{1}{2gm}} \\ &\downarrow \\ &= \text{iam} \cdot \frac{2gm_5 \left(\frac{\rho_{0,g}}{2} / \frac{\rho_{0,D}}{2} \right)}{1 + 2gm \left(\frac{\rho_{0,g}}{2} / \frac{\rho_{0,D}}{2} \right)} \end{aligned}$$



$$i_2 - i_1 = i_{\text{out}} = \text{iam} \cdot \frac{(gm_1 - gm_2)}{1 + 2gm \left(\frac{\rho_{0,g}}{2} / \frac{\rho_{0,D}}{2} \right)}$$

$$\downarrow \\ \approx \frac{\Delta gm_6}{2gm_6} \cdot \frac{\frac{\rho_{0,g}}{2} + \frac{\rho_{0,D}}{2}}{\frac{\rho_{0,g}}{2} / \frac{\rho_{0,D}}{2}} \text{iam} = \frac{\Delta gm_6}{gm_6} \frac{\text{iam}}{2gm} \left(\frac{\rho_{0,g}}{\rho_{0,D}} + \frac{\rho_{0,D}}{\rho_{0,g}} \right)$$

$$\Rightarrow \Sigma_D^{(\text{STAT})} = \frac{\Delta gm_6}{gm_6} \left(\frac{2\rho_{0,g}}{\rho_{0,D}} + 1 \right)$$

For $\rho_{0,g} \rightarrow +\infty$ we get OVR → $\frac{2gm_6 \rho_{0,D}}{\left(\frac{\Delta gm_6}{gm_6} \right) \frac{\rho_{0,D}}{\rho_{0,g}}} = \frac{gm_6 \rho_{0,D}}{\left(\frac{\Delta gm_6}{gm_6} \right)}$

OFFSET

In a single-ended OTA, in principle, the output voltage should be at $\frac{V_{DD} - V_{EE}}{2}$ if no differential signal drives the two inputs. If the parameters varied deviate from nominal values, we may have that $V_{OS} \neq \frac{V_{DD} - V_{EE}}{2}$, thus causing an output voltage offset. We usually describe the output as an ideal one with an offset equivalent current placed between the output terminals, when

$$V_{OS} = \frac{V_{OS,DS}}{I(D)}$$


Minibias between transistors of the input stage are more critical, being thus amplified by the total gain of the stage.

$$\rightarrow \frac{k \text{ mismatch}}{I_1 \delta I_2}$$

$$I_1 = \left(k + \frac{\Delta k}{2} \right) (V_{GS} - V_T)^2 ; \quad I_2 = \left(k - \frac{\Delta k}{2} \right) (V_{GS} - V_T)^2$$

$$|\Delta I| = |\Delta k (V_{GS} - V_T)^2| = |I_1 - I_2|$$

$$V_{OS/km} = \frac{|\Delta I|}{gm} = \frac{V_{os}^2 \Delta k}{gm} = \frac{V_{os}^2 \cdot \Delta k}{2k \cdot V_{os}} = \frac{\Delta k}{k} \cdot \left(\frac{V_{os}}{2} \right)$$

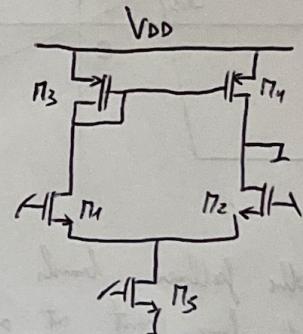

$$\rightarrow \frac{V_T \text{ mismatch}}{I_1 \delta I_2}$$

$$I_1 = k \left(V_{GS} - V_T - \frac{\Delta V_T}{2} \right)^2 ; \quad I_2 = k \left(V_{GS} - V_T + \frac{\Delta V_T}{2} \right)^2$$

$$|\Delta I| = \left| k \left[\left(V_{GS} - V_T \right)^2 + \frac{\Delta V_T^2}{4} - 2V_{os} \cdot \frac{\Delta V_T}{2} - \left(V_{GS} - V_T \right)^2 + \left(\frac{\Delta V_T^2}{4} \right) - 2V_{os} \cdot \frac{\Delta V_T}{2} \right] \right| = 2k V_{os} \cdot \Delta V_T$$

$$V_{OS/\Delta V_T} = \frac{|\Delta I|}{gm} = \frac{2k V_{os}}{2k V_{os}} \cdot \Delta V_T = \Delta V_T$$

$$\rightarrow \frac{k \text{ mismatch}}{I_3 \delta I_4}$$

$$I_3 = \left(k_m + \frac{\Delta k_m}{2} \right) (V_{GS} - V_T)^2 ; \quad I_4 = \left(k_m - \frac{\Delta k_m}{2} \right) (V_{GS} - V_T)^2$$

$$|\Delta I| = 2 \frac{\Delta k_m}{2} (V_{GS} - V_T)^2$$

$$V_{OS/\Delta k_m} = \frac{|\Delta I|}{gm} = \frac{\Delta k_m}{2k_D \cdot V_{os}} V_{os}^2 = - \frac{\Delta k_m V_{os, D}^2}{2I} V_{os, D} = \frac{V_{os, D}}{2} \left(\frac{\Delta k_m}{k_m} \right)$$

$$\rightarrow \frac{V_T \text{ mismatch}}{I_3 \delta I_4}$$

$$I_3 = k_m \left(V_{GS} - V_T - \frac{\Delta V_T}{2} \right)^2 ; \quad I_4 = k_m \left(V_{GS} - V_T + \frac{\Delta V_T}{2} \right)^2$$


38

$$|\Delta I| = 2k_m V_{os,M} \cdot \Delta V_T$$

$$V_{os}|_{AVT} = \frac{2k_m V_{os,M}}{g_m} \Delta V_T = \frac{2k_m V_{os,M}}{2I} \cdot V_{os,D} \cdot \Delta V_T = \frac{2I}{V_{os,M}} \cdot \frac{V_{os,D} \Delta V_T}{2I} = \frac{V_{os,D}}{V_{os,M}} \Delta V_T$$

$$\Rightarrow \sigma^2(V_{os}) = \sigma^2(\Delta V_T) + \sigma^2(\Delta V_{os,D}) \left(\frac{V_{os,D}}{V_{os,M}} \right)^2 + \left[\sigma^2\left(\frac{\Delta V_T}{V_{os,D}}\right) + \sigma^2\left(\frac{\Delta V_{os,D}}{V_{os,D}}\right) \right] \left(\frac{V_{os,D}}{2I} \right)^2$$

Offset is compensated by FEEDBACK:

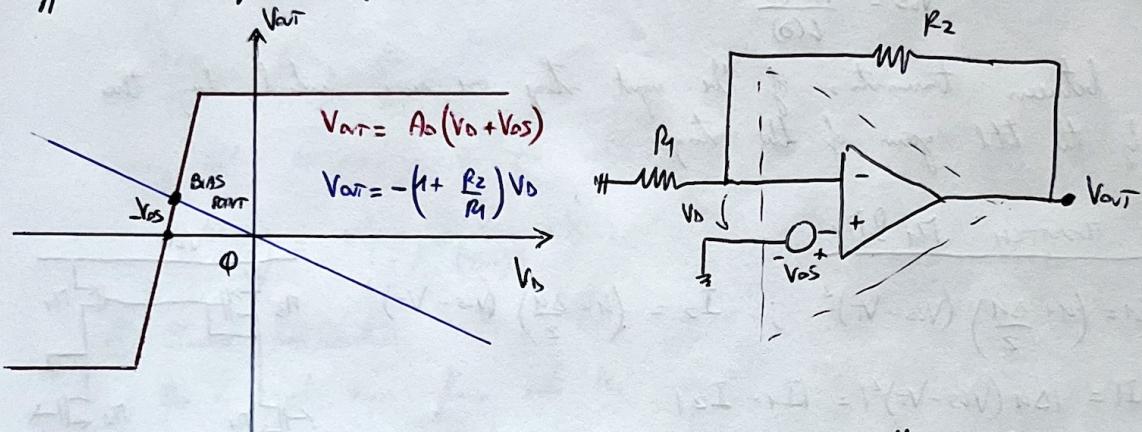

the feedback branch introduces a new relationship in the system, this setting the bias point at a value lower than the power supply. In order to have this situation, it must be

$$(1 + \frac{R_2}{R_1}) \ll A_o$$

↓

$$A_o \frac{R_1}{R_1 + R_2} \gg 1$$

$A_o \frac{R_1}{R_1 + R_2}$

[Therefore in order to properly act on the feedback nodes, the loop gain must be properly wired and $\gg 1$.]