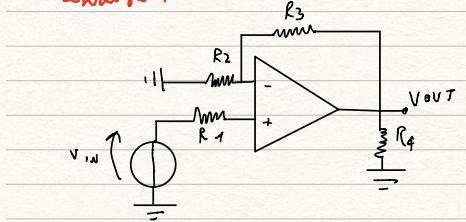


Exercise 1



$$G_{\text{loop}} = \frac{G_{1d}}{1 - \frac{1}{G_{\text{loop}}}}$$

$$R_2 = 10 \text{ k}\Omega$$

$$R_3 = 100 \text{ k}\Omega$$

$$R_4 = 100 \text{ k}\Omega$$

$$A_{\text{diff}} = 720 \text{ dB} (\approx 10^6)$$

Opamp ideal $A_{\text{diff}} \rightarrow \infty$

RETROAZIONE NEGATIVA

1) Amplificatore reale $\frac{V_{\text{OUT}}}{V_{\text{IN}}}$

$-G_{1d}$ (HP: Opamp non ideale)
 $-G_{\text{loop}}$

Salendo G_{1d} :

$$i_{R_1} = 0 \rightarrow V^+ = V_{\text{IN}}$$

$$V^- = V^+$$

$$V_{R2} = V^- = V_{\text{IN}}$$

$$i_{R2} = \frac{V_{R2}}{R_2} = \frac{V_{\text{IN}}}{R_2}$$

$$i_{R3} = i_{R2} \rightarrow V_{R3} = i_{R3} \cdot R_3 = \frac{V_{\text{IN}}}{R_2} \cdot R_3$$

$$V_{\text{OUT}} = V^+ + V_{R3} = V_{\text{IN}} \left(1 + \frac{R_3}{R_2} \right)$$

$$G_{1d} = \left(1 + \frac{R_3}{R_2} \right) = 11$$


esempio

$$V_{\text{IN}} = 100 \text{ mV}$$

$$V_{\text{OUT}} = 1,1 \text{ V}$$

$$V_{\text{OUT}} = V_{\text{diff}} \quad A_{\text{diff}}$$

$-G_{\text{loop}}$

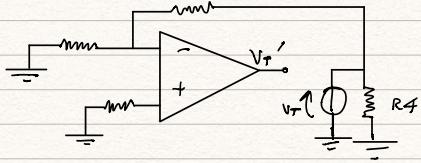

$$G_{loop} = \frac{V_T'}{V_T}$$

$$V^- = V_T \cdot \frac{R_2}{R_2 + R_3}$$

$$V^+ = 0$$

$$V_T' = (V^+ - V^-) \cdot A_{diff} = -A_{diff} \cdot \frac{R_2}{R_2 + R_3} \cdot V_T$$


$$G_{loop} = -A_{diff} \frac{R_2}{R_2 + R_3} = -90909$$

$$G_{feed} = \frac{G_{ID}}{1 - \frac{1}{G_{loop}}} = \frac{11}{1 - \frac{1}{(-90909)}} = 109998$$

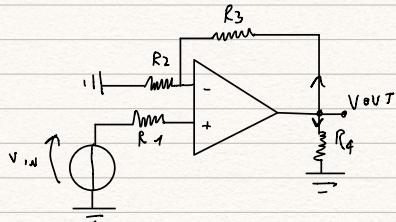2) Amplificatore rail to rail

$$V_{DD} = +15V \quad V_{SS} = -15V$$


Quanto vale la massima corrente di uscita?



CASO PESSIMO PER $V_{OUT} = +15V$

$$I_{OUT} = I_{R4} + I_{retro} = V_{OUT} \left(\frac{1}{R_4} + \frac{1}{R_3 + R_2} \right) = 286,4 \mu A$$

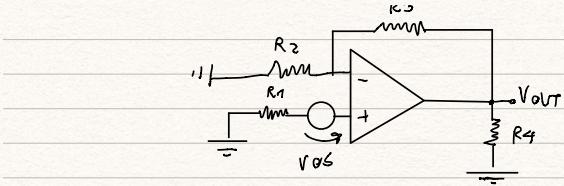
3) Voltaggio effetto su V_{OUT} di V_{OS} = $\pm 3,5 mV$



$$V^+ = V_{os}$$

$$V^- = V^+$$
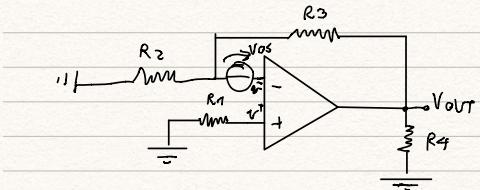
$$V_{out} = \pm V_{os} \left(1 + \frac{R_3}{R_2} \right)$$



$$V^+ = 0$$

$$V^- = V^+$$

$$V_{R2} = -V_{os} \rightarrow i_{R2} = -\frac{V_{os}}{R_2}$$

$$V_{R3} = -\frac{V_{os}}{R_2} R_3$$

$$V_{out} = \pm \left(V_{os} \left(1 + \frac{R_3}{R_2} \right) \right) = \pm 27.5 \text{ mV}$$

4) Soluzio[n]e effetto delle correnti di bias incanti e dell'offset di corrente dell'op.amp. sull'uscita


$$I_{BIAS} = \frac{I^+ + I^-}{2}$$

$$I_{os} = |I^+ - I^-|$$


$$I^+ = I_{BIAS} + \frac{I_{os}}{2}$$

$$I^- = I_{BIAS} - \frac{I_{os}}{2}$$


$$-I_{BIAS}$$

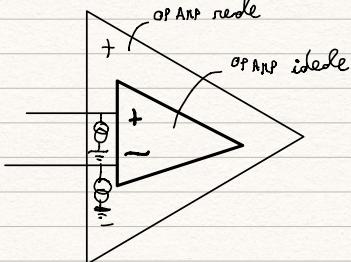

$$I_B^+ = I_B^- = I_{BIAS}$$

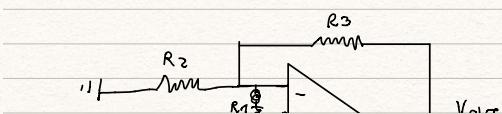

$$V_{out}|_{I_B \neq 0} = I_B^+ R_1 \left(1 + \frac{R_3}{R_2} \right)$$

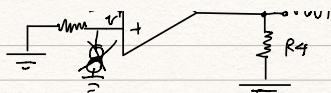


$$V_{\text{OUT}} | I_B = -I_B / R_3$$

$$V_{\text{OUT}} = I_{\text{BIAS}} \left(R_1 \left(1 + \frac{R_3}{R_2} \right) - R_3 \right)$$

$$\text{Se } R_1 \left(1 + \frac{R_3}{R_2} \right) = R_3$$

$$V_{\text{OUT}} | I_{\text{BIAS}} = 0$$

- I_{OS}

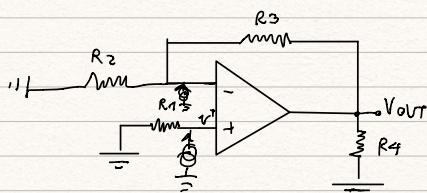


$$V_{\text{OUT}} | I_{\text{OS}}^+ = +I_{\text{OS}}^+ R_1 \left(1 + \frac{R_3}{R_2} \right)$$

$$V_{\text{OUT}} | I_{\text{OS}}^- = +I_{\text{OS}}^- R_3$$

$$|I_{\text{OS}}^+| = |I_{\text{OS}}^-| = \frac{I_{\text{OS}}}{2}$$

$$V_{\text{OUT}} | I_{\text{OS}} = \pm \frac{I_{\text{OS}}}{2} \left(R_1 \left(1 + \frac{R_3}{R_2} \right) + R_3 \right)$$

Exercise 2:

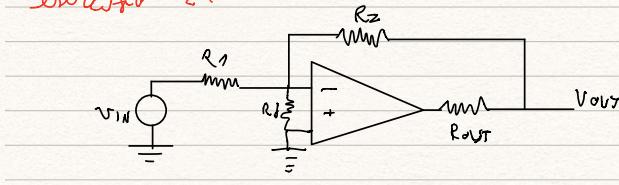

$$R_f = 10 \text{ k}\Omega$$

$$R_2 = 100 \text{ k}\Omega$$

$$R_1 = 1 \text{ M}\Omega$$


$$R_{\text{out}} = 1 \text{ k}\Omega$$

$$A_{\text{diff}} = 100 \text{ dB} (10^5)$$

RETROAZIONE NEGATIVA

$$\text{1) Girele} = \frac{V_{\text{OUT}}}{V_{\text{IN}}} | \text{girele}$$

G_{D} :

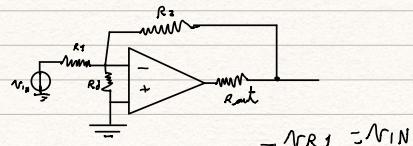


$$I_{R_2} = \frac{V_{\text{IN}}}{R_1} = i R_2$$

$$V_{\text{OUT}} = \beta + (-V_{R_2}) = -V_{\text{IN}} \frac{R_2}{R_1}$$

$$v^- = v^+ = \emptyset \rightarrow i_{Rd} = \emptyset$$

$$\left| \frac{V_{out}}{V_{in}} \right|_{ID} = -\frac{R_2}{R_1}$$

- Gloop

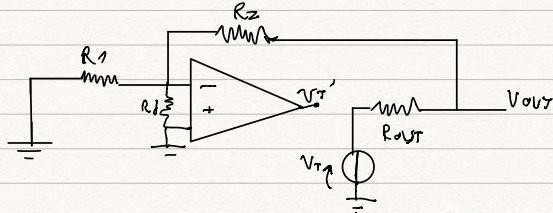

$$\frac{v'_T}{v_T} = G_{loop}$$


$$v^- = v_T - \frac{R_1/R_d}{(R_1/R_d) + R_2 + R_{out}}$$

$$v'_T = -v^- A_{diff}$$


$$G_{loop} = -A_{diff} \frac{R_1/R_d}{(R_1/R_d) + R_2 + R_{out}} = -8927$$

$$Grade = \frac{G_{id}}{1 - \frac{1}{G_{loop}}} = 9,9$$

2) T-Subtree zu Z_{out}

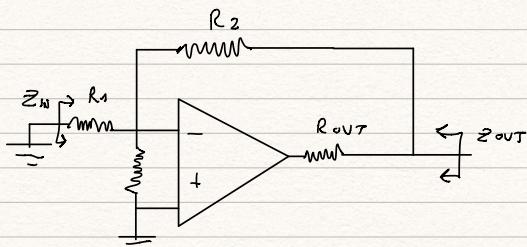

Z_{out}

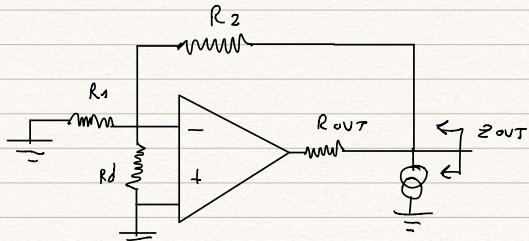


$$Z_{out}^0 = \frac{Z_{out}^0}{1 - G_{loop}}$$

$$Z_{out}^0 = R_{out} \parallel \left[R_2 + \left(R_1 / (R_d) \right) \right] = 991 \Omega$$

$$Z_{out} = \frac{991 \Omega}{1 + 992 f} = 9.11 \Omega$$

Z_{in}

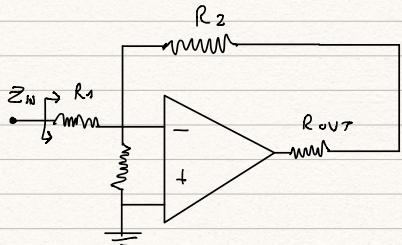


$$Z_{in} = R_1 + R_d \parallel Z^*$$

$$Z^* = \frac{Z^0}{1 - G_{loop}^*}$$


$$Z^0 = R_2 + R_{out}$$

$$G_{loop}^* = -A_{difff}$$
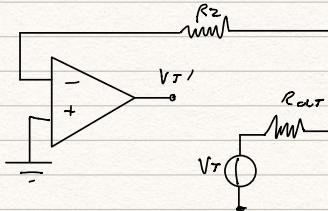
$$Z^* = \frac{R_2 + R_{out}}{1 + A_{difff}} = 1.01 \Omega$$


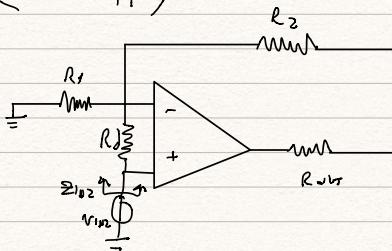
$$Z_{in} = R_1 + R_d \parallel \left(\frac{R_2 + R_{out}}{1 + A_{difff}} \right)$$



retrograde $i_{Rd} \rightarrow 0$


$$Z_{in2} = Z_{in2}^0 (1 - G_{loop})$$

$$Z_{IN2} = R_d + \left[R_1 / (R_2 + R_{OUT}) \right]$$

$$G_{loop} = -\frac{R_1 / R_d}{R_1 / R_d + R_2 + R_{OUT}} \quad A_{diff} \approx -8927$$

$$Z_{IN2} \approx 1 \text{ M}\Omega \quad (1 + 8927) = 8928 \text{ M}\Omega$$

Exercise 3:

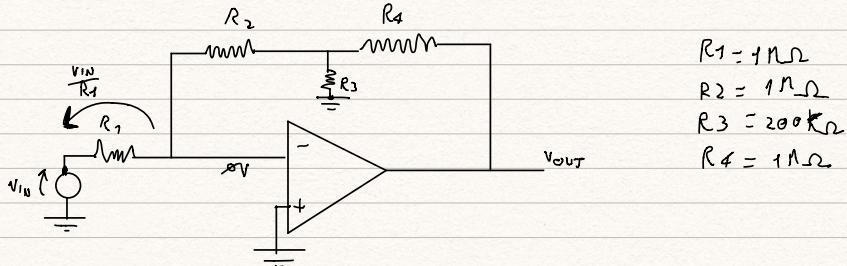

7) G_{ID}

$$iR_1 = iR_2$$

$$\mathcal{V}_{R3} = -\frac{\mathcal{V}_{IN}}{R_1} R_2$$


$$i_{R3} = -\frac{\mathcal{V}_{IN}}{R_1} \frac{R_2}{R_3}$$

$$i_{R4} = iR_2 - iR_3 \approx \frac{\mathcal{V}_{IN}}{R_1} - \left(-\frac{\mathcal{V}_{IN}}{R_3} \frac{R_2}{R_1} \right) = \mathcal{V}_{IN} \left(\frac{1}{R_1} + \frac{R_2}{R_3 R_1} \right)$$

$$\mathcal{V}_{R4} = \frac{\mathcal{V}_{IN}}{R_1} \left(1 + \frac{R_2}{R_3} \right) R_4$$

$$\mathcal{V}_{OUT} = -\frac{\mathcal{V}_{IN}}{R_1} R_2 - \frac{\mathcal{V}_{IN} R_4}{R_1} \left(1 + \frac{R_2}{R_3} \right) = \mathcal{V}_{IN} \left(-\frac{R_2}{R_1} + \frac{R_4}{R_1} \left(1 + \frac{R_2}{R_3} \right) \right)$$

Exercise 4:

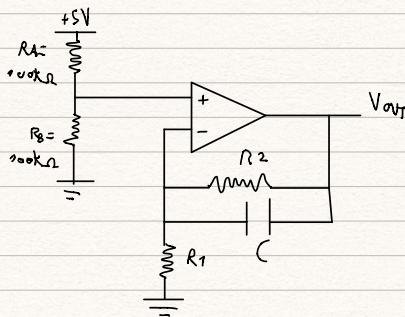


$$\begin{aligned}
 R_2 &= 2 \text{ k}\Omega \\
 R_1 &= 1 \text{ k}\Omega \\
 C &= 5 \text{ pF} \\
 A_{diff} &= 100 \text{ dB} (\rightarrow 10^5) \\
 CMRR &= 80 \text{ dB}
 \end{aligned}$$

$$\left(\frac{A_{diff}}{A_{CM}} = CMRR \rightarrow \frac{10^5}{A_{CM}} = 10^5 \rightarrow A_{CM} = 10 \right)$$

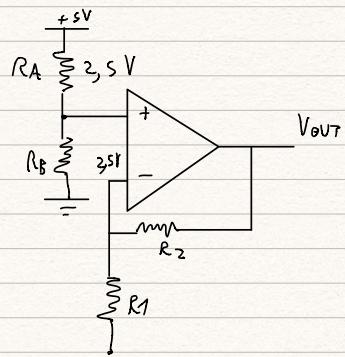7) Con $i_{IN} = 0$

Voltmetro effettua su V_{OUT} solo modo comm. di ingresso



$$V_{OUT} = 2.5 \text{ V} \left(1 + \frac{R_2}{R_1}\right) = 7.5 \text{ V}$$

$$V_{CN} = 2.5 \text{ V}$$