

FILTERS

→ Filter synthesis procedure:

- ① FILTER MASK
- ② FILTER TRANSFER FUNCTION
- ③ NETWORK IMPLEMENTATION (ideal)
- ④ NON-IDEALITIES OPTIMIZATION

→ Filters are divided (classified) into

LOW PASS; HIGH PASS; BAND PASS; STOP-BAND; EQUALIZERS (all pass)

The ideal filter should have

- 1) constant magnitude
- 2) linear phase shift proportional to ω

↓
Def: Let's consider a rigid filter in the pass-band of a filter. It is affected by a phase precession by φ , so

$$x(t) \rightarrow \boxed{\text{FILTER}} \rightarrow y(t) = Ax(t - \varphi)$$

φ must affect my harmonic component, so each harmonic suffers from a $\Delta\varphi = -\frac{2\pi}{T} \cdot \varphi = -\omega\varphi$ shift

These conditions cannot be fulfilled by a real filter, since

Def: Let's consider an ideal LP on a tilted frequency axis, so a rectangle. The inverse Fourier transform is a

$$\begin{aligned} h(t) &= \frac{1}{2\pi} \int_{-\infty}^{\infty} H(\omega) e^{j\omega t} d\omega = \frac{H_0}{2\pi j\omega} \left[\frac{e^{j\omega t}}{j\omega} \right]_{-\infty}^{\infty} = \frac{H_0}{\pi t} \min(\omega t) \\ &\downarrow \\ &= \frac{\omega_0 H_0}{\pi} \frac{\min(\omega t)}{\omega t} = h_0 \cdot \min(\omega t) \end{aligned}$$

$h(t) \neq 0$ for $t < 0 \Rightarrow$ ANTI-CAUSAL, NOT FEASIBLE!

→ Important definitions for the FILTER MASK are

A_{sp} ATTENUATION IN BAND-PASS (maximum)

A_{sb} ATTENUATION IN STOP-BAND (minimum)

ω_{cp} CUT-OFF FREQUENCY

ω_{sb} LOWER LIMIT OF THE STOP-BAND

$\omega_c = \sqrt{\omega_{bp} \cdot \omega_{ap}}$ CENTRAL FREQUENCY OF A BAND-PASS FILTER

$Q = \frac{\omega_c}{\Delta\omega}$ Q FACTOR OF A BAND-PASS FILTER

(49)

$$K = \frac{W_{BP}}{W_{SB}} < 1 \quad \text{SECURITY INDEX} \quad (\text{lower} = \text{worse})$$

$$\epsilon_{BP} = \sqrt{10^{\frac{A_{BP}}{20}} - 1} \quad \text{MAXIMUM ATTENUATION INDEX IN BAND-PASS}$$

$$\epsilon_{SB} = \sqrt{10^{\frac{A_{SB}}{20}} - 1} \quad \text{MINIMUM ATTENUATION INDEX IN STOP-BAND}$$

$$K_E = \frac{\epsilon_{BP}}{\epsilon_{SB}} < 1 \quad \text{DISCRETINATON INDEX} \quad (\text{lower} = \text{better})$$

$$Z_{GD} = -\frac{d\phi}{dw} \quad \text{GROUP DELAY (ideally constant)}$$

ALL POLES FUNCTIONS

- BUTTERWORTH

They require maximum band-pass and stop-band flatness

$$\left. \frac{d^n}{dw^n} |H(jw)|^2 \right|_{w=0} = 0 \quad \text{for } n=1, 2, \dots, 2n-1$$

$$\left. \frac{d^n}{dw^n} |H(jw)|^2 \right|_{w=\infty} = 0 \quad \text{for } n=1, 2, \dots, 2n-1$$

For a required $\omega_0 = 1 \text{ rad/s}$ angular frequency, these conditions are fulfilled by

$$|H(jw)|^2 = \frac{1}{1 + w^{2n}}$$

All poles are placed on a circle of radius $\omega_0 = 1 \text{ rad/s}$ on the complex plane, while

$$Q = \frac{1}{2\zeta} = \frac{|P|}{2\operatorname{Re}[P]} = \frac{1}{2} \quad \text{if REAL}$$

Poles are equally spaced and form the next on the circle by $\frac{\pi}{m}$ and the ones with half Q factors are $\frac{\pi}{2n}$ from from the m th order.

In order to achieve a lower A_{BP} than 3dB we may choose a different ω_0 , then having

$$|H(jw)|^2 = \frac{1}{1 + \left(\frac{w}{\omega_0}\right)^{2n}}$$

Let's fulfill the yes:

$$\frac{1}{1 + \left(\frac{\omega_{BP}}{\omega_0}\right)^{2n}} \geq \frac{1}{1 + \epsilon_{BP}^2} \Rightarrow \omega_0 \geq \frac{\omega_{BP}}{\epsilon_{BP}^{1/m}}$$

$$\frac{1}{1 + \left(\frac{\omega_{SB}}{\omega_0}\right)^{2n}} \leq \frac{1}{1 + \epsilon_{SB}^2} \Rightarrow \omega_0 \leq \frac{\omega_{SB}}{\epsilon_{SB}^{1/m}}$$

(50)

DEM: $\omega_0 \geq \frac{\omega_{BP}}{E_B^{1/m}}$ & $\omega_0 \leq \frac{\omega_{SB}}{E_S^{1/m}}$, by multiplying the
first two from $E_S^{1/m}$ we get

$$\frac{\omega_{BP}}{E_B^{1/m}} \cdot E_S^{1/m} \leq \omega_0 E_S^{1/m} \leq \omega_{SB}$$



$$\omega_{BP} \cdot \kappa^{-1/m} \leq \omega_{SB}$$



$$\kappa^{-1/m} \leq \kappa^{-1}$$



$$\frac{1}{m} \ln(\kappa^{-1}) \leq \ln(\kappa^{-1})$$



$$M \geq \frac{\ln(\kappa^{-1})}{\ln(\kappa^{-1})}$$

And $\frac{\omega_{BP}}{E_B^{1/m}} \leq \omega_0 \leq \frac{\omega_{SB}}{E_S^{1/m}}$

BESSEL

They realize the maximum phase linearity,

$$\left. \frac{d^k \omega_0}{d \omega^k} \right|_{\omega=0} = 0 \quad \text{for } k=1, 2, \dots, M$$

They have poles placed outside the ω_0 characteristic frequency circle, in order to reach a better group delay, thus also a lower selectivity.

In order to realize this, we can either resort to $\omega_0 = 1 \text{ rad/s}$ and we try to see if a specific ω_0 will fulfill the requirement.

CHEBYSHEV - I

They realize the maximum selectivity, but with an in-band ripples.

$$\max \left\{ 1 - |H(j\omega)|^2 \right\}_{\omega \leq 1} \leq E_B^2 \quad \text{maximum ripple requirement}$$

$$\left. \frac{d^k |H(j\omega)|^2}{d\omega^k} \right|_{\omega \rightarrow \infty} = 0 \quad \text{for } k=1, 2, \dots, 2n-1 \quad \text{stop-band flatness}$$

The DC value must be set to 1 for ^{odd} order T.F. and to

$\frac{1}{\sqrt{1+E_B^2}}$ for even order T.F., in order to have $|H(j\omega)| \leq 1$ in band.

51

USEFUL CHEBYSHEV FORMULAS

$$m \geq \frac{\operatorname{arcln}(4\epsilon^{-1})}{\operatorname{arcln}(4\eta^{-1})}$$

$$\Gamma = \left(\frac{1 + \sqrt{1 + \epsilon_{bp}^2}}{\epsilon_{bp}} \right)^{1/m}$$

$$z_n = - \sin \left[(2n-1) \frac{\pi}{2m} \right] \frac{\Gamma^2 - 1}{2\Gamma} + j \cos \left[(2n-1) \frac{\pi}{2m} \right] \frac{\Gamma^2 + 1}{2\Gamma}$$

(for $n = 1, \dots, m$)

$m = \#$ of half oscillations in low-pass

Conside only ~~below~~ the one with $\prod_{k=1}^m [] < 0$

→ POLES AND ZEROS

• CHEBYSHEV II

They have imaginary conjugate zeros in stop band only to be a couple the real will HF disturbances.

$$\max \left\{ 1 - |H(j\omega)|^2 \right\}_{\omega \geq 1} \geq \epsilon_{SB}^2 \quad \text{minimum attenuation in stop band } (\epsilon = \frac{1}{\epsilon_{SB}})$$

$$\left. \frac{d^n}{d\omega^n} |H(j\omega)|^2 \right|_{\omega=0} = 0 \quad \text{for } n = 1, 2, \dots, 2m-1$$

• CHEB

They are a couple ripples both in stop band and in low-pass. Once n and the in-band ripples are set, the stop-band ripple is determined.

• GENERALIZED ELLIPTICAL

They give an additional degree of freedom, so we can independently set η and both ripples, but we get a bad E_{DD} .

→ ADDITIONAL DEMONSTRATION

It can be shown that for a Chebyshev-type-I filter it is

$$|H(j\omega)|^2 = \frac{1}{1 + \epsilon^2 C_m^2(\omega)}$$

$\epsilon \triangleq$ ROLL-OFF FACTOR
 $C_m =$ Chebyshev polynomial

when

$$C_m(\omega) = \begin{cases} \cos \left[m \operatorname{arccos} \left(\frac{\omega}{\omega_{bp}} \right) \right] & \left(\frac{\omega}{\omega_{bp}} \leq 1 \right) \\ \operatorname{ch} \left[m \operatorname{arctanh} \left(\frac{\omega}{\omega_{bp}} \right) \right] & \left(\frac{\omega}{\omega_{bp}} \geq 1 \right) \end{cases} \quad (=1 \text{ for } \omega = \omega_{bp})$$

so

$$|H(j\omega_{bp})|^2 = \frac{1}{1 + \epsilon^2} \Rightarrow \epsilon = \sqrt{10 \frac{\omega_{bp}}{\omega_0} - 1} = \epsilon_{bp}$$

In order to derive $m = \frac{\operatorname{SetCh}(\eta \epsilon^{-1})}{\operatorname{SetCh}(\eta^{-1})}$ with $|H(j\omega_{bp})|^2 = \frac{1}{1 + \epsilon_{bp}^2 C_m^2(\omega_{bp})} \dots$

NORMALIZATION AND TRANSFORMATION

Filter synthesis is performed in a domain or referred to a low pass filter with $\omega_{\text{bp}} = 1 \text{ rad/s}$. Therefore we need normalize the transformation.

→ LOW PASS

$$\omega = \frac{\omega}{\omega_{\text{bp}}} \quad \text{in order to get } \omega_{\text{bp}} = 1 \text{ rad/s}$$

Starting from the normalized Butterworth polynomials subject to $\omega_0 = 1 \text{ rad/s}$ we need first to set

$$\hat{s} = \omega_{\text{bp}} s$$

s normalized low-pass with $\omega_0 = 1 \text{ rad/s}$

$$\hat{s} \quad " \quad " \quad " \quad " \quad " \quad \omega_0 \neq 1 \text{ rad/s}$$

Then, we get

$$s = \omega_{\text{bp}} \cdot \hat{s}$$

s low-pass

→ HIGH PASS

$$\omega = \frac{\omega_{\text{bp}}}{\omega} \quad \text{in order to have } \omega_{\text{bp}} = 1 \text{ rad/s and to flip the axis}$$

$$\hat{s} = \frac{\omega_{\text{bp}}}{s}$$

→ BAND-PASS

DEF: Let's consider the transformation

$$\hat{s} = \hat{p} + \frac{1}{\hat{p}}$$

↓


$$\hat{p}^2 - \hat{s}\hat{p} + 1 = 0$$

↓

$$\hat{p} = \frac{\hat{s} \pm \sqrt{\hat{s}^2 - 4}}{2} \Rightarrow \alpha + j\omega = \frac{\Lambda + j\omega \pm \sqrt{\Lambda^2 - \omega^2 + 2j\Lambda\omega - 4}}{2}$$

Now, the $\text{Im}[\cdot]$ axis of \hat{s} ($\Lambda = 0$) is mapped into
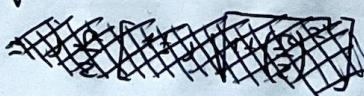
$$\alpha + j\omega = \frac{j\omega \pm j\sqrt{\omega^2 + 4}}{2} = j \frac{\omega}{2} \pm j \sqrt{1 + \left(\frac{\omega}{2}\right)^2}$$



as $\omega = 0$ and the $\text{Im}[\cdot]$ axis of \hat{s} is mapped into the point on the $\text{Im}[\cdot]$ axis of \hat{p} .

(53)

In particular,

$$\omega = 0 \Rightarrow \omega_{1,2} = \pm 1$$

$$\omega = 1 \Rightarrow \omega_{1,2} = +1,62; -0,62$$

Being ω_1 the cut-off of the low pass filter, this is equal to ω_{ap} of the band pass, as it sets the BW to 1. So, to have a BW really ω_{ap} of the band pass, we shall apply the transformation to a LP with $\omega_{ap} = \frac{1}{Q}$. Finally, to shift the cut-off frequency, we shall expand \hat{p} , the freq $s = \hat{p} \cdot \omega_0$



$$\hat{s} = Q\tilde{s} = Q \left[\hat{p} + \frac{1}{\hat{p}} \right] = Q \left[\frac{s}{\omega_0} + \frac{\omega_0}{s} \right] = Q \left[\frac{s^2 + \omega_0^2}{s\omega_0} \right]$$



which in terms of related frequency they converge to

$$\omega = Q \left(\frac{\omega^2 - \omega_0^2}{\omega\omega_0} \right)$$


ACTIVE CELLS

We can always split the T.F. in the product of 1st and 2nd order terms, so we can make each of them as a block and then cascade all of them (roughly decoupled) in order to make the full T.F.. We can use OPAMPS!

→ 1ST ORDER CELL

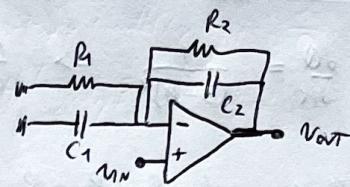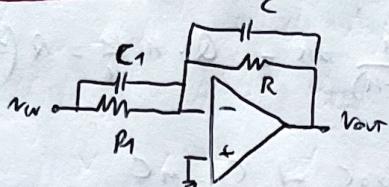

→ 2ND ORDER CELL (Sallen - Key)

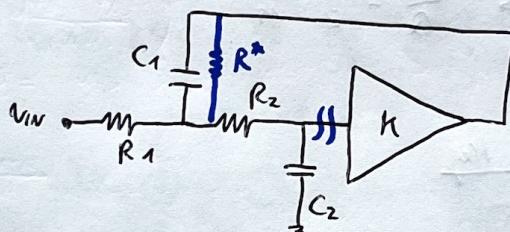

$$\Delta \text{loop}(s) = +K \cdot \frac{R_1}{R_1 + R^*}$$

$$a_1 = R^* C_1$$

$$b_1 = C_2 (R_2 + R_1 // R^*) + C_1 \cdot (R^* // R_1)$$

$$b_2 = C_1 C_2 (R^* // R_1) R_2$$

$$\Delta \text{loop}(s) = +K \cdot \frac{R_1}{R_1 + R^*} \cdot \frac{1 + \omega C_1 R^*}{1 + [C_2 (R_2 + R_1 // R^*) + C_1 (R^* // R_1)] + \omega C_1 C_2 R_2 (R^* // R_1)}$$

$\downarrow R^* \rightarrow \infty$

$$= +K \cdot \frac{\omega C_1 R_1}{\omega^2 C_1 C_2 R_1 R_2 + \omega [C_1 R_1 + C_2 (R_1 + R_2)] + 1}$$

By solving $\Delta \text{loop}(s) - 1 = 0$ we get the desired L.P. transfer:

$$\omega^2 (R_1 R_2 C_1 C_2) + \omega [R_1 (1 - K) C_1 + (R_1 + R_2) C_2] + 1 = 0$$

$$\therefore \omega_0 = \frac{1}{\sqrt{C_1 C_2 R_1 R_2}} \quad \text{and} \quad Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{C_1 R_1 + C_2 (R_1 + R_2) - K C_1 R_1}$$

$$\downarrow$$

$$= \frac{(R_1 C_1) \sqrt{R_1 R_2 C_1 C_2}}{(1 - K) + \frac{C_2}{R_1 C_1} (R_1 + R_2)} = \frac{\sqrt{\frac{R_2}{R_1} \frac{C_2}{C_1}}}{(1 - K) + \frac{C_2}{C_1} \left(1 + \frac{R_2}{R_1}\right)}$$

(55) Q signals are ratios \Rightarrow affected by sign changes, mitigated by mixing
 w/o signals are absolute values \Rightarrow affected by sign-to-sign changes

① $K \neq 1$ and $R_1 = R_2 = R$ and $C_1 = C_2 = C$

$$w_0 = \frac{1}{RC} \quad Q = \frac{1}{3-K} \quad \Rightarrow \quad n = 3 - \frac{1}{Q} \quad \text{dependent on } Q!$$


$$\frac{dQ}{dk} = \frac{1}{(3-n)^2} \quad \Rightarrow \quad \frac{dQ}{Q} = \frac{1}{(3-n)} \quad dk = Q \cdot n \frac{dn}{n} = Q \left(\frac{3-1}{Q} \right) \frac{dn}{n}$$

② $n=1$ and $R_1 = R_2 = R$ and $C_2 = C$ and $C_1 = nC$

$$w_0 = \frac{1}{\sqrt{n} RC} \quad Q = \frac{\sqrt{n}}{2} \quad \Rightarrow \quad n = 4Q^2$$

$$\frac{dQ}{dn} = \frac{1}{4\sqrt{n}} \quad \Rightarrow \quad \frac{dQ}{Q} = \frac{1}{2} \frac{dn}{n}$$

\rightarrow HIGH-PASS Sallen-Key

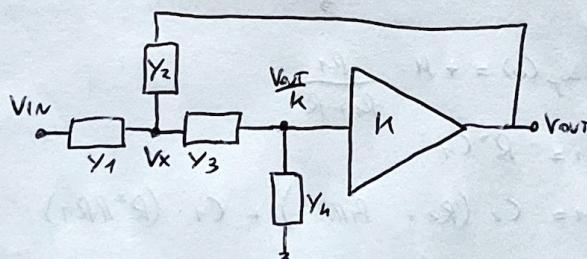

Def:

$$\begin{cases} (V_{IN} - V_x) Y_1 + (V_{OUT} - V_x) Y_2 = (V_x - \frac{V_{OUT}}{K}) Y_3 \\ V_x = \frac{V_{OUT}}{K} (1 + \frac{Y_4}{Y_3}) \end{cases}$$

\downarrow

$$V_{OUT} \left(Y_2 + \frac{Y_3}{K} \right) - V_x \left[Y_1 + Y_2 + Y_3 \right] = - V_{IN} Y_1$$

\downarrow

$$V_{OUT} \left(Y_2 + \frac{Y_3}{K} \right) - \frac{V_{OUT}}{K} \left[1 + \frac{Y_4}{Y_3} \right] \left[Y_1 + Y_2 + Y_3 \right] = - V_{IN} Y_1$$

\downarrow

$$V_{OUT} \left[Y_2 + \frac{Y_3}{K} - \frac{Y_1}{K} - \frac{Y_2}{K} - \frac{Y_3}{K} - \frac{Y_1 Y_4}{K Y_3} - \frac{Y_2 Y_4}{K Y_3} - \frac{Y_4}{K} \right] = - V_{IN} Y_1$$

\downarrow

$$\frac{V_{OUT}}{V_{IN}} = \frac{Y_1}{\frac{1}{K} \left[Y_1 + Y_2 + Y_3 + \frac{Y_1 Y_4}{Y_3} + \frac{Y_2 Y_4}{Y_3} + Y_4 - K Y_2 \right]} = \frac{K Y_1 Y_3}{Y_4 \left[Y_1 + Y_2 + Y_3 \right] + Y_1 Y_3 + Y_2 Y_3 (1 - K)}$$

→ UNIVERSAL CELL

Also called Koenig - Buelmann - Neumark (KBN)

DEF: let's consider a high-pass T.F.

$$\frac{V_{HP}(s)}{V_N} = \frac{\gamma s^2}{(s^2 + \frac{s w_0}{Q} + \frac{w_0^2}{\gamma^2})}$$


In order to let the integrator appear, let's divide for the highest power of s :

$$V_{HP} \left[1 + \frac{w_0}{Qs} + \frac{w_0^2}{s^2} \right] = \gamma V_N$$

↓

$$V_{HP} = \gamma V_N - \frac{w_0}{s} \frac{V_{HP}}{Q} - \frac{w_0^2}{s^2} V_{HP}$$

BLOCK DIAGRAM:

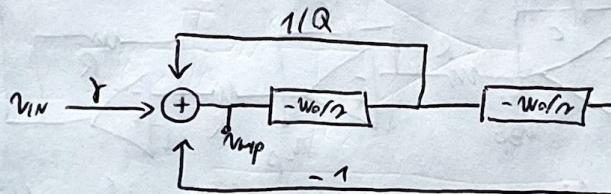


After the first integrator we get a BAND-PASS

$$\frac{V_{BP}(s)}{V_N(s)} = - \frac{\gamma w_0 s}{(s^2 + \frac{s w_0}{Q} + \frac{w_0^2}{\gamma^2})}$$

and after the next we get a LOW-PASS
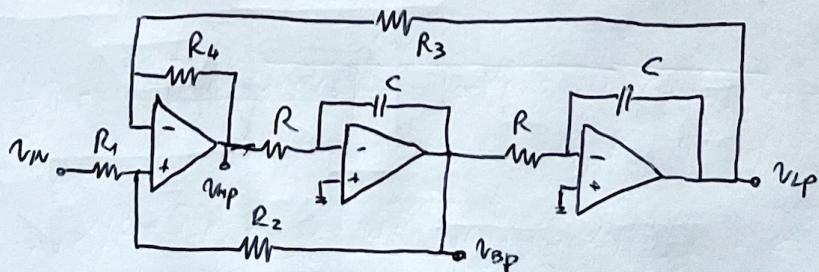
$$\frac{V_{LP}(s)}{V_N(s)} = \frac{\gamma w_0 s^2}{(s^2 + \frac{s w_0}{Q} + \frac{w_0^2}{\gamma^2})}$$





$$\Rightarrow V_{HP}(s) = \frac{R_2}{R_1 + R_2} \cdot \frac{R_3 + R_4}{R_3} \cdot V_N(s) + \frac{R_1}{R_1 + R_2} \cdot \frac{R_3 + R_4}{R_3} V_{BP}(s) + \left(-\frac{R_4}{R_3} \right) V_{LP}(s)$$

So we get

$$R_4 = R_3 \quad (\text{---} -1) \quad \gamma = \frac{2R_2}{R_1 + R_2} \quad \text{and} \quad \frac{1}{Q} = \frac{2R_1}{R_1 + R_2}$$

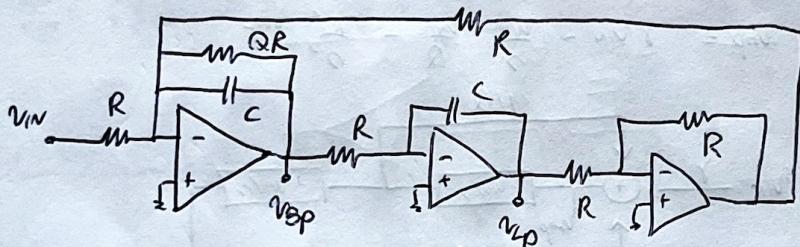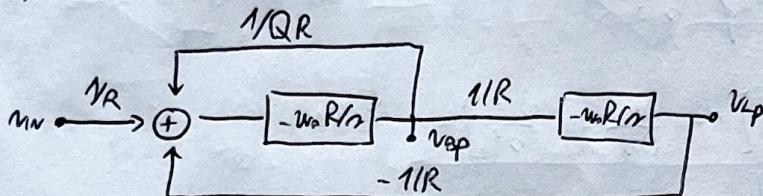(57) $\frac{B_1}{R_1} = 2Q - 1$ and $\lambda = \left(2 - \frac{1}{Q}\right)$ dependent of each other!
 If we sum the three digits in a word and we may get a T.F. with the zeros.

→ Tor-Tomas Am FLEISCHER-THOMAS
 We may sum just signs instead of numbers by using an integrator V.C.. To this aim we need to divide besides ~~the~~ entry the integrator by $\frac{1}{R}$ and to multiply integrator T.F. by R.




In a fully differential mode we don't need the resistors, it's enough to flip the cables.

By using with m_0 in all the V.C. we get a Fleischer-Thom. all with also the zeros.

The idea is to exploit interactions between different components in the same cell in order to compensate nonidealities. In active cells instead, each cell contributes independently to mobility.

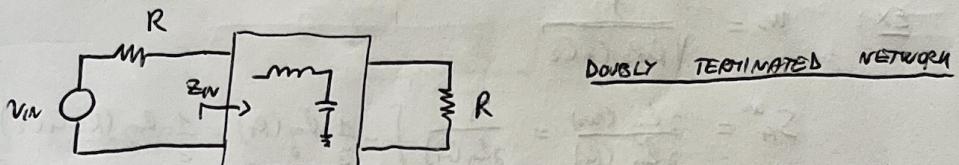DEM: These networks are PASSIVE COMPONENTS, like this:



At the maximum of the T.F. $Z_N = R$. At the mid frequency or the powers delivered to the load can be written as

$$P_L = \frac{\frac{V_{IN}^2}{2}}{R} = \frac{V_{IN}^2}{2R} |T(j\omega, X_0)|^2 \quad X_0 \triangleq \text{mid value for } L \text{ and } C$$

Let's assume to have a maximum Q $\omega = \omega^*$, then

$$\left. \frac{\partial P_L}{\partial \omega} \right|_{\omega=\omega^*} = \frac{V_{IN}^2}{2R} \cdot 2 |T(j\omega^*, X_0)| \cdot \frac{\partial |T(j\omega^*, X_0)|}{\partial \omega} \Big|_{\omega=\omega^*} = 0$$

$$\left. \frac{\partial}{\partial \omega} |T(j\omega^*, X_0)| \right|_{\omega=\omega^*} = 0 = \left. \frac{\partial}{\partial X} |T(j\omega^*, X)| \right|_{X=X_0} \quad \text{by an absolute maximum}$$


So the reactance of the T.F. to minimum of L and C is nil at the powers and remains nil around it due to symmetry (ORCHARD THEOREM)

How to implement resistors?


→ CREATORS

They are active circuits to generate an inductive impedance

(1)

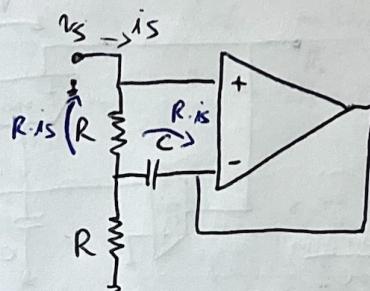

\Leftrightarrow

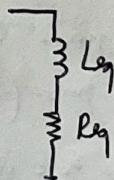

$$v_S = R \cdot i_S + (i_S + R \cdot i_S \cdot C) \cdot R$$

$$\downarrow \\ = i_S [2R + sCR^2]$$

29 OCT 2024

SENSITIVITY ANALYSIS

$$S_x^Y = \frac{\frac{\partial Y}{\partial x}}{Y} = \frac{\partial \log(Y)}{\partial \log(x)}$$

$x = \text{unit parameter}$
 $y = \text{filter parameter}$
 $\log = \text{natural log ln}$

Ex: $N_D = \frac{1}{R_1 R_2 C_1 C_2}$

$$S_{N_D}^{W_0} = \frac{\partial \log(N_D)}{\partial \log(R_1)} = \frac{\partial \log(N_D)}{\partial \log(R_1)} \left[-\frac{1}{2} \log(R_1) - \frac{1}{2} \log(R_2 C_1 C_2) \right] = -\frac{1}{2}$$

same for $S_{R_2}^{W_0}$, $S_{C_1}^{W_0}$, $S_{C_2}^{W_0}$, and for $S_K^{W_0} = 0$

Ex: $Q = \frac{1}{[R_1(1-k)C_1 + (R_1+R_2)C_2] W_0}$

$$\begin{aligned} S_Q^{W_0} &= \frac{\partial}{\partial \log(R_1)} \left[-\log(W_0) - \log(R_1(1-k)(1 + (R_1+R_2)C_2)) \right] = \\ &= \frac{1}{2} - \frac{R_1}{2R_1} \left[\log(R_1(1-k)(1 + (R_1+R_2)C_2)) \right] = \\ &= \frac{1}{2} - R_1 \frac{(1-k)(C_1 + C_2)}{R_1(1-k)(1 + (R_1+R_2)C_2)} = \\ &= \frac{R_1[1-k](C_1 + (R_1+R_2)C_2) - 2C_1R_1(1-k) - 2C_2R_1}{2[R_1(1-k)(1 + (R_1+R_2)C_2)]} = \\ &= -\frac{C_1R_1(1-k) + (R_1 - R_2)C_2}{2[R_1(1-k)(1 + (R_1+R_2)C_2)]} \end{aligned}$$

The others can be found similarly in the same way...

MISMATCH ISSUE IN GYRATORS

If the two gm_2 transconductances do not match, we have that

$$gm_2' = gm_2 + \frac{\Delta gm}{2}$$

$$gm_2'' = gm_2 + \left(-\frac{\Delta gm}{2}\right)$$



$$i_{IN} = gm_2' v_c = \frac{v_s}{2C} \frac{gm_1 gm_2'}{gm_2 + \frac{\Delta gm}{2}} + \frac{v_s}{2C} \frac{gm_1 \Delta gm}{gm_2 + \frac{\Delta gm}{2}}$$

$$i_{OUT} = gm_2'' v_c = \frac{v_s}{2C} \frac{gm_1 gm_2''}{gm_2 - \frac{\Delta gm}{2}} - \frac{v_s}{2C} \frac{gm_1 \Delta gm}{gm_2 - \frac{\Delta gm}{2}}$$

$$i_{IN} - i_{OUT} = \Delta i = \frac{v_s}{2C} \frac{gm_1}{gm_2} \frac{\Delta gm}{gm_2} = i_s \frac{\Delta gm}{gm_2} = \frac{v_s}{2Lg} \frac{\Delta gm}{gm_2}$$


We basically get the return:
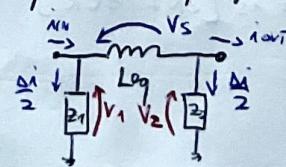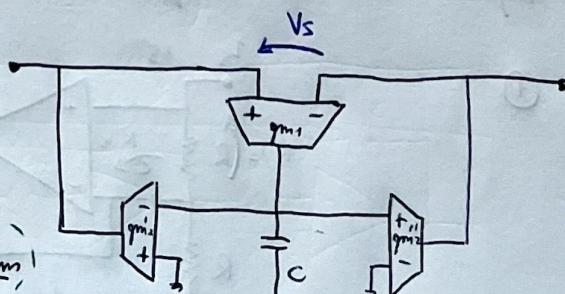
$$z_2 = \frac{v_2}{\Delta i} ; z_1 = \frac{v_1}{\Delta i}$$



$$\begin{cases} v_1 = \frac{v_s}{2} + v_{cm} \\ v_2 = -\frac{v_s}{2} + v_{cm} \end{cases}$$

② Antenna Circuit


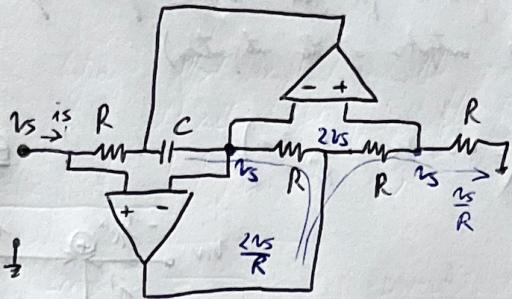


$$\frac{2V_s}{R} \cdot \frac{1}{2C} = i_s \cdot R$$

↓

$$\frac{2V_s}{i_s} = \approx CR^2$$

③ Other solutions

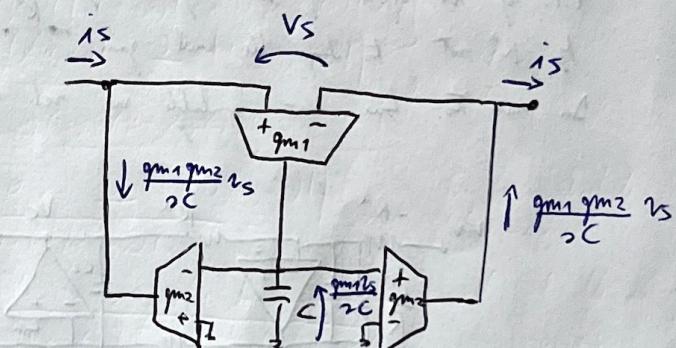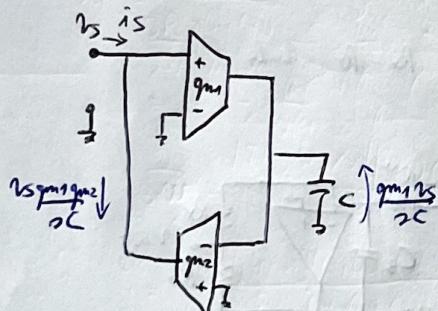

Problems of generators are

- { - limited GSWP of active shorts
- noise


→ INTEGRATORS (DEVI.)

Let's consider this 3rd order ladder network:

$$\text{KVL: } v_{in} - v_c = (sL_1 + R)i_1$$

$$\text{KVL: } v_c - v_{out} = sL_2 i_2$$

$$\text{KCL: } i_1 - i_2 = sC v_c$$

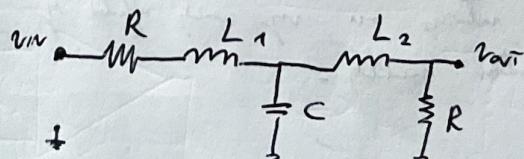

Find the nulls
(inductor anti, capacitor antipar)

Now write the anti as auxiliary voltages divided by an auxiliary resistance R'

$$\left\{ \begin{array}{l} v_{in} - v_c = \frac{sL_1 + R}{R'} \cdot v_1 \\ v_c - v_{out} = \frac{sL_2}{R'} v_2 \end{array} \right.$$

$$\frac{v_1 - v_2}{R'} = sC v_c$$

$$v_{out} = \frac{R}{R'} v_2$$

(61) Now divide each equation for the highest power of s in order to let the integrators appear: (with the outputs of the integrators)

↓

$$v_1 = -\frac{R^a}{sL_1} \left(-v_{IN} + v_C + \frac{R^a}{R^a} v_1 \right)$$


Block Diagram

~~v_{IN}~~

$$v_C = -\frac{1}{sCR^a} (-v_1 + v_2)$$


$$v_2 = -\frac{R^a}{sL_2} (-v_C + v_{out})$$

$$v_{out} = \frac{R^a}{R^a} v_2$$

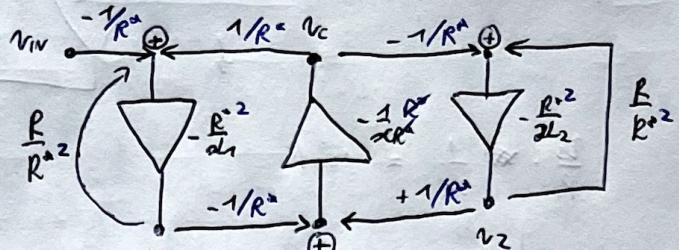

We may use initial gains in order to remove signals, so we need to divide each T.F. of the inputs of the integrator by $\frac{1}{R^a}$ and then to multiply each integrator T.F. by R^a , not to change the overall gain.

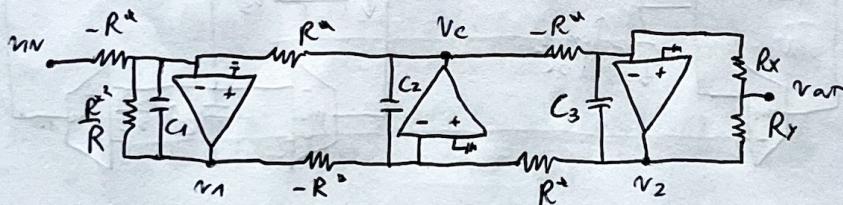In order to have v_{out} available we add an $R_x - R_y$ bridge



$$\left\{ R_x + R_y = \frac{R^a}{R} \right.$$

$$\left. v_{out} = \frac{R_x}{R_x + R_y} v_2 = \frac{R}{R^a} v_2 \Rightarrow R_x = R^a \text{ and } R_y = \frac{R^a}{R} - R^a \right.$$

The resistors are very nearly affected by feedback capacitors' variability, but they are affected by resistor variability.