

Noise And Op-Amp Non-Idealities

Dynamic Range \geq ratio between maximum and minimum signal levels handled by the circuit.

DEF: Let's consider this circuit

The maximum output signal is $2V_{DD}$, so a sinusoid with $V_{PEAK} = \frac{2V_{DD}}{2}$, so $\langle V_{out}^2 \rangle = \frac{d^2 V_{DD}^2}{8}$

While the RMS value of the sinusoid due to just the resistor R is

$$uNTR \cdot \frac{1}{4RC} = \frac{uT}{C}$$

and the additional noise due to the amplifier is $F \cdot \frac{uT}{C}$, so we get

$$DR = \sqrt{\frac{2^2 V_{DD}^2 / 8}{(1+F) uT / C}} = 2V_{DD} \sqrt{\frac{C}{8uT(1+F)}}$$

So, to measure the DR (which means to measure the number of bits of an A/D converter, being $DR = \frac{FSR}{LSB}$) we need to measure both C (more one) and V_{DD}

(more power dissipation)

On each ~~full~~ half-period the capacitor is charged up to $2V_{DD}$ and then discharged, so it dissipates

$$\frac{2V_{DD} \cdot C \cdot V_{DD}}{T} \cdot \frac{\Delta Q}{\Delta t}$$



Noise

Let's consider this amplifier

$$\textcircled{1} \quad \text{error}_1 = L_1 \cdot \frac{R}{R_1} \cdot \frac{1}{4\pi f_0 R C}$$


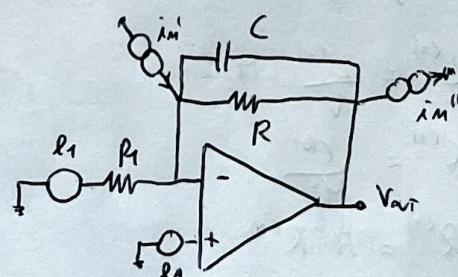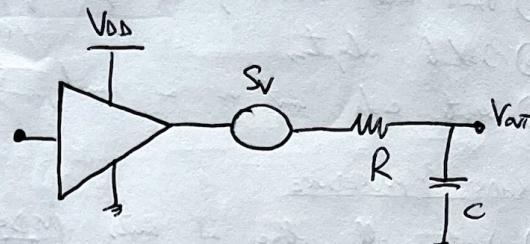
$$S_{V_{out}, M} = S_{V_{in}, M} \left(\frac{R}{R_1} \right)^2 \frac{1}{4RC} = \frac{uT}{C} \frac{R}{R_1}$$



$$\textcircled{2} \quad V_{out,2} \Rightarrow S_{I,R2} \cdot R^2 \cdot \frac{1}{4RC} = \frac{hT}{C}$$

$$\textcircled{3} \quad V_{out,A} \Rightarrow S_A \cdot \frac{w_0}{4} + S_A \left(1 + \frac{R}{R_1}\right)^2 \frac{w_0}{4}$$

we take two into account due to the finite GBWP of the amplifier, so that we consider the HF transfer to be limited by the ENBW = $\frac{w_0}{4}$

To be more accurate we should notice that the finite comp. of the amplifier affects the small T.F., i.e.

$$L_{out,A} = L_A \left[1 + \frac{R}{R_1} \frac{1}{1 + \omega RC} \right] \cdot \frac{1}{\left(1 + \frac{\omega}{w_0}\right)} = L_A \left(1 + \frac{R}{R_1}\right) \frac{\left(1 + \frac{\omega}{w_0}\right)}{\left(1 + \frac{\omega}{w_0}\right)\left(1 + \frac{\omega}{w_0}\right)}$$

$$w_0 \text{ freq} = \frac{1}{C(R_1/R)}$$

If we rewrite it in this way, we can use the standard integral

$$\int_0^{+\infty} \left| \frac{1 + \frac{\omega}{w_0}}{\frac{\omega^2}{w_0 w_M} + \omega \frac{(w_0 + w_M)}{w_0 w_M} + 1} \right|^2 d\omega = \frac{w_0 w_M}{(w_0 + w_M)} \frac{1}{h} \left[1 + \frac{w_0 w_M}{w_0^2} \right] = ENBW$$

$$\textcircled{3} \quad L_{out,A} = S_A \cdot \left(1 + \frac{R}{R_1}\right)^2 \cdot ENBW \xrightarrow{w_M \gg w_0} S_A \cdot \left(1 + \frac{R}{R_1}\right)^2 \cdot \frac{w_0}{4} \left[1 + \frac{w_0 w_M}{w_0^2} \right]$$

which converges to the approximated result. \downarrow
 $= S_A \left(1 + \frac{R}{R_1}\right)^2 \cdot \left[\frac{w_0}{4} + \frac{w_0}{4} \left(\frac{R_1}{R_1 + R_0} \right)^2 \right]$

$$\textcircled{4} \quad \text{Sout} = \underbrace{S_{V-IN} G^2}_{\text{INPUT}} \cdot \frac{w_0}{4} + hTR \cancel{\left(\frac{w_0}{4} + S_{V-A} \left[\gamma + (1+G)^2 \right] \frac{w_0}{4} + hTR G \frac{w_0}{4} \right)} \\ \downarrow \\ = S_{V-IN}^2 \frac{w_0}{4} \left[1 + \frac{hTR}{S_{V-IN}} \left(\frac{1+G}{G^2} \right) + \frac{S_{V-A}}{S_{V-IN}} \frac{\gamma + (1+G)^2}{G^2} \right] = S_{V-IN} \cdot G^2 \frac{w_0}{4} \left[1 + F \right]$$

So, in order to minimize F , we need to

- 1) have $G > 1$
- 2) resistor value noise is $< S_{V-IN}$
- 3) amplifier noise noise is $< S_{V-IN}$
- 4) limit the bandwidth by a suitable GBWP

$$\begin{cases} G = \frac{R}{R_1} \\ \gamma = \frac{w_M}{w_0} \end{cases}$$

LADDER NETWORKS Summary

KTF-1971-1000 97A-90 and 20

2

→ KL PROCEDURE

- ① Use KL in order to write relations among STATE VARIABLES (i_L, v_C)
- ② Divide each number by the highest power of ω
- ③ Isolate integrators
- ④ Write each unit or an auxiliary voltage divided by R^a

→ FLOWCHART PROCEDURE

- ① Write all integrators and units INSIDE COMPONENTS
- ② Draw integrators
- ③ Use KL to write the inputs of integrators (i_L, v_C)
- ④ Divide the branches going into V.C. by R^a and multiply the integrators T.F. for R^a
- ⑤ Multiply units on the down side for R^a , divide branches going up for R^a and multiply branches going down for R^a
- ⑥ Multiply for (-) inputs of integrators and integrators T.F.

→ DE-NORMALIZATION

Remember $w_o \propto \frac{1}{\sqrt{LC}}$ and $Q \propto w_o RC$, so to shift us to a value N times higher we need to multiply

$$\begin{cases} L^{(1)} = \frac{L^{(0)}}{N} \\ C^{(1)} = \frac{C^{(0)}}{N} \end{cases}$$

This does not change Q .


Moreover, to further decrease C without changing w_o and Q we need to multiply L and R by M :

$$\begin{cases} L^{(1)} = \frac{L^{(0)}}{N} \cdot M \\ C^{(1)} = \frac{C^{(0)}}{MN} \\ R^{(1)} = M \cdot R^{(0)} \end{cases}$$

OP-Amp Non IDEALITIES

Let's consider an integrator:

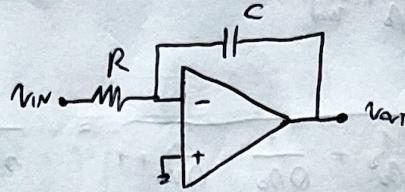We know that the forward gain is the opAMP, while the $\beta(s)$ is



$$\beta(s) = \frac{R}{R + \frac{1}{sC}} = \frac{sCR}{1 + sCR}$$

$$\begin{cases} CR = \omega_0 \\ \frac{1}{CR} = \omega_0 \end{cases}$$

$$\frac{1}{\beta}(s) = \frac{1 + \frac{s}{\omega_0}}{\frac{s}{\omega_0}} = 1 + \frac{\omega_0}{s}$$

The loop gain is equal to $|G_{loop}(s)| = -\frac{A_0}{(1+s\tau)} \frac{s\omega_0}{(1+s\omega_0)}$, it has a low frequency pole due to the opAMP, a zero in DC and a pole at ω_0 , so the loop gain @ middle freq is

$$|G_{loop}(MF)| = A_0 \frac{\omega_0}{\tau} = \frac{GBWP}{f_0} \quad (\text{we need } GBWP \geq 100 \text{ fo to have a flat loop gain})$$

and the closed loop transfer function has a pole at

$$\omega_L = \frac{\omega_0}{A_0} = \frac{1}{A_0 RC} \quad (\text{MILLER POLE})$$

and another pole at

$$\omega_H = GBWP$$

So, in the end,

$$H_{int}(s) = \frac{-A_0}{(1 + \frac{s}{\omega_L})(1 + \frac{s}{\omega_H})}$$

DC GAIN		
LOW FREQUENCY		POLE
HIGH FREQUENCY	POLE	

DC GAIN AND LF POLE EFFECT

$$T(s) = \frac{\omega_0^2 \cdot \frac{1}{s^2}}{\left(\omega_0^2 + \frac{\omega_0}{Q} + \frac{1}{s^2}\right)} = \frac{\left(\frac{-\omega_0}{s}\right)^2}{\left(-\frac{\omega_0}{s}\right)^2 - \frac{1}{Q} \left(\frac{\omega_0}{s}\right) + 1} = \frac{H_{int}^2(s)}{H_{int}^2(s) - \frac{1}{Q} H_{int}(s) + 1}$$

Let's consider now $H_{int}(s) = \frac{-A_0}{1 + \frac{s}{\omega_L}}$ at low frequency, we can write it as

$$H_{int}(s) = -\frac{1}{\left(\frac{1}{A_0} + \frac{s}{\omega_0}\right)}$$

and replace it into $T(s)$

(66)

$$\begin{aligned}
 T(s) &= \frac{\frac{1}{(\frac{1}{A_0} + \frac{2}{\omega_0})^2}}{\frac{1}{(\frac{1}{A_0} + \frac{2}{\omega_0})^2} + \frac{1}{Q(\frac{1}{A_0} + \frac{2}{\omega_0})} + 1} = \frac{1}{1 + \frac{1}{Q} \left(\frac{1}{A_0} + \frac{2}{\omega_0} \right) + \left(\frac{1}{A_0} + \frac{2}{\omega_0} \right)^2} \\
 &\downarrow \\
 &= \frac{1}{\frac{\omega^2}{\omega_0^2} + \frac{2\omega}{\omega_0 A_0} + \frac{1}{A_0^2} + \frac{1}{Q A_0} + \frac{2}{Q \omega_0} + 1} = \frac{\omega_0^2}{\omega^2 + \frac{2\omega \omega_0}{A_0} + \frac{\omega_0^2}{A_0^2} + \frac{\omega_0^2}{Q A_0} + \omega^2 + \frac{2\omega_0}{Q}} \\
 &\downarrow \\
 &= \frac{\omega_0^2}{\omega^2 + \omega \omega_0 \left(\frac{1}{Q} + \frac{2}{A_0} \right) + \omega_0^2 \left(1 + \frac{1}{Q A_0} + \frac{1}{A_0^2} \right)}
 \end{aligned}$$

$$\Rightarrow \omega' = \omega_0 \sqrt{1 + \frac{1}{A_0 Q} + \frac{1}{A_0^2}} \quad \text{RADIAL FREQUENCY SHIFT}$$

$$\Rightarrow \frac{1}{Q'} \approx \left(\frac{1}{Q} + \frac{2}{A_0} \right) \rightarrow Q \left(\frac{1}{Q} - \frac{1}{Q'} \right) = \frac{Q' - Q}{Q' Q} \cdot Q = \frac{\Delta Q}{Q} = -\frac{2Q}{A_0} \quad \text{IN-BAND DROP}$$

→ FINITE CBWP EFFECT

Let's write now the real integrator T.F. at high frequency:

$$H_{int}(s) = -\frac{\omega_0}{s^2} \frac{1}{\left(1 + \frac{2}{\omega_m}\right)^2}$$

so we get

$$\begin{aligned}
 T(s) &= \frac{\left(\frac{\omega_0}{s}\right)^2 \cdot \frac{1}{\left(1 + \frac{2}{\omega_m}\right)^2}}{\left(\frac{\omega_0}{s}\right)^2 \frac{1}{\left(1 + \frac{2}{\omega_m}\right)^2} + \frac{\omega_0}{Q s} \frac{1}{\left(1 + \frac{2}{\omega_m}\right)} + 1} \\
 &\downarrow \\
 &= \frac{1}{1 + \frac{\omega^2}{Q \omega_0} \left(1 + \frac{2}{\omega_m}\right) + \frac{2^2}{\omega_0^2} \left(1 + \frac{2}{\omega_m}\right)^2}.
 \end{aligned}$$

This T.F. has two complex conjugate poles + the additional pole due to the integrator. Omitting to write at $|s| \ll \omega_m$ we may write

$$\left(1 + \frac{2}{\omega_m}\right)^2 \left[\frac{2^2}{\omega_0^2} + \frac{2}{Q \omega_0 \left(1 + \frac{2}{\omega_m}\right)} + \frac{1}{\left(1 + 2/\omega_m\right)^2} \right] = 0$$

$$\left(1 + \frac{2}{\omega_m}\right)^2 \left[\frac{2^2}{\omega_0^2} + \frac{2}{Q \omega_0} \left(1 - \frac{2}{\omega_m}\right) + \left(1 - \frac{2}{\omega_m}\right)^2 \right] = 0$$

so we get

$$\frac{w_0^2}{Q w_m} \left[1 - \frac{w_0}{Q w_m} + \left(\frac{w_0}{w_m} \right)^2 \right] + \frac{2}{w_0} \left(\frac{1}{Q} - 2 \frac{w_0}{w_m} \right) + 1 = 0$$

↓

$$\frac{w^2}{Q^2} + 2 \frac{w_0}{\left[1 - \frac{w_0}{Q w_m} + \left(\frac{w_0}{w_m} \right)^2 \right]} \frac{\left(1 - 2 \frac{w_0}{w_m} Q \right)}{Q} + \frac{w_0^2}{\left[1 - \frac{w_0}{Q w_m} + \left(\frac{w_0}{w_m} \right)^2 \right]} = 0$$

$$\Rightarrow w_0' = \sqrt{1 - \frac{w_0}{Q w_m} + \left(\frac{w_0}{w_m} \right)^2} \approx w_0 \left(1 + \frac{w_0}{2 Q w_m} \right) \quad (w_m \gg w_0)$$

$$\Rightarrow \frac{1}{Q'} \approx \frac{1}{Q} \frac{\left(1 - 2 \frac{w_0}{w_m} Q \right)}{\left[1 - \frac{w_0}{Q w_m} + \left(\frac{w_0}{w_m} \right)^2 \right]} \approx \left(\frac{1}{Q} - 2 \frac{w_0}{w_m} \right) \quad (w_m \gg w_0)$$

$$\text{So } \frac{Q' - Q}{Q'} \approx \frac{\Delta Q}{Q} = 2 \frac{w_0}{w_m} \cdot Q$$

Conclusion: the real response of the opAMP affects the w_0 and the Q of the real integrator, so mostly it affects the gain of the filter, which becomes more sensitive if the Q factor is higher! This happens because the $\frac{\Delta Q}{Q}$ term is proportional to Q .

Although the positive Q shifts due to HF influences may exceed the negative shift due to the DC gain and the LF pole, we consider the worst case, setting a constant on the maximum absolute value for both the positive and negative swing.

$$\left| \frac{\Delta Q}{Q} \right| \leq \text{Error \%}$$

As a final result, we may consider the contribution arising from the positive zero in the open loop Op-AMP T.F., or

$$H_{int}(s) = - \frac{w_0}{s} \left(1 - \frac{2}{w_2} \right)$$

$$T(s) = \frac{H_{int}(s)}{H_{int}^2(s) - \frac{1}{Q} H_{int}(s) + 1} = \frac{\left(\frac{w_0}{s} \right)^2 \left(1 - \frac{2}{w_2} \right)^2}{\left(\frac{w_0}{s} \right)^2 \left(1 - \frac{2}{w_2} \right)^2 + \frac{w_0}{Q s} \left(1 - \frac{2}{w_2} \right) + 1}$$

The poles will be given by the roots of

$$\frac{2}{w_0^2} + \frac{2}{Q w_0} \left(1 - \frac{2}{w_2} \right) + \left(1 - \frac{2}{w_2} \right)^2 = 0$$

(68)

So we get

$$\frac{\gamma^2}{\omega_0^2} \left[1 - \frac{\omega_0}{Q\omega_2} + \left(\frac{\omega_0}{\omega_2} \right)^2 \right] + \left(\frac{2}{Q\omega_0} \left(1 - \frac{\omega_0}{\omega_2} \right)^2 \frac{\omega_0}{\omega_2} Q \right) + 1 = 0$$

$$\downarrow$$

$$\frac{\gamma^2 + \frac{2\omega_0}{\left[1 - \frac{\omega_0}{Q\omega_2} + \left(\frac{\omega_0}{\omega_2} \right)^2 \right]}}{Q} + \frac{\left(1 - \frac{2\omega_0}{\omega_2} Q \right)}{Q} + \frac{\omega_0^2}{\left[1 - \frac{\omega_0}{Q\omega_2} + \frac{\omega_0}{\omega_2} \right]^2} = 0$$

So


$$\omega_0' = \sqrt{1 - \frac{\omega_0}{Q\omega_2} + \left(\frac{\omega_0}{\omega_2} \right)^2} \approx \omega_0 \left(1 + \frac{2\omega_0}{Q\omega_2} \right) \quad (\omega_2 \gg \omega_0)$$

$$\frac{1}{Q'} = \frac{1}{Q} \frac{\left(1 - \frac{2\omega_0}{\omega_2} Q \right)}{\sqrt{1 - \frac{\omega_0}{Q\omega_2} + \left(\frac{\omega_0}{\omega_2} \right)^2}} \approx \frac{1}{Q} \left(1 - \frac{2\omega_0}{\omega_2} \right) \quad (\omega_2 \gg \omega_0)$$

$$\downarrow$$

$$\left(\frac{1}{Q} - \frac{1}{Q'} \right) Q \approx \frac{\Delta Q}{Q} = \left(\frac{2\omega_0}{\omega_2} Q \right) \quad \text{POSITIVE SHIFT, line for the LSWP}$$

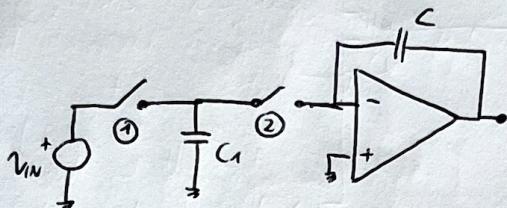In the low frequency range we'd require very large resistors in order to have suitable values of capacitors, but they are hard to be made in integrated technology, so we use switched capacitors.



Phase ① \Rightarrow ① is closed and C_1 stores $Q = C_1 \cdot V_{IN}$

Phase ② \Rightarrow ② is closed and C_1 charges C , $\Rightarrow v_C = \frac{C_1 V_{IN}}{C}$

At the output we get a staircase with slope $\frac{C_1 V_{IN}}{C \cdot T}$

The output of an integrator has a slope of

~~$\frac{V_{IN}}{RC}$~~

\Rightarrow we can say that the switched capacitor provides $R_{eq} = \frac{1}{C_1}$

- ADVANTAGES:
- much larger resistors by using null capacitors
 - no need of buffer output stages in ladder networks made of integrators
 - no dc drifts on the ratio between the capacitors, which can be controlled by null

DISADVANTAGES: we have to deal with a discrete signal, so Shanon must be respected