

PROTOTYPICAL DIFFERENTIAL STAGE

(14)

Differential amplifier \Rightarrow amplifies the potential difference, regardless of the average potential


$$CMRR \triangleq \left| \frac{G_d}{G_{av}} \right|$$

① RESISTANCES

$$G_d = \frac{g_m R_L}{2} = \frac{I R_L}{V_{DD}}$$

$$G_{av} = \frac{-v_{av}}{2R_E + \frac{1}{g_m}} \cdot R_L \approx -2g_m \frac{R_L}{2R_E} \quad (\text{HALF CIRCUIT})$$
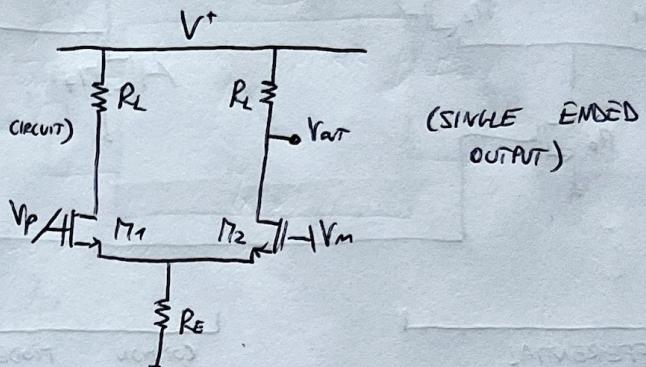
$$CMRR = \frac{g_m R_L}{2} \cdot \frac{2R_E}{R_L} = g_m R_E$$



$G_{d,max}$ limited by $I \cdot R_L = V_{L,max}$ (M_1 & M_2 may become linear)

$CMRR_{max}$ limited by the maximum current I , which is limited by the maximum V_{DD} .

② CURRENT GENERATORS

We may think to improve R_{av} without having to deal with high voltage drops by replacing R_E with current generators.


Similarly, we should also replace R_L by substituting it with a current generator.

$$G_{av} = \frac{r_o}{2R_E}$$

$$G_d = \frac{g_m r_o}{2}$$

$$CMRR = \frac{g_m r_o}{2} \cdot \frac{2R_E}{r_o} = g_m R_E$$


Maybe improve $r_{o,g}$ using CASCODES!

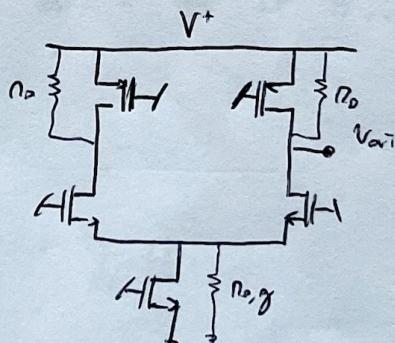

③ COMMON MODE FEEDBACK

The previous circuit indeed needs to have the two transistors perfectly matching the MOS current, otherwise the intermediate drain nodes will be out of balance to push the upper or lower pair into the linear region, until the units match. Other transistors though have lower $r_{o,g}$ so larger $G_d \Rightarrow \text{BAD!}$

We need feedback:

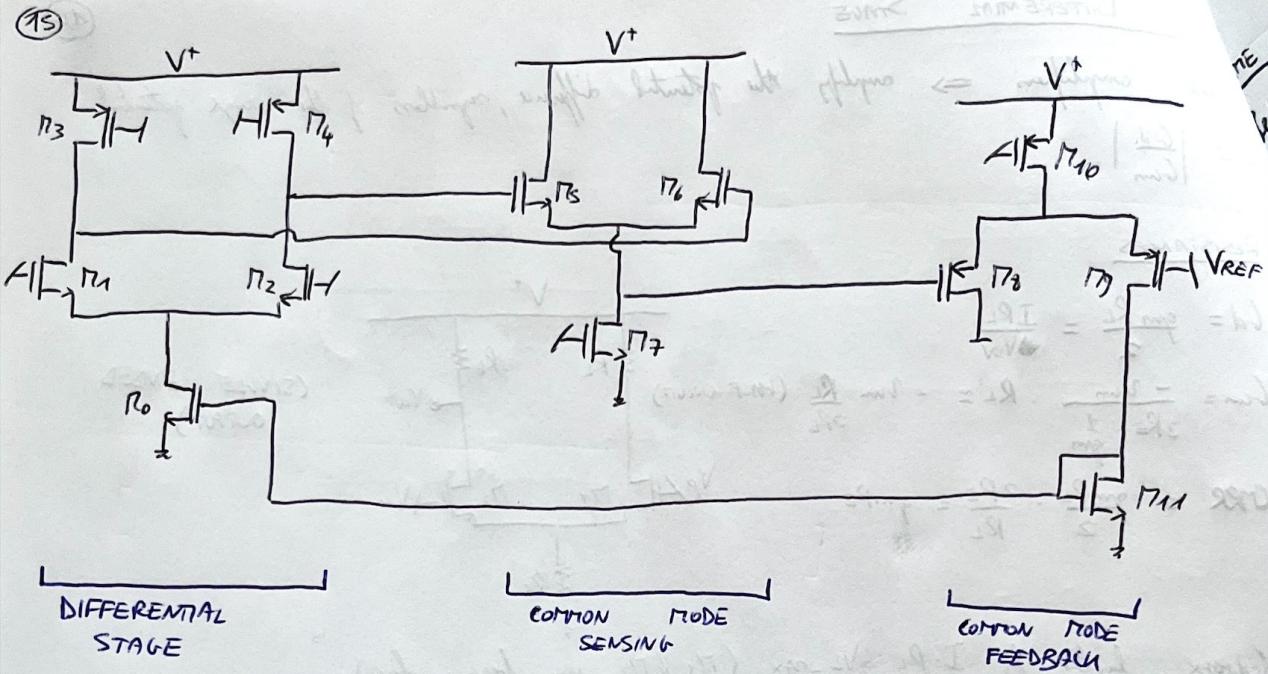

TIME CONSTANTS METHOD

Let's consider a linear time-invariant network with a resistor R_m and one capacitor:

Input Variables: i_c & V_{IN}

Output Variables: V_{out} & V_C



$$\left\{ \begin{array}{l} V_{out} = A_0 V_{IN} + R_m i_c \\ V_C = B_0 V_{IN} + R_1 \cdot i_c \end{array} \right.$$

$(A_0, B_0, R_m, R_1) \in \mathbb{R}$ being the core resistive.

Let's consider that $V_C = -\frac{i_c}{\omega C}$



$$\left\{ \begin{array}{l} V_{out} = A_0 V_{IN} - \omega C R_m i_c \\ V_C = B_0 V_{IN} - \omega C R_1 i_c \end{array} \right.$$

$$\Rightarrow V_C = \frac{B_0 V_{IN}}{1 + \omega C R_1}; \quad V_{out} = A_0 V_{IN} \left[1 - \omega C \frac{R_m B_0 / A_0}{1 + \omega C R_1} \right]$$

$$V_{out} = A_0 V_{IN} \frac{1 + \omega C (R_1 - R_m B_0 / A_0)}{1 + \omega C R_1}$$

So we have a pole at $\omega = -\frac{1}{C R_1}$ and a zero at $\omega = -\frac{1}{C (R_1 - R_m B_0 / A_0)}$

For a zero to exist it must be

$$A_0 V_{IN} + R_m i_c = 0$$



$$i_c = -\frac{A_0}{R_m} V_{IN} \quad \text{or} \quad V_{IN} = -\frac{R_m}{A_0} i_c$$

So

~~REZISTENZA SEEN~~


$$V_C = -\frac{B_0}{A_0} R_m i_c + R_1 i_c$$



$$\frac{V_C}{i_c} = \left(R_1 - \frac{R_m B_0}{A_0} \right) = R_{eq}$$

[RESISTANCE SEEN Across C when $V_{out} = 0$]

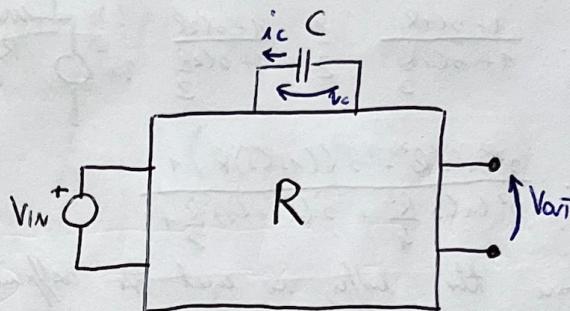
$$\Rightarrow \frac{V_{out}}{V_{IN}} = A_0 \frac{1 + \omega C R_{eq}}{1 + \omega C R_1}$$



17 Let's consider now two RC networks decoupled by a buffer, the overall T.F. will be the cascade of the two:

$$T(s) = \frac{1}{2} \cdot \frac{1 + sC_1R}{1 + sC_1\frac{R}{2}} \cdot \frac{1}{2} \cdot \frac{1 + sC_2R}{1 + sC_2\frac{R}{2}}$$
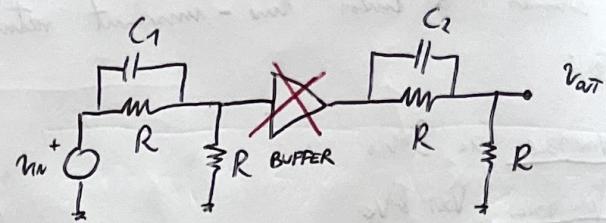
$$= \frac{1}{4} \cdot \frac{s^2 C_1 C_2 R^2 + 2(C_1 + C_2)R + 1}{s^2 C_1 C_2 \frac{R^2}{4} + 2(C_1 + C_2)\frac{R}{2} + 1}$$



If we remove the buffer, we expect the coefficients to change, but just for the resistive part. Moreover, also the DC gain changes!

$[A_0 \stackrel{\text{DEF}}{=} \text{GAIN WITH ALL THE CAPACITORS OPEN}]$

① $C_2 \rightarrow 0$

$$T(s) = A_0 \frac{s(C_1 d_1 + 1)}{s(C_1 \beta_1 + 1)}$$

and we know that $d_1 = R_{1,0}^{(0)}$ $\beta_1 = R_1^{(0)}$

~~$$T(s) = A_0 \frac{s^2(C_1 d_1 d_2 + s(C_1 d_1 + C_2 d_2) + 1)}{s^2(C_1 d_2 \beta_1 + s(C_1 \beta_1 + C_2 \beta_2) + 1)}$$~~

② $C_1 \rightarrow 0$

$$T(s) = A_0 \frac{s(C_2 d_2 + 1)}{s(C_2 \beta_2 + 1)}$$

and we know that $d_2 = R_{2,0}^{(0)}$ $\beta_2 = R_2^{(0)}$

③ $C_1 \rightarrow \infty$ (a short)

$$T(s) = A_0 \frac{s^2(C_1 C_2 d_{12} + s(C_1 R_{01}^{(0)})}{s^2(C_1 C_2 \beta_{12} + s(C_1 R_1^{(0)}))} = A_0 \frac{s^2 C_1 C_2 d_{12} + C_1 R_{01}^{(0)}}{s^2 C_1 C_2 \beta_{12} + C_1 R_1^{(0)}} =$$

$$= A_0 \frac{R_{01}^{(0)}}{R_1^{(0)}} \frac{s C_2 d_{12} / R_{01}^{(0)} + 1}{s C_2 \beta_{12} / R_1^{(0)} + 1}$$

and since the network can be seen as the one of a single capacitor C_2 and C_1 as a short, we may write

$$\begin{cases} \frac{d_{12}}{R_{01}^{(0)}} = R_{02}^{(1)} \\ \frac{\beta_{12}}{R_1^{(0)}} = R_2^{(1)} \end{cases} \Rightarrow \begin{cases} d_{12} = R_{01}^{(0)} R_{02}^{(1)} \\ \beta_{12} = R_1^{(0)} R_2^{(1)} \end{cases}$$

If we chose $C_2 \rightarrow \infty$ instead of C_1 , we'd get

$$\begin{cases} d_{12} = R_{02}^{(0)} R_{01}^{(1)} \\ \beta_{12} = R_2^{(0)} R_1^{(2)} \end{cases}$$

which must be equal to the one obtained for $C_1 \rightarrow \infty$, otherwise the T.F. is wrong!

→ POLAROID RESULTS

Starting from a 3rd order T.F., we may write

$$D(s) = b_3 s^3 + b_2 s^2 + b_1 s + 1 = \left(1 - \frac{s}{p_1}\right) \left(1 - \frac{s}{p_2}\right) \left(1 - \frac{s}{p_3}\right)$$

$$b_1 = - \left(\frac{1}{p_1} + \frac{1}{p_2} + \frac{1}{p_3} \right) \approx - \frac{1}{p_1} \quad (\text{assuming } p_1 \ll p_2, p_3)$$


Q MF

$$D(s) \approx b_3 s^3 + b_2 s^2 = s^2(b_3 s + b_2) = 0$$

$$p_3 \approx - \frac{b_2}{b_3} = \text{residue thus...}$$

→ MILLER THEOREM

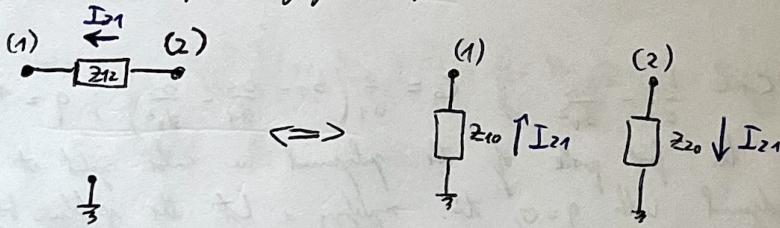We want to replace Z_{12} with two resistors Z_{10} and Z_{20} , we must set that the input entering or going out of the nodes remain unchanged



$$I_{21} = \frac{V_2 - V_1}{Z_{12}} = -\frac{V_1}{Z_{10}} \quad \left[\frac{V_2}{V_1} = K(s) \right]$$



$$V_2 - V_1 = -\frac{Z_{12}}{Z_{10}} V_1$$



$$Z_{10} = -\frac{V_1}{V_2 - V_1} \cdot Z_{12} = \frac{V_1}{V_1 - V_2} Z_{12}$$



$$\Rightarrow Y_{10} = \frac{V_1 - V_2}{V_1} Y_{12} = [1 - K(s)] Y_{12}$$

$$I_{21} = \frac{V_2 - V_1}{Z_{12}} = \frac{V_2}{Z_{20}}$$



$$Z_{20} = \frac{V_2}{V_2 - V_1} Z_{12}$$



$$Y_{20} = \frac{V_2 - V_1}{V_2} Y_{12}$$

$$\Rightarrow Y_{20} = \frac{K(s) - 1}{K(s)} Y_{12}$$

→ APPROXIMATIONS AND CIRCUIT INSIGHTS

It's important to derive some estimates of the poles and zeros by using approximations in order to understand which parameters are limiting the stability. Let's consider a third order T.F. for example:

$$D(s) = b_3 s^3 + b_2 s^2 + b_1 s + 1$$

(19) We may divide it for first order terms

$$(b_3 z^3 + b_2 z^2 + b_1 z + 1) \div (d_1 z + 1)$$

$$\begin{aligned} & \overline{b_3 z^3 + b_2 z^2 + b_1 z + 1} \\ & \overline{b_3 z^3 + \frac{b_3}{d_1} z^2} \\ & \approx \left(b_2 - \frac{b_3}{d_1} \right) z^2 + b_1 z + 1 \\ & \overline{\left(b_2 - \frac{b_3}{d_1} \right) z^2 + \frac{1}{d_1} \left(b_2 - \frac{b_3}{d_1} \right) z} \\ & \approx \left(b_1 - \frac{b_2}{d_1} - \frac{b_3}{d_1^2} \right) z + 1 \\ & \left(b_1 - \frac{b_2}{d_1} - \frac{b_3}{d_1^2} \right) z + \frac{1}{d_1} \left(b_1 - \frac{b_2}{d_1} - \frac{b_3}{d_1^2} \right) \end{aligned}$$

$$\frac{d_1 z + 1}{\begin{aligned} & b_3 z^2 + \frac{1}{d_1} \left(b_2 - \frac{b_3}{d_1} \right) z + \frac{1}{d_1} \left(b_1 - \frac{b_2}{d_1} - \frac{b_3}{d_1^2} \right) \end{aligned}}$$

So we get

$$C_2 z^2 + C_1 z + C_0 + \frac{q}{d_1 z + 1}$$

where

$$C_2 = \frac{b_3}{d_1}; \quad C_1 = \frac{b_2}{d_1} - \frac{b_3}{d_1^2}; \quad C_0 = \frac{1}{d_1} \left(b_1 - \frac{b_2}{d_1} - \frac{b_3}{d_1^2} \right); \quad q = 1 - \frac{1}{d_1} \left(b_1 - \frac{b_2}{d_1} - \frac{b_3}{d_1^2} \right)$$

If $-\frac{1}{d_1}$ was exactly the first pole of the polynomial we could split it into a 2nd and a 1st order polynomial with $q=0$, this simplifying a lot the problem. However, even if we don't have exactly p_1 , we have that it is = not by the Miller's approximation, so we may say

$$p_1 \approx -\frac{1}{b_1}$$

so we get

$$C_2 = \frac{b_3}{b_1}; \quad C_1 = \frac{b_2}{b_1} - \frac{b_3}{b_1^2}; \quad C_0 = \frac{1}{b_1} \left[b_1 - \frac{b_2}{b_1} - \frac{b_3}{b_1^2} \right]; \quad q = \frac{1}{b_1} \left(b_1 - \frac{b_2}{b_1} - \frac{b_3}{b_1^2} \right)$$

and split the denonator like this

$$(C_2 z^2 + C_1 z + 1)(1 + \alpha b_1)$$

only $q \approx 0$. It can be shown that these results are really close to the ones obtained by shorting CC and counting the remaining poles using the extended trapezoidal method.

ANGLE - ENDED OTA

The single-ended configuration is another option to guarantee consistent bias of the stage. The adoption of the current mirror leaves the current from M_4 to the current delivered by the tail, hence inverting the control logic directly in the differential stage.

In order for the bias to be consistent, we need

$$\begin{cases} I_1 = I_3 \\ I_2 = I_4 \end{cases}$$


(neglecting V_{DS} in $(V_{DS}-V_{GS})/V_A$)

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left(V_{GS,1} \right)^2 \left[1 + \frac{V_X - V_S}{V_A} \right] = I_1$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_3 \left(V_{GS,3} \right)^2 \left[1 + \frac{V_{DD} - V_X}{V_A} \right] = I_3$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_2 \left(V_{GS,2} \right)^2 \left[1 + \frac{V_{GS,2} - V_S}{V_A} \right] = I_2$$
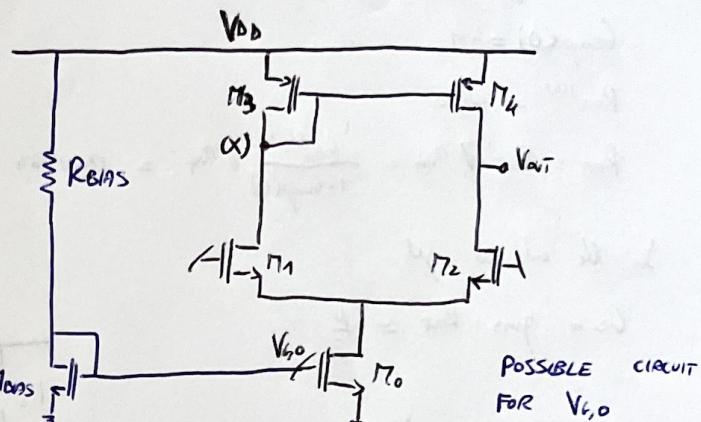
$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_4 \left(V_{GS,4} \right)^2 \left[1 + \frac{V_{DD} - V_{GS,4}}{V_A} \right] = I_4$$



POSSIBLE CIRCUIT
FOR $V_{GS,0}$

$$\frac{I_1}{I_2} = \frac{I_3}{I_4} \Rightarrow \left(1 + \frac{V_X - V_S}{V_A} \right) \left(1 + \frac{V_{DD} - V_{GS,1}}{V_A} \right) = \left(1 + \frac{V_{DD} - V_X}{V_A} \right) \left(1 + \frac{V_{GS,3} - V_S}{V_A} \right)$$

by inspection it turns out that $V_X = V_{GS,1}$

→ VOLTAGE SWINGS

$$V_{CM,1_{MAX}} = V_{DD} - V_{GS,3} + |V_T| = V_{DD} - V_{GS,3} - |V_T| + |V_T| = V_{DD} - V_{GS,3} \quad (\text{Saturation of } M_1)$$

$$V_{OT,1_{MIN}} = V_{GS,0} + V_{GS,1} = V_{GS,0} + V_{GS,1} + |V_T| \quad (\text{Saturation of } M_0)$$

Not symmetric! Towards ground it has to accommodate for a V_{GS} in addition to an overdrive voltage.

$$V_{OT,1_{MAX}} = V_{CM,1_{MIN}} - |V_T| = V_{GS,0} + V_{GS,1} \quad (\text{Saturation of } M_2)$$

$$V_{OT,1_{MIN}} = V_{DD} - V_{GS,4} \quad (\text{Saturation of } M_4)$$

→ DIFFERENTIAL GAIN

Due to the introduction of the mirror, the circuit is not symmetric anymore, since the resistances on the drain of M_1 and M_2 are different! In order to recover symmetry, we use the Norton theorem:

- in order to compute i_{ce} we need to short the drain of M_4 . In this very little the bias of M_1 and M_2 are connected to low-Z nodes, we can assume them to be 0 or with an error $\sim \frac{1}{gm_{M4}}$.

(21) Now we've restored symmetry and we see that midiff splits evenly on the two transistors, thus being the same state on small signal operation. Neglecting also the mirroring error, we get

$$i_{CC} = g_m \cdot \text{midiff}$$

- R_{out} can be computed by noticing that we have a loop acting to fix V_{out} to V_{DD} , so we may cut the loop, recompute the midpoint (V_{mid}) and compute

$$\text{loop}(0) = -1$$

$$R_{out}^{(0)} = 2R_{D2}$$

$$R_{out} = R_{out}^{(0)} \parallel R_{D4} = \frac{R_{out}^{(0)}}{1 - \text{loop}(0)} \parallel R_{D4} = R_{D2}/R_{D4}$$

In the end we get

$$G_{D2} = g_{mD2} \cdot R_{out} = \frac{k}{2}$$

